

## CHAPTER - 6 - DIGITAL CIRCUITS

→ Digital Electronics used in many applications such as

1. Television
2. Communication system
3. Radar, navigation
4. Military systems.
5. Medical
6. Industrial process control
7. Consumer electronics.

→ Signals :

→ Analog signals : Analog signal is defined as signal having continuous values. They can have infinite number of different values.  
Most of the quantities observed in nature are analog.

Ex. Temperature, Brightness, Sound.

Analog signals are continuous in time & value.

→ Digital Signals : Digital signal is defined as signal which has only finite number of distinct values.

Digital signals are discrete signal. (not continuous)

Digital signals are discrete in time & value.

Ex. Binary signal can take 0 & 1 value.

Binary logic in Digital Circuit :


→ In Binary logic there are only two levels. 0 & 1.



## Positive logic:

Logic 0 (Low) = 0V


Logic 1 (High) = 5V

 

## Negative logic:

Logic 0 (Low) = +5V

Logic 1 (High) = 0V

 


Negative logic.

## Logic Operators:

- 1) AND operator.  $A \cdot B$
- 2) OR operator.  $A + B$
- 3) NOT operator.  $\bar{A} = \text{NOT} - A$

## Logic Gates:

 




Q. Draw symbol, truth table & equation for NOT, AND, NAND, OR, NOR, EXOR & EXNOR Gates

1) NOT.

Symbol.

 


$$X = \bar{A}$$

Truth table.

input	output
A	$X = \bar{A}$
0	1
1	0


2) AND

 

Truth table

inputs	output
A B	X
0 0	0
0 1	0
1 0	0
1 1	1


3) NAND

 

Truth table

inputs	output
A B	X
0 0	1
0 1	1
1 0	1
1 1	0

4) OR

 


Truth table

inputs	output
A B	X
0 0	0
0 1	1
1 0	1
1 1	1




5) NOR

 

inputs		output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	0


6) EXOR

 

Truth table

inputs		output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

7) EXNOR

 


Truth table

inputs		output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	1



Q. Implement NOT, AND & OR gates using switches.

1) NOT.

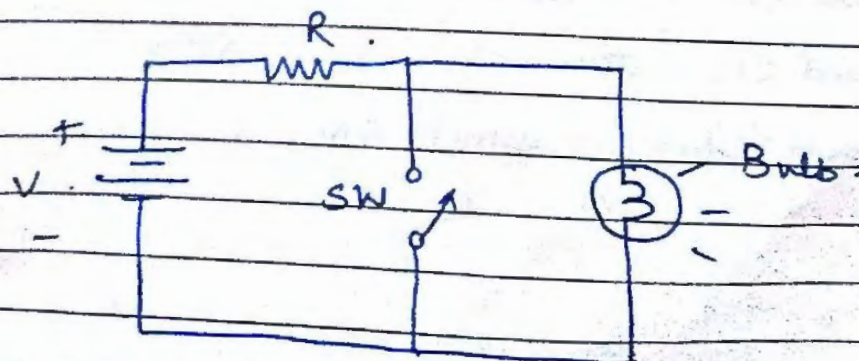




Input Switch (A)	Output Bulb (B)
open (0)	ON (1)
closed (1)	OFF (0)

 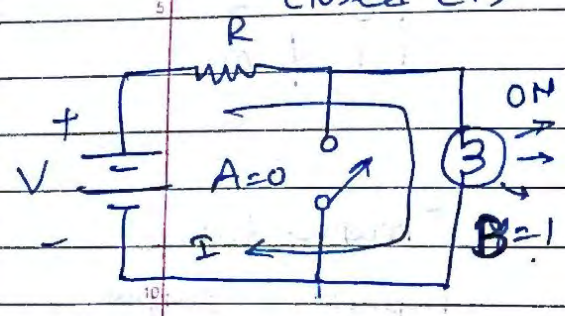


## 2) AND Gate:

 

Input A S <sub>1</sub>	Input B S <sub>2</sub>	Output (Bulb) Y
open (0)	open (0)	OFF (0)
open (0)	closed (1)	OFF (0)
closed (1)	open (0)	OFF (0)
closed (1)	closed (1)	ON (1)




### 3) OR Gate

 

Input A $S_1$	Input B $S_2$	Output Bulb (y)
open (0)	open (0)	OFF (0)
open (0)	closed (1)	ON (1)
closed (1)	open (0)	ON (1)
closed (1)	closed (1)	ON (1)

### Q. Implement AND & OR Gate using Diodes.

#### 1) AND Gate Using diode:

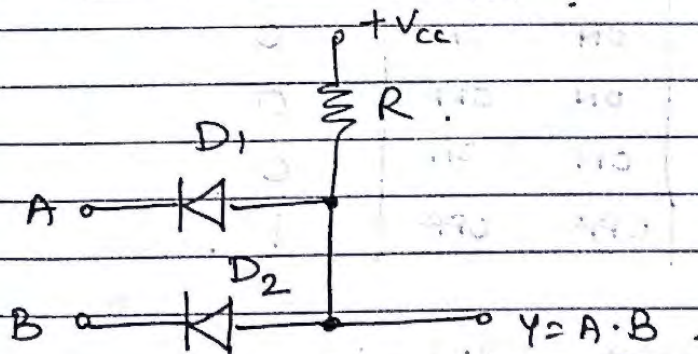

#### Operation of Circuit

- 1) When  $A = B = 0$ ,  $D_1$  &  $D_2$  forward bias, so ON.  
(Here we consider ideal diode, drop across diode is 0) then  $Y = 0$ .



2) when  $A=0$ ,  $B=1$

→  $D_1$  is forward Bias ( $A=0$ )

→  $D_2$  is reversed Bias ( $B=1$ )

So,  $D_1=ON$ ,  $D_2=OFF$ ,  $Y=0$ .

3) When  $A=0$ ,  $B=1$ .


→  $D_1 \rightarrow ON$ ,  $D_2 \rightarrow OFF$ ,  $Y=0$ .

4) When  $A=1$ ,  $B=1$ .

→ Both diode OFF, so  $Y$  is connected to  $V_{CC}$  through  $R$  so,  $Y=1$

Inputs		Diodes		Output (Y)
A	B	$D_1$	$D_2$	
0	0	ON	ON	0
0	1	ON	OFF	0
1	0	OFF	ON	0
1	1	OFF	OFF	1

OR Gate Using Diodes:

 



→ When  $A = B = 0$

→ Both diodes are reversed biased

→ So  $Y = 0$

→ When  $A = 0, B = 1$

→  $D_1$  reversed Biased

→  $D_2$  Forward Biased

So,  $Y = 1$  (Here we consider ideal diodes)

→ When  $A = 1, B = 0$

→  $D_1$  ON

→  $D_2$  OFF

& output  $Y = 1$

→ When  $A = 1, B = 1$

→ Both diodes are forward Biased &  
 $Y = 1$

Inputs		Diodes		Output
A	B	$D_1$	$D_2$	(Y)
0	0	OFF	OFF	0
0	1	OFF	ON	1
1	0	ON	OFF	1
1	1	ON	ON	1




Q. Justify NAND & NOR gate as Universal gate.

OR.  
Why NAND & NOR gate is called Universal gate?

→ NAND & NOR gate is called universal gate as we can implement all basic gates using only NAND or only NOR gate.

NAND as Universal Gate:

→ NOT using NAND:

 


→ OR using NAND:

$$X = A + B$$

$$= \overline{\overline{A + B}}$$

$$X = \overline{\bar{A} \cdot \bar{B}} \quad (\text{Using De Morgan's theorem})$$
 
$$\overline{A + B} = \bar{A} \cdot \bar{B}$$




→ AND Using NAND:

$$X = A \cdot B$$


$$= \overline{\overline{A \cdot B}}$$



 

## NOR as Universal Gate:

→ NOT using NOR:

 


→ AND using NOR:

$$X = A \cdot B$$

$$= \overline{\overline{A \cdot B}}$$

$$= \overline{A + B} \quad (\text{using De Morgan's theorem})$$

 
$$\overline{A \cdot B} = \overline{A} + \overline{B}$$



→ OR using NOR:

$$X = A + B$$

$$= \overline{\overline{A + B}}$$

 



Define:


Fan-in: Number of inputs a gate has  
Ex. 2 input gate has fan-in equal to 2.

Fan out: Maximum number of inputs of same IC family that gate can drive without falling outside the specified o/p voltage limit.

Ex. fan out is 5 means ~~one~~ <sup>gate</sup> can drive at the most 5 inputs of the same IC family.

Noise Margin:

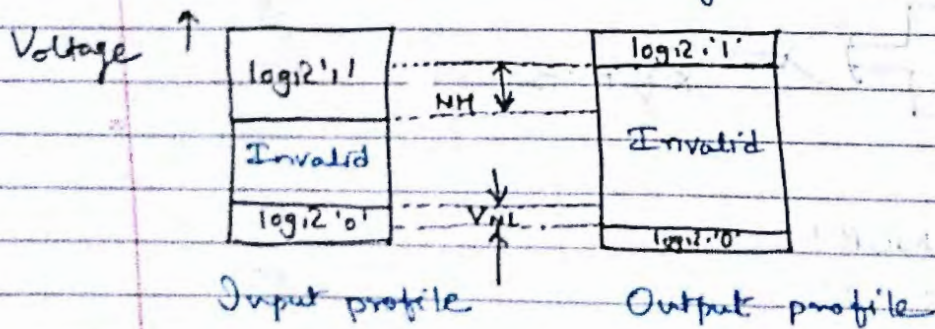
It is defined as ability of logic circuit to tolerate the noise without causing the output to change undesirably.



Propagation Delay:

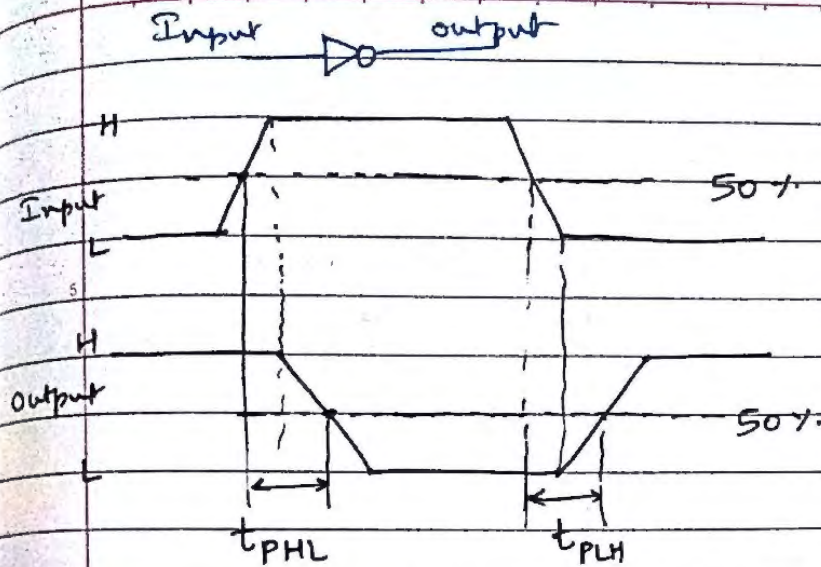- The output of logic gate does not change its state instantaneously when state of its input is changed.
- Time delay between the instant of application of an input pulse & instant of occurrence of the corresponding output pulse.





### Power Dissipation:


- Due to applied voltage & currents flowing through the logic ICs, some power will be dissipated in it in form of heat.  
power drawn by IC from power supply.

$$P = V_{CC} \times I_{CC}$$

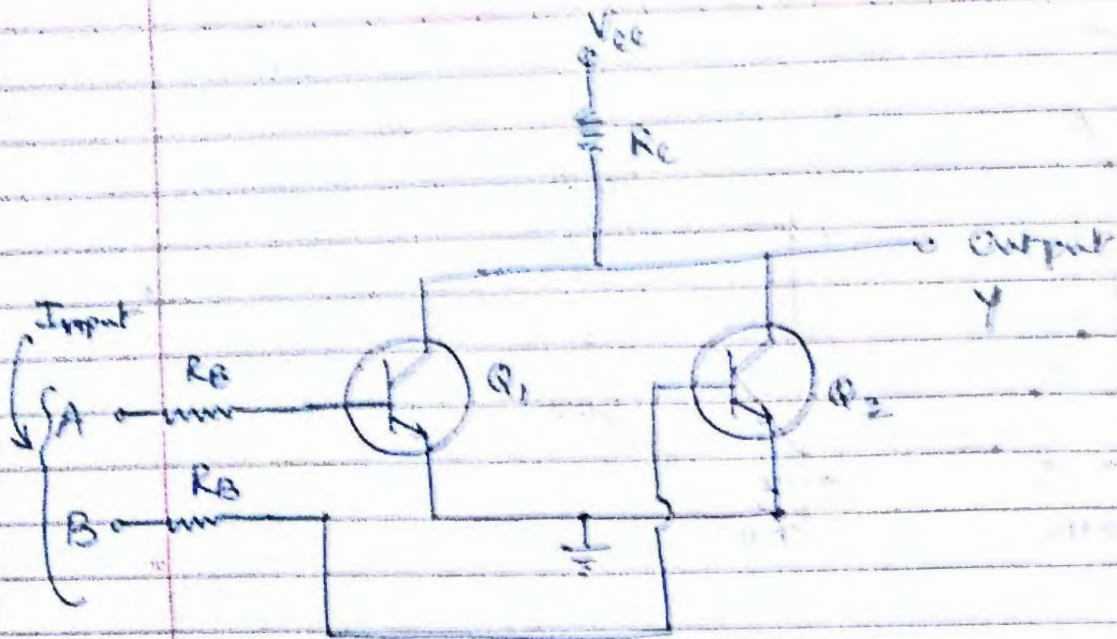Q. 20 Implement NOR & NAND using Resistor transistor logic (RTL)

- RTL is the earliest logic family but it has become obsolete now.
- Full form of RTL is resistor, transistor logic which suggests that it uses resistors & transistors.
- RTL circuits were first constructed using discrete components.





Truth table.

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Operation:

Case 1

→  $A=0, B=0$

→ Both transistor remain OFF

→ current through  $R_c$  is zero.

→ So drop across it is 0.

→ output voltage is equal to  $V_{cc}$

Case 2

$A=0, B=1$

→ with  $A=0$  &  $B=1$   $Q_1$  is OFF &  $Q_2$  ON

So output voltage  $V_{out} = V_{CE2(sat)}$  i.e. 0

So. When  $A=0, B=1$

$Y=0$



3.  $A=1, B=0$

with  $A=1$  &  $B=0$ ,  $Q_1$  is saturated &

$Q_2$  - OFF

So,  $Y=0$

$Y = V_{CE(sat)}$

4.  $A=1$  &  $B=1$

Both transistors saturated &  $Y=1$

Advantage: This uses minimum number of transistors.

Limitations:


- High power dissipation
- Its fan in is only 3
- Low noise margin (0.4V)
- Low fan out (only 3)
- Low speed.

Characteristics of RTL

	Characteristic	Value
1.	Fan in	3
2.	Fan out	3
3.	Power dissipation	30 mW
4.	Propagation delay	12 ns
5.	Noise	0.4V



Q. Implement NAND Gate using RTL.

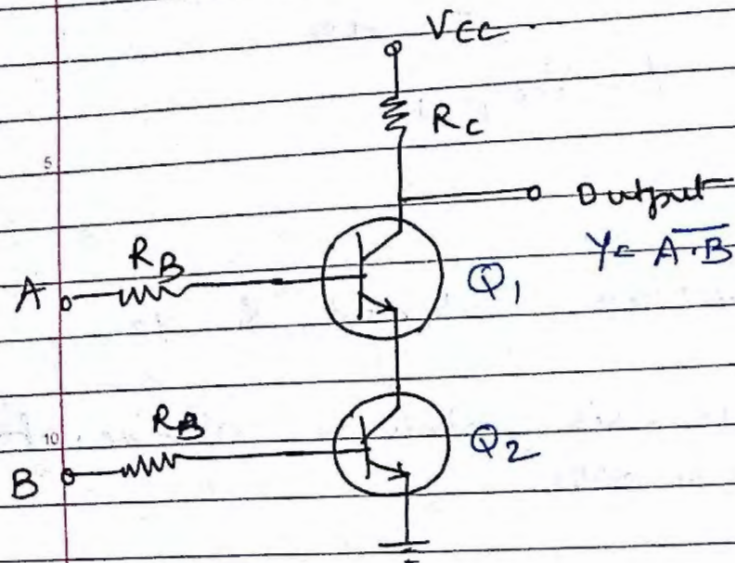

truth table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Operations:

Case.1  $A=0, B=0$

→ Both transistors  $Q_1$  &  $Q_2$  are in cutoff so output is connected to  $V_{cc}$ .  
so,  $Y=1$

Case.2  $A=0, B=1$

→ Here transistor  $Q_1$  is in cutoff & transistor  $Q_2$  BE junction is forward biased.  
→ As  $Q_1$  is in cutoff output is connected to  $V_{cc}$ .  $Y=1$

Case.3  $A=1, B=0$

→ In transistor  $Q_1$ , BE junction forward biased  
→  $Q_2$  is in cutoff  
→ Output is connected to  $V_{cc}$ .  
so,  $Y=1$


Case.4  $A=1, B=1$

→ here transistors  $Q_1$  &  $Q_2$  both saturated  
 $Y=0$



Q. Implement NAND using DTL.

→ DTL stands for diode transistor logic.

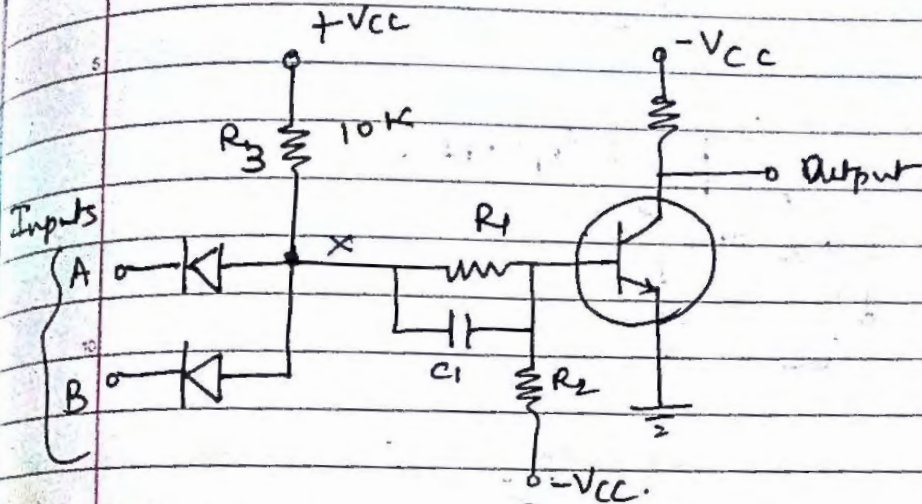


Truth table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 1. Operation with  $AB = 00, 01$  or  $10$

When  $AB = 00$ , both the diodes  $D_1$  &  $D_2$  are conducting so potential at X is  $0.7V$ .



→ When  $V_x = 0.7V$  Base of emitter is -ve as shown in circuit above, so,  $V_{BE}$  is -ve & transistor BE junction Reverse biased. So output is 1 (High).


Thus when  $AB = 00/01/10$ , output  $Y = 1$

2. Operation with  $AB = 11$

→ When  $AB = 11$ , both  $D_1$  &  $D_2$  are reverse biased and acts as open circuit,



## Equivalent Circuit B

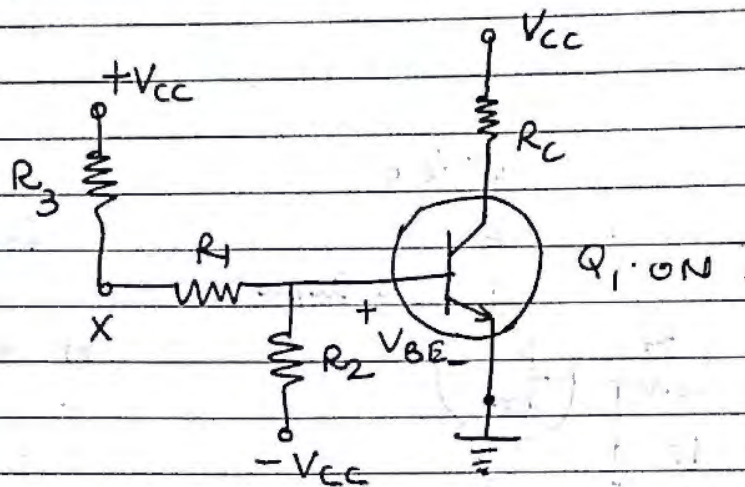

→ As both Diodes are off  $V_x$  is much higher than  $V_{BE} = 0.7V$ , so Base of  $Q_1$  transistor will be positive & BE junction will get forward biased in  $Q_1$ . So, output  $y=0$ .

Thus when  $AB=11$ ,  $y=0$ .

## Advantages:


- Greater fan-out is possible. (due to high input impedance)
- Higher noise margin than RTL.
- use of diode than Capacitor & resistors make DTL circuit more economical in IC form.

Sr. No.	Characteristics	value
1.	Voltage levels	$V_{OH} = 5V$ $V_{OL} \geq 0.2V$ $V_{IH} = 1.5V$ $V_{IL} = 1.4V$
2.	Fanout	45



3.	Power dissipation	10mW
4.	Propagation delay	75ns
5.	Noise margin	0.7V

Q. Implement NOR Gate using DTL.

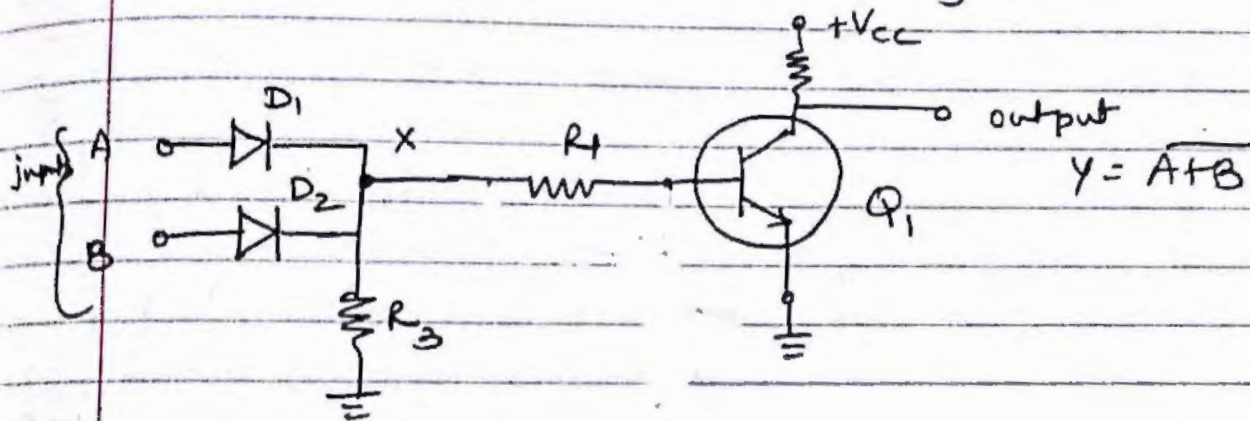

Truth table

AB	Y
0 0	1
0 1	0
1 0	0
1 1	0

Case.1 operation with

$A=0 \text{ \& } B=0$

→ Voltage at Node X is denoted by  $V_x$ .

→ When  $A=0 \text{ \& } B=0$

→ both diodes are reverse biased and  $V_x=0$  as node X is connected to ground through  $R_3$ .

→ So voltage at base of transistor is 0 & so, base to emitter junction is reverse biased so in cutoff.

→ So,  $Y=1$



Case.2      $A=0, B=1$   
                   $A=1, B=0$   
                   $A=1, B=1$

- When  $A=0$  &  $B=1$  diode  $D_2$  is ON (forward biased) and  $V_x$  is high voltage.
- When  $A=1, B=0$  diode  $D_1$  is ON, &  $V_x$  is high voltage.
- When  $A=1, B=1$ , both  $D_1$  &  $D_2$  are ON &  $V_x$  is high voltage.
- So Base of transistor  $Q_1$  is connected to high voltage, so BE junction is forward biased & current flows through transistor, so Output  $y=0$ .

### TTL Family:

- Long form of TTL is transistor logic.
- In TTL only transistors are used as their basic building blocks.

### TTL characteristics

- Texas Instruments first introduced two TTL series - 54 series & 74 series.

	TTL Series	Supply voltage Rating	Temperature Range
1.	74 series	4.75V to 5.25V	0°C to 70°C
2.	54 series	4.5V to 5.5V	-55°C to 125°C



## Important Parameters for TTL

Sr. No	Parameters	Values.
1.	Supply voltage	(74 series - 4.75 to 5.25 V 54 series - 4.5 to 5.5 V)
2.	temperatures	(74 series - 0 to 70°C 54 series - -55°C to 125°C)
3.	Voltage levels	$V_{IL(max)} = 0.8V$ $V_{OL(max)} = 0.4V$ $V_{IH(min)} = 2V$ $V_{OH(min)} = 2.4V$
4.	Noise margin	0.4V
5.	Power dissipation	10 mW
6.	Propagation delay	10 ns
7.	Fan out	10
8.	Fan in	100

## Advantages of TTL

- TTL circuits are fast
- Low propagation delay
- Power dissipation is not dependent on frequency.
- Compatible to all other families.
- High current sourcing & sinking capabilities.



## CMOS Logic:

→ CMOS Logic stands for complementary MOSFET.

### CMOS characteristics:

Sr. No	Parameters	CMOS
1.	$V_{IH}(\min)$	3.5V ( $V_{DD} = 5V$ )
2.	$V_{IL}(\max)$	1.5V
3.	$V_{OH}(\min)$	4.95V
4.	$V_{OL}(\max)$	0.05V
5.	High level Noise margin	$V_{NH} = 1.45V$
6.	Low level Noise margin	$V_{NL} = 1.45V$
7.	Noise immunity	Better than TTL
8.	Propagation delay	105ns (Metal gate CMOS)
9.	Switching speed	Less than TTL
10.	Power dissipation	$P_D \approx 0.1mW$
11.	Fan out - 50.	
12.	Power supply	3V to 15V.