

## **MOST IMPORTANT QUESTION– BEE (3110005)**

### **MIMP question**

- 1) State and explain (i) Kirchhoff's current and voltage laws (ii) Ohm's law
- 2) Derive expression for delta to star and star to delta conversion of resistive network.
- 3) Explain construction and working of single phase transformer and three phase transformer and Derive EMF equation for transformer.
- 4) Explain ideal transformer and what is difference between ideal transformer and actual transformer?
- 5) Explain Auto transformer and its applications and Explain the different types of losses in transformer
- 6) Explain types of cable and Explain Cable construction with neat sketch diagram
- 7) Explain charging and discharging equation for lead acid battery
- 8) Explain the phenomena of electrical resonance in R –L –C series circuit connected to variable frequency supply. Also derive the equation for resonance frequency. Explain Q factor and draw the resonance curve.
- 9) Established relationship between line and phase voltages and currents in balanced delta and star connection. Draw complete phasor diagram of voltages and currents.
- 10) Explain the two wattmeter method to measure power in 3- phase a.c. circuit, gives total power consumed by the circuit.
- 11) What is fuse? Give the types and purpose of fuse. Explain any one type of fuse.
- 12) What is power factor? Explain the methods to improve the power factor.
- 13) What is the need of earthing? Explain the different method of earthing. OR State the different methods of earthing and explain plate and pipe earthing with neat diagram.
- 14) Explain the concept of Rotating Magnetic Field (RMF).
- 15) Explain the construction and working of 3-phase induction motor with neat sketch.

### **IMP question**

- 1) Explain Superposition Theorem
- 2) Explain transformer on No load and on load.

- 3) Explain terms (1) A-h Capacity (2) W-h capacity and Safety precaution for electrical appliances
- 4) Give the definitions of following quantities:
  - (1) Form factor (2) Peak or Crest factor (3) rms and average value (4) Phase voltage (5) Line voltage (6) Phase current (7) Line current (8) Q-factor (9) Resonance phenomenon (10) Active power and Reactive power
- 5) Give the circuit diagram of ELCB. Explain its working in brief. (Most IMP)
- 6) Explain the construction and working of Synchronous generator with neat sketch.