

## Questions :- CH-2

- 1) Why transistor called Bipolar?
- 2) Write short note on unbiased transistor.
- 3) Explain Biased N-P-N transistor.
- 4) Explain Biased P-N-P transistor.
- 5) Explain input and output characteristic of common base configuration and derive current relation for common Base  $\Rightarrow \alpha$

Imp. 6) Derive current relation for common emitter configuration.  $\Rightarrow \beta$

- 7) Draw and explain input-output characteristic for Common emitter OR Explain Base curve and collector curve for BJT.
- 8) Define  $\alpha$  and  $\beta$ , and derive relation bet<sup>n</sup>  $\alpha$  and  $\beta$  for transistor.
- 9) Write short note on common collector configuration.
- 10) Define terms ① Load line ② Bias point or operating point (Q point)
- 11) What is load line and explain it in detail and also explain what is Q point (bias point/operating point)
- 12) Explain factors affecting stability of Q point.  $\Rightarrow V_{BE}, I_{CBO}, \beta \Rightarrow T$ .
- 13) Define stability factors,  $S, S', S''$ .
- 14) Explain fixed bias circuit in detail.
- 15) Explain emitter feedback bias circuit also explain stabilization of Q point int.
- 16) Explain collector feedback bias circuit with stabilization of Q point explain (collector to base)
- 17) describe the Voltage divider bias circuit.



$S^a = \frac{\Delta I_c}{\Delta I_{cBO}}$	$S^i = \frac{\Delta I_c}{\Delta V_{BE}}$	$S^{ii} = \frac{\Delta I_c}{\Delta \beta_{dc}}$
$V_{BE}$ and $\beta_{dc}$ constant	$I_{cBO}$ and $\beta_{dc}$ constant	$I_{cBO}$ and $V_{BE}$ constant