

SILVER OAK COLLEGE OF ENGINEERING & TECHNOLOGY**BE - SEMESTER-I • MID SEMESTER-II EXAMINATION – WINTER 2018****SUBJECT: BASIC ELECTRONICS (3110016) (IT)**

DATE: 21-12-2018

TIME: 02:00 pm to 3:30 pm

TOTAL MARKS:40

- Instructions:** 1.Q. 1 is compulsory.
 2. Figures to the right indicate full marks.
 3. Assume suitable data if required.

- Q.1 (a) Give Answer with most suitable/correct option. [05]
- (i) The number of depletion layers in a transistor is/are _____.
 (a)one (b) three (c)two (d) four
- (ii) A JFET is also called _____ transistor.
 (a) unijunction (b) Bipolar (c) Unipolar (d) Both a and b
- (iii) In p-channel JFET, the charge carriers responsible for drain current flow are _____.
 (a)Electrons (b) holes (c)both a and (d)NONE
- (iv) Which biasing method is most suitable for Q-point stability?
 (a) Fixed Bias (b) Voltage Divider Bias
 (c) Collector to Base Bias (d) Emitter Bias
- (v) In which region of operation, transistor can operate as an amplifier?
 (a)Cutoff (b)Saturation (c)Active (d)Inverse
- (b) Explain and draw the circuit of transistor as a switch. Also indicate its application. [05]

- Q.2 (a) State the three regions of BJT and explain construction characteristics of each region. [06]
- (b) Draw the structure of n-channel JFET and explain its working. [05]
- (c) Draw the structure of n-channel enhancement type MOSFET. Also, draw its drain characteristics. [04]

OR

- Q.2 (a) How to draw DC load line on the output characteristics of CE transistor? Also, locate Q-point on DC load line. [06]
- (b) Draw the structure of n-channel depletion type MOSFET and explain its working. [05]
- (c) Draw drain characteristics and transfer characteristics of n-channel JFET. [04]

- Q.3 (a) List the Biasing methods of transistor. Draw and explain the circuit of voltage divider biasing. [06]
- (b) Draw T-model and Π – model of transistors for small signal ac analysis. [05]
- (c) Write Short Note on Tunnel diode [04]

OR

- Q.3 (a) What do you mean by thermal instability in transistor? State the need of biasing the transistor. Also, draw and explain Fixed Bias method of transistor biasing. [06]
- (b) Draw and explain input output characteristics of CE transistor configuration. [05]
- (c) Explain the basic principles of operation of LED and Photodiode. [04]

