


Q.B-2

- 1) Explain all types of series clipping circuit with necessary diagrams


Series clipper circuit

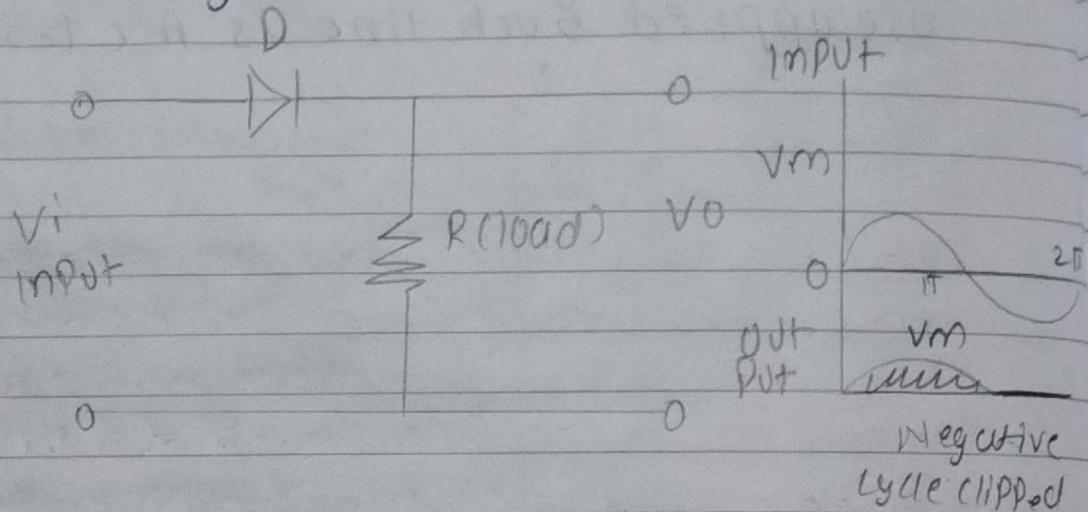- 1) Series Negative clipper

- Diode used in this configuration is assumed to be ideal one
- The clipper called as negative clipper as it clips off the negative half cycle of applied voltage



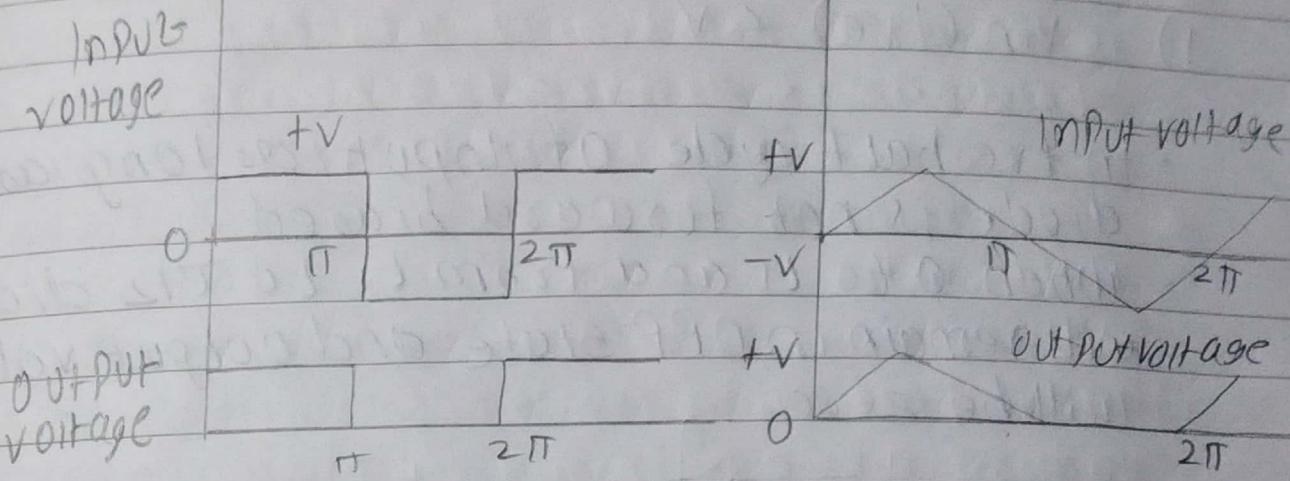
- In Positive halfcycle of sinusoidal input, the diode is forward biased. Being an ideal diode it acts as closed switch and connects load across input. The load voltage is therefore equal to input voltage in positive half cycle
- In negative halfcycle of input, the diode is reverse biased and act as open circuit switch. The load voltage is zero during negative half cycle



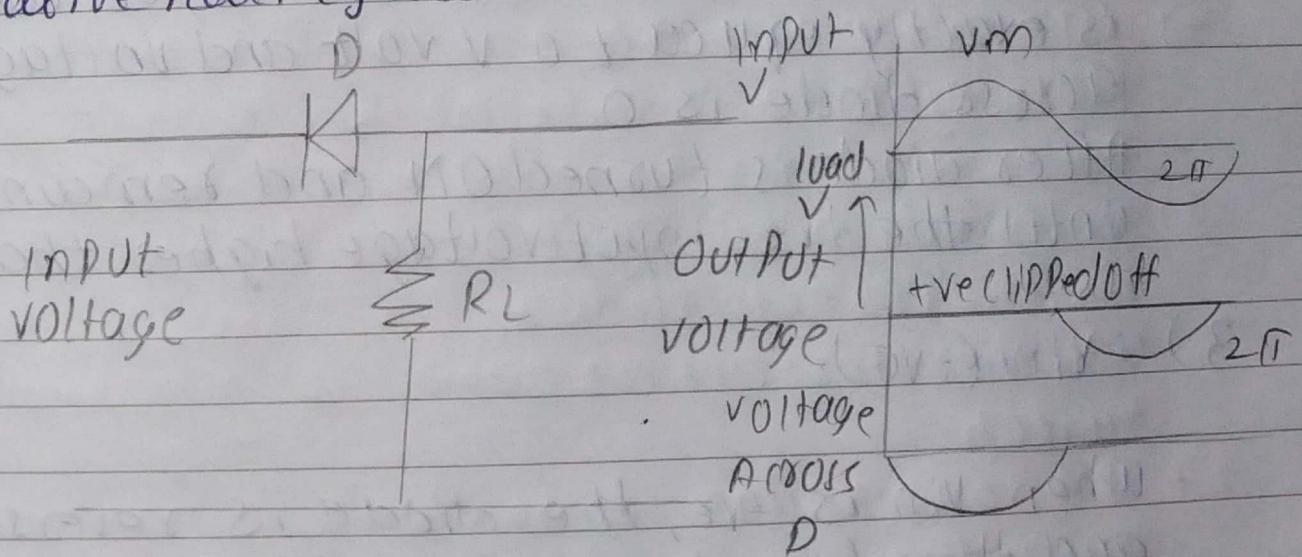2) Series positive clipper

By reversing the direction of diode, it is possible to obtain the series positive clipper configuration

- The positive side of each waveform has been clipped off as now diode conducts only in negative half cycles.




3) Biased series Negative clipper

Operation divided in three parts

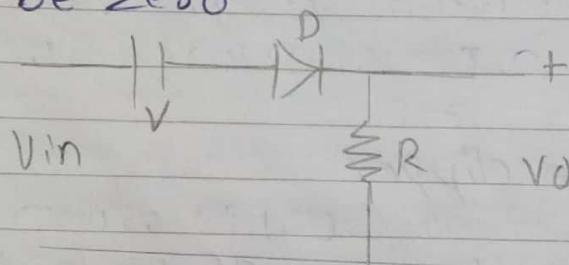1) $V_{in} (+ve) < V$

- In the half cycle of input as long as $V_{in} < V$, diode is not forward biased
- When 0 to t_1 and from t_1 to $T/2$ diode will remain in OFF state and output voltage will be zero




2) $V_{in} (+ve) > V$

- At the instant t_1 the true input voltage is exactly equal to V volt and voltage across diode is 0
- After diode is turned ON and remains ON until the true input voltage higher than V

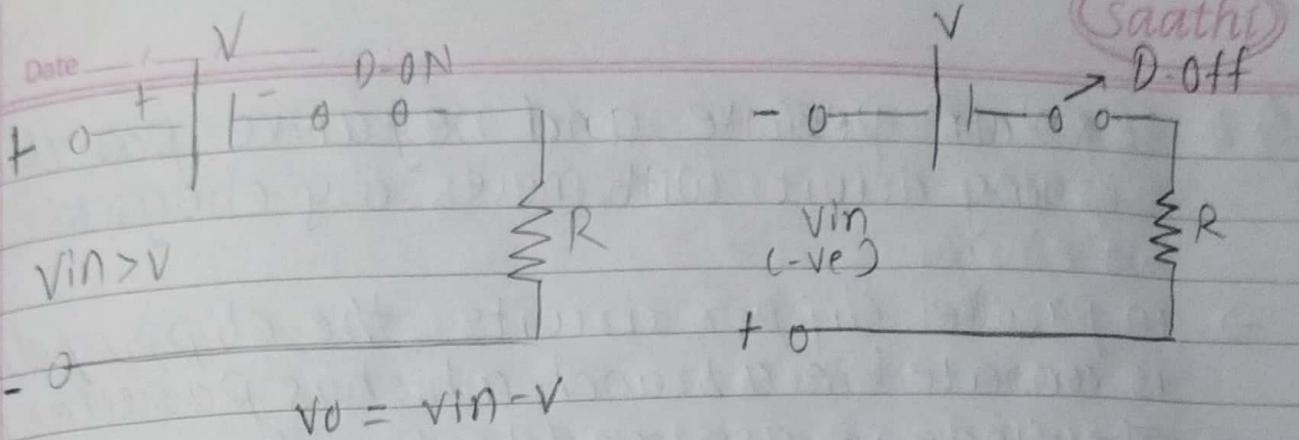3) $V_{in} (-ve)$

- When V_{in} is -ve, the diode is reverse biased and therefore it remains off. The load voltage is zero during entire -ve half cycle




a) Biased Series Positive clipper

The diode will be off and hence equivalent to an open circuited switch in whole the half cycle of Input and for a part of negative half cycle of Input.

for $V_{in} < V$, diode will forward Biased

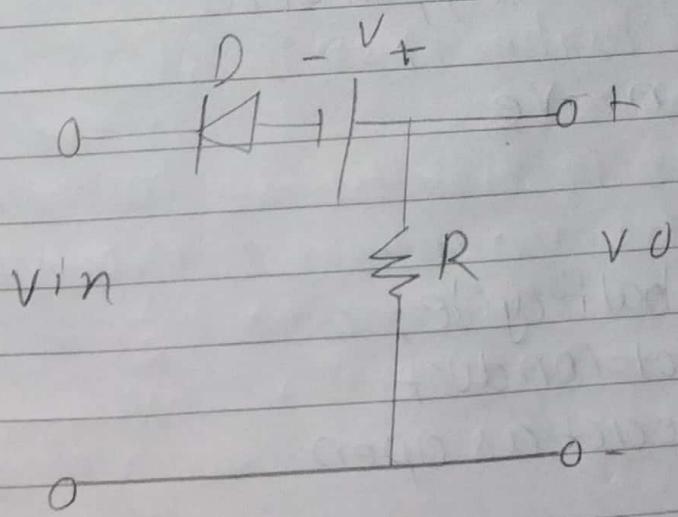for $V_{in} > V$, diode will remain off and output voltage is 0



Q-2

Explain positive and negative parallel clipping circuit with necessary diagrams

- In parallel clipper circuits, the clipping diode is connected in a branch which is parallel to load.

- The diode is assumed to be ideal one.

PARALLEL POSITIVE CLIPPER

- Operation in +ve Half cycle

- 1) In the half cycle of input voltage Diode is forward biased and therefore conducts from 0 to π

- 2) The output voltage will therefore be zero in positive half cycle of input voltage. The positive half cycle is thus clipped off




- ⇒ Operation in -ve Half cycle

- 1) In negative half cycle, diode does not conduct and therefore act as open switch


- 2) The load voltage is equal to instantaneous input voltage.

Thus negative half cycle appears across the load

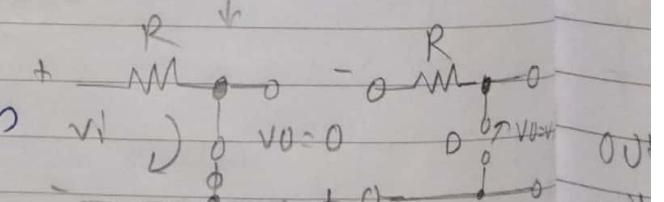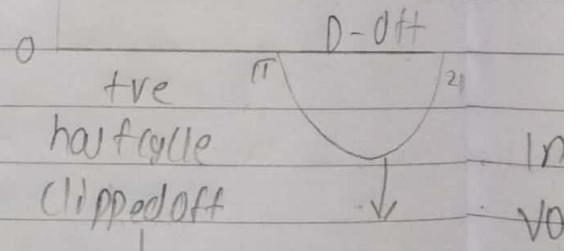
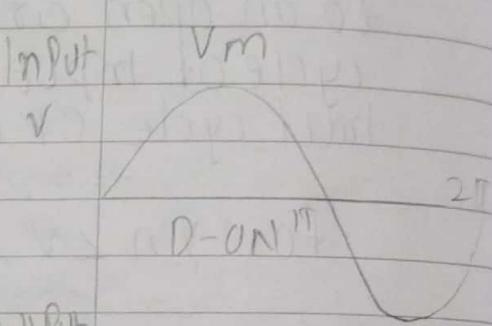
- 3) As the part clipped off it is the clipper



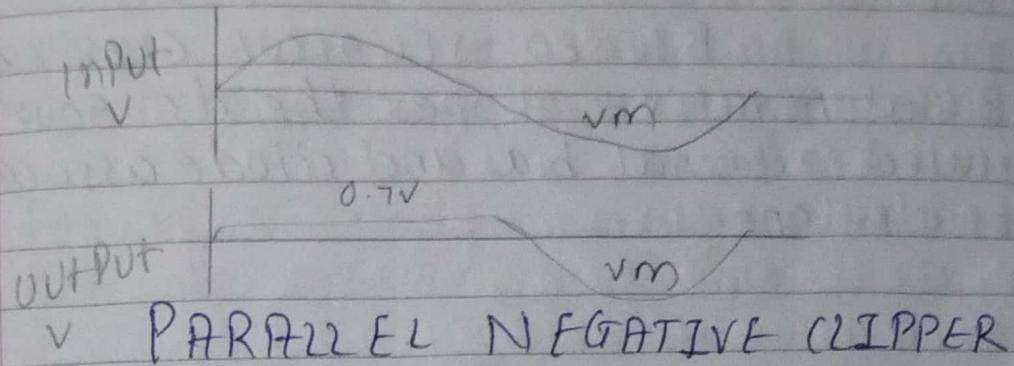- If diode is non ideal then voltage across conducting diode will be $0.7V$ instead of $0V$



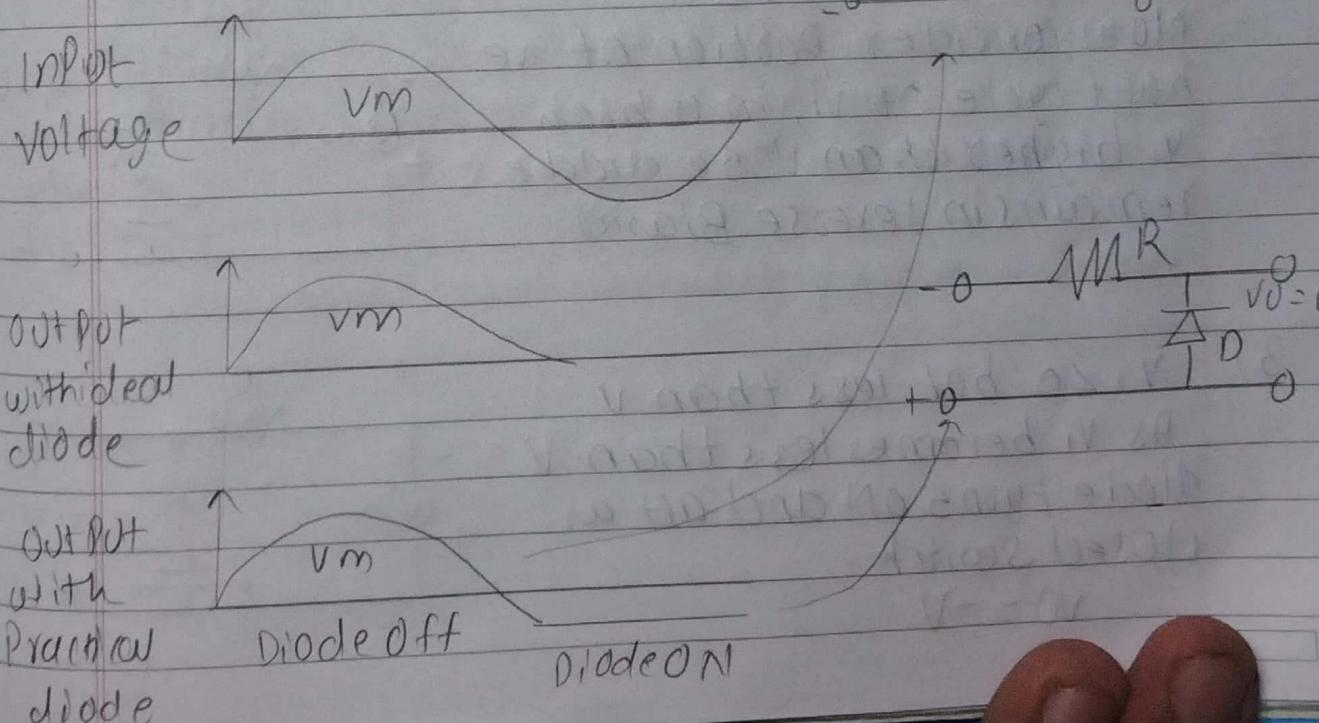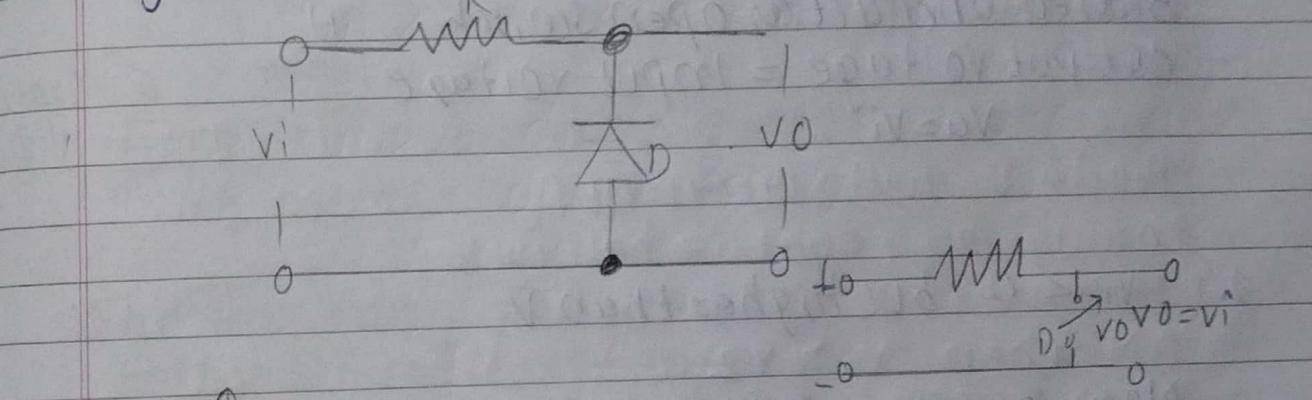- By reversing the direction of diode in parallel positive clipper we can get negative clipper
- The diode will conduct only in negative half cycle of input to clip it off.




Date _____

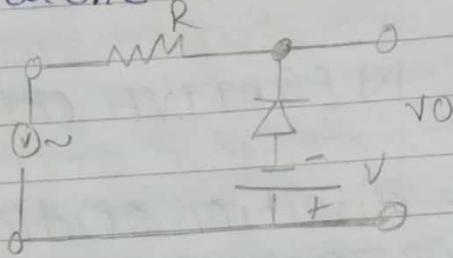Q.3 Explain Biased positive and negative parallel clipping circuit with necessary waveforms


BIASED NEGATIVE CLIPPER

- In Biased negative clipper the d.c source is called external bias and diode assumed to be ideal one



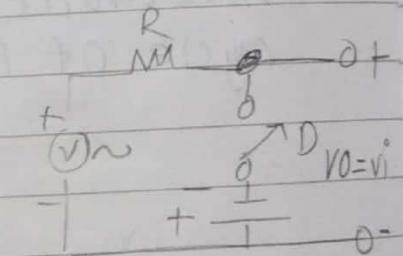
1) $Vi > 0$

- when $Vi > 0$ Diode is reverse biased and acts as open switch
- Output voltage = Input voltage $Vo = Vi$



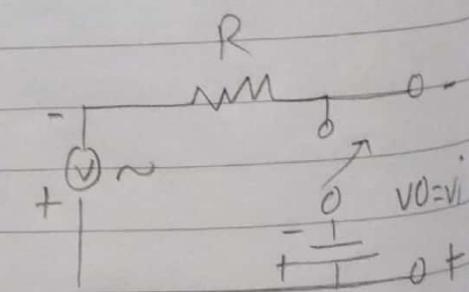2) $Vi < 0$ but higher than V


- Now consider portion of -ve half cycle of Vi , in which Vi higher than V so diode remains in reverse biased



3) $Vi < 0$ but less than V


- As Vi becomes less than V diode turns ON and act as closed switch.

$$Vo = -V$$

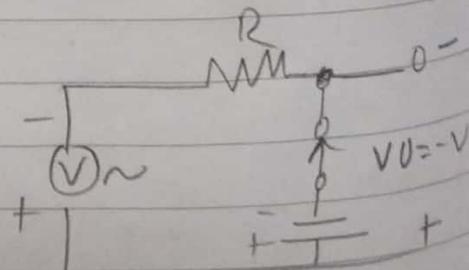


BIASED POSITIVE CLIPPER

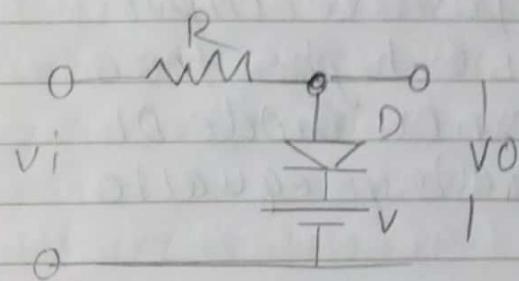- The diode will conduct only from $t=t_1$ to $t=t_2$ when $v_i > v$. When diode is conducting the output voltage equal to v
- for $v_i < v$ diode is reverse biased and turned off so $v_o = v_i$



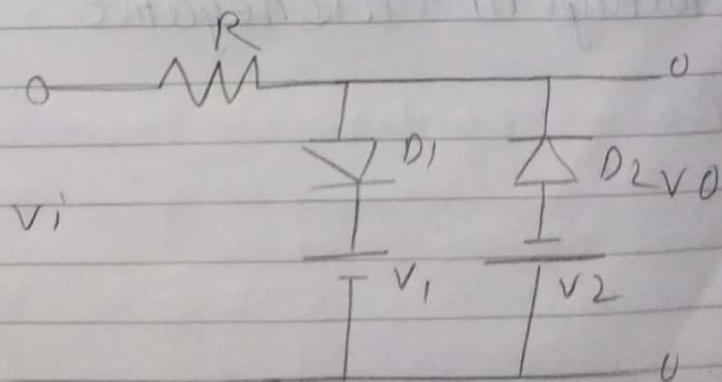
Q4 Explain combination Parallel clipping circuit with necessary waveforms

- The two-way Parallel clipper circuit to clip both half cycles of input due to presence of Diodes D_1 and D_2 in opposite direction. Both diode assumed to be ideal one




Operation in +ve Half cycle

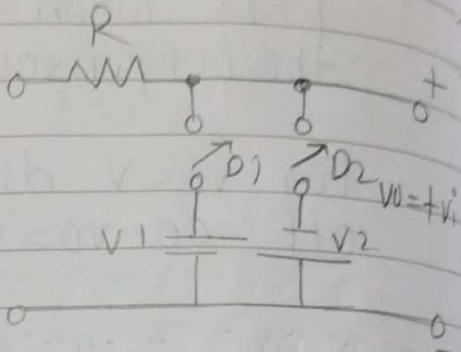- In positive half cycle
 $V_i > V_1$, D_1 will reverse bias whereas D_2 is reverse biased during complete +ve half cycle
- As soon as positive input voltage becomes higher than V_1 it will turn on Diode D_1 and output voltage equal to V_1



Operation in -ve Half cycle

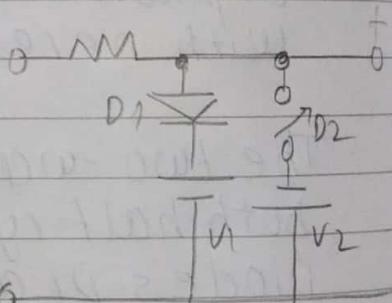- Diode D_1 will remain OFF throughout negative half cycle
- However D_2 will turn ON when $V_i > V_2$.
- And when D_1 and D_2 both are OFF output voltage equal to input voltage and it is negative




5 Explain all types of clapper circuit with necessary waveforms

- Clapper circuits are those circuits that are used to clamp the input signal to different DC level

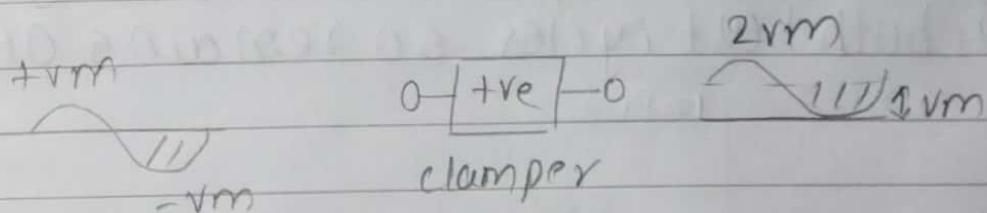1) Positive clapper


- It adds a positive DC voltage to AC input voltage. AC input is shifted upwards




- The clamping network will always consist of three elements: capacitor, diode, Resistor

Some assumptions

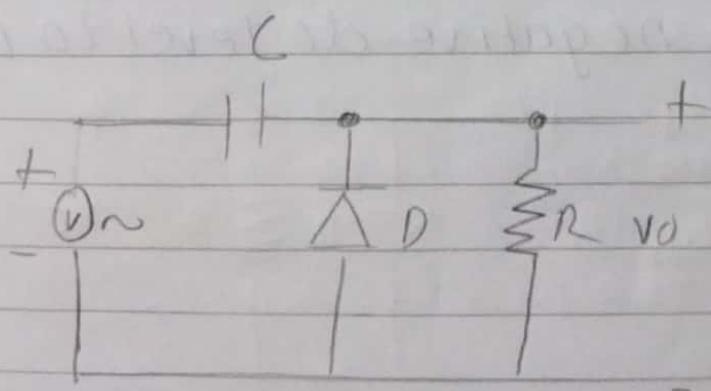
- Input is perfect sine waveform
- Diode to be ideal one
- $RC > 100T$



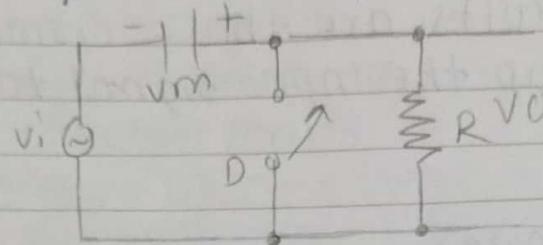- In first negative half cycle after turning on the circuit diode act as close switch and charges capacitor to peak input voltage




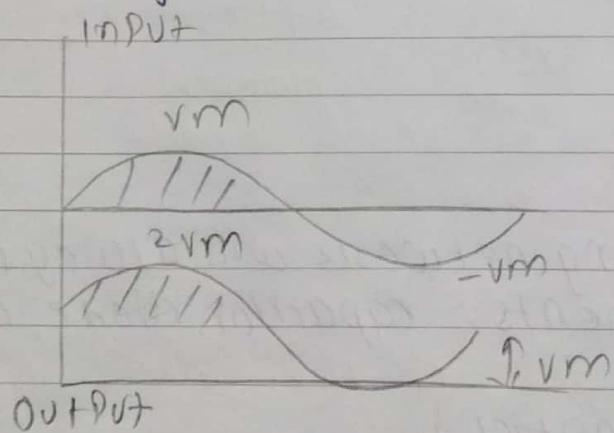- In all Positive and negative half cycles due to large RC time constant the capacitor does not loose too much charge so V_O almost remains constant
- So for rest of operation diode is reverse biased in both half cycles, so remains OFF





⇒ NEGATIVE CLAMPER

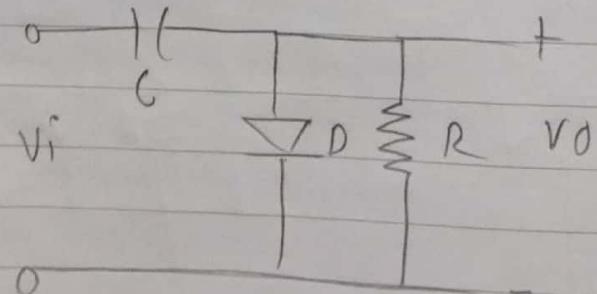- It adds a negative dc level to input signal



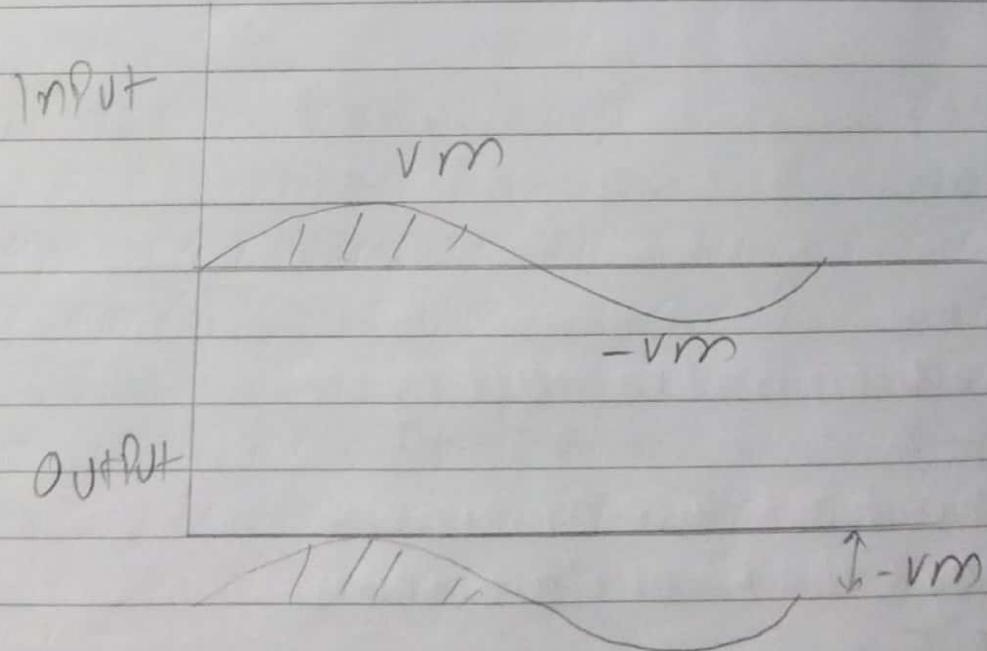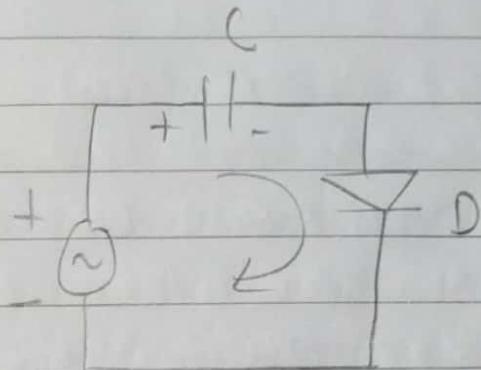- In first +ve half cycle the capacitor will charge through forward Biased diode to peak voltage
- This charging takes very quickly as diode resistance negligibly small.
- Once capacitor charges to V_m diode is reverse biased and stops conducting.



Saathi

Date _____



Q.6

Two children sit side by side. They have different hobbies. One likes to play football and the other likes to play chess. They also like to eat ice cream. They both like to go to the park. They both like to go to the park.

Q2 Difference clipper and clammer

Parameter	clipper	clammer
Components used	Diode, Resistors	Diodes, Capacitor, Resistors
function	TO remove a part of Input waveform	TO add a dc shift to Input waveform
frequency of input	Not important as capacitor not used	The value of C is chosen on basis of Input frequency
Applications	Diode clamp, waveshaping circuits	voltage multipliers

Configuration

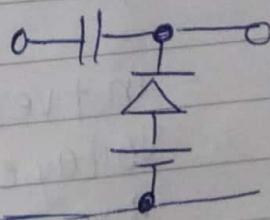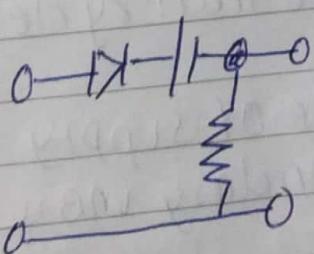


Q.8 Write and explain voltage multipliers

A voltage multiplier is an electrical circuit that converts AC electrical power from lower voltage to higher DC voltage using network of capacitors and diodes.

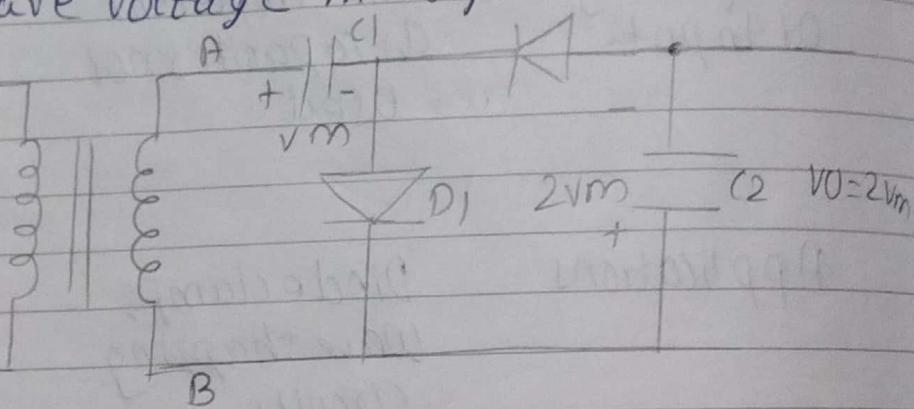
1) Half wave voltage multipliers

A half wave circuit consists of clamps and half wave rectifier. Therefore it is known as half wave voltage multipliers.




→ Operation in the half cycle

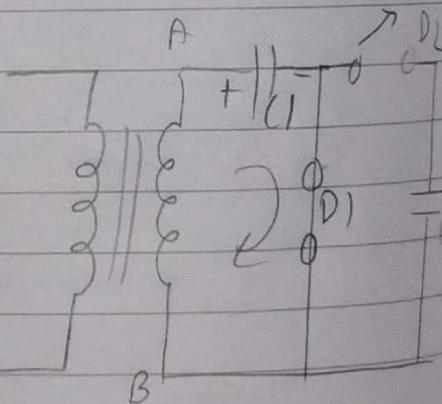- In the half cycle of supply voltage the secondary V_{AB} is +ve
- This will turn ON Diode D_1 and capacitor C_1 will charge through it quickly to peak secondary voltage
- Diode D_2 remains OFF and isolates capacitor C_2 from C_1




→ Operation in -ve half cycle

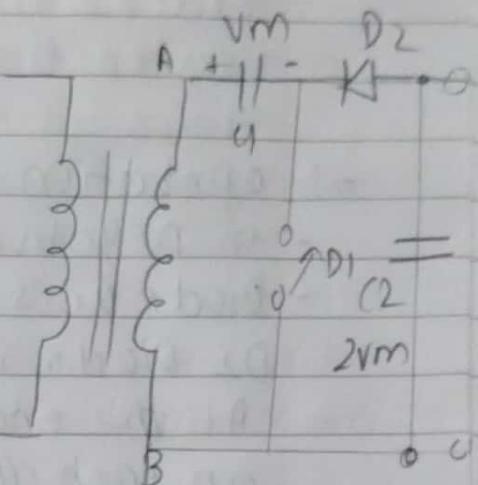- In negative half cycle the secondary voltage V_{AB} is $-v_e$
- This voltage will turn OFF D₁ and turn ON D₂ (capacitor C₂ will acquire voltage of $2v_m$)
- we have assumed v_m is constant during complete -ve half cycle
- In next positive half cycle Diode D₂ is non conducting and capacitor C₂ will discharge load if no load is connected across capacitor C₂ both capacitors will remain charged.



⇒ full wave Doubler

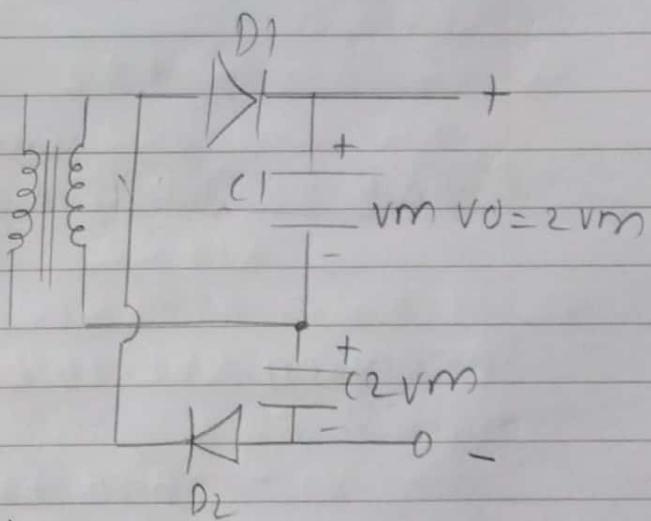


→ Operation in +ve half cycle

- In +ve half cycle V_{AB} is +ve and induced secondary voltage
- This will turn ON D₁ and turn off D₂ as it is reverse bias. The capacitor C₁ charges quickly

\Rightarrow operation in negative half cycle

- in negative half cycle of input secondary voltage v_{AB}
- Diode D_1 is reverse bias and cannot conduct
- D_2 diode is forward bias and charges capacitor C_2
- At the end of -ve half cycle the voltage on each capacitor is v_m .

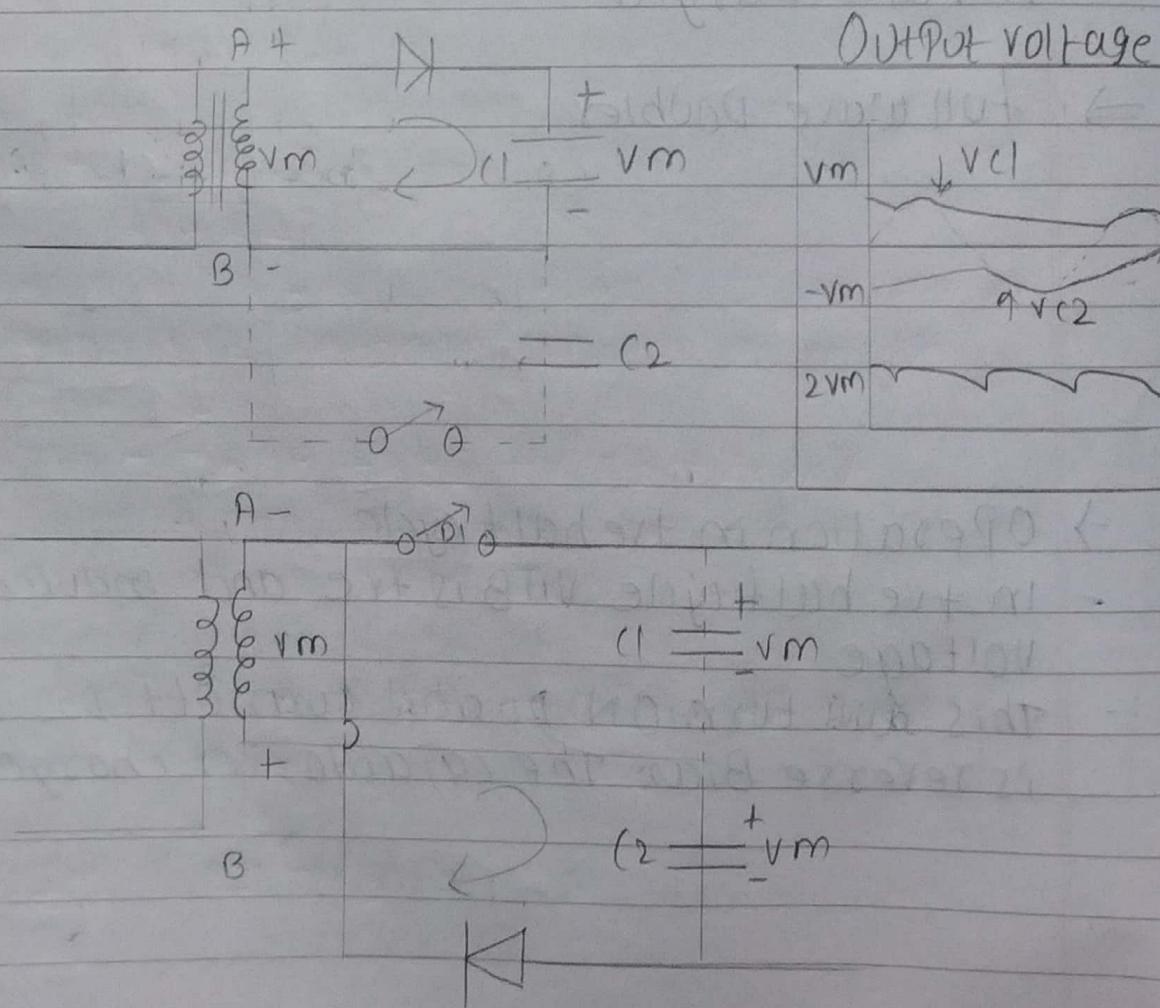Hence output voltage $v_o = v_{C1} + v_{C2}$
 $v_o = 2v_m$





Date _____

Saathi

⇒ Voltage Tripler and Quadriplexer


Operation

- In first +ve half cycle of input, capacitor C_1 is charged to v_m through Diode D_1
- In next negative half cycle, the secondary voltage V_{AB} is -ve which turns Diode D_2 ON. The Capacitor C_2 will charge to $2v_m$
- In next Positive half cycle, the Diode D_3 is ON V_{AB} is +ve. This will charge capacitor C_3 to $2v_m$
- In next negative half cycle, Diode D_4 is ON which will charge capacitor C_4 to $2v_m$

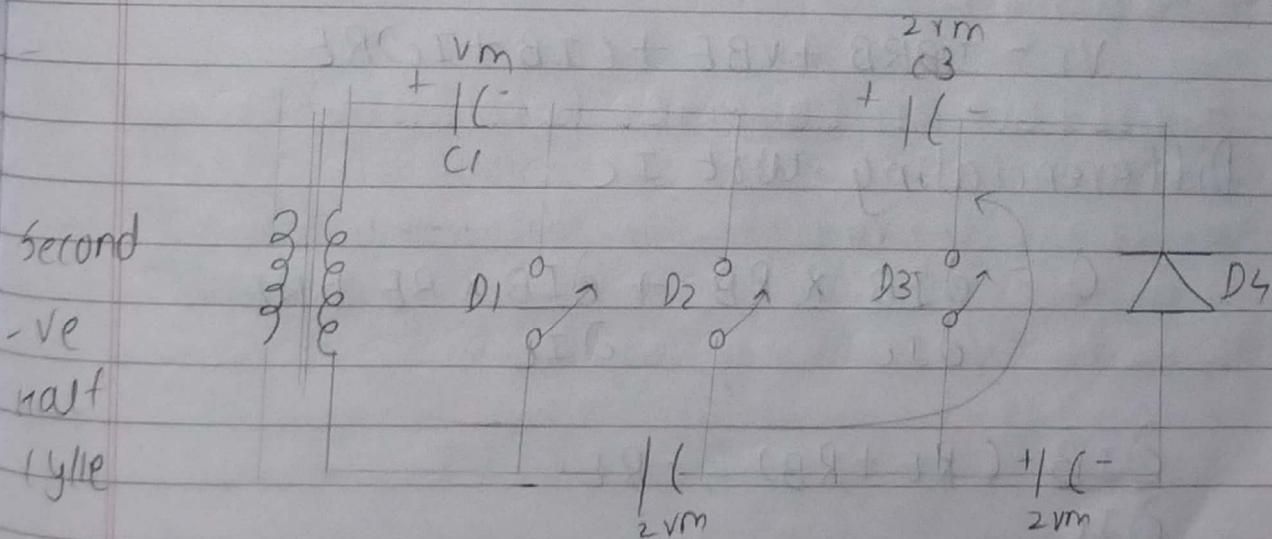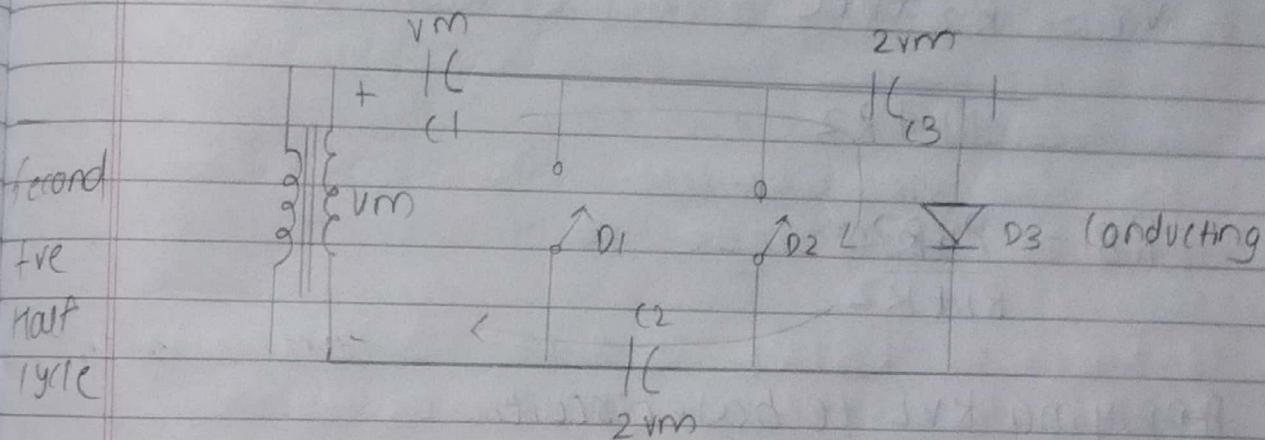

1) Mention essentials of biasing circuit

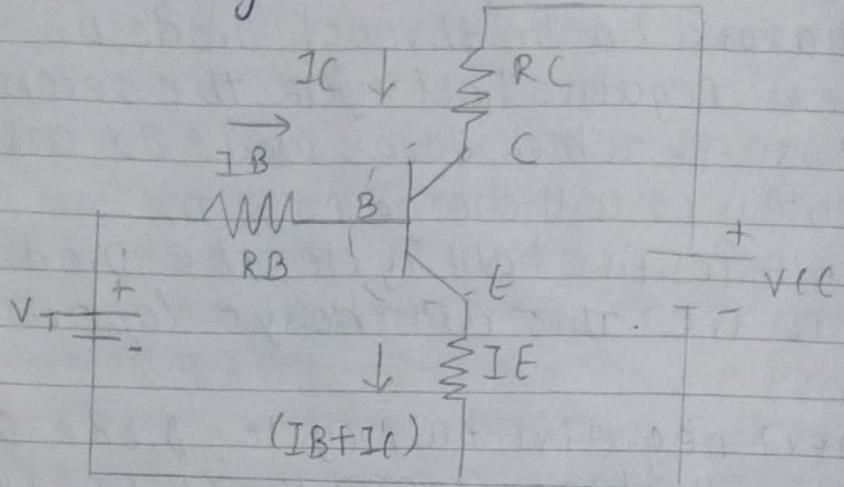4. Describe stability factor for voltage divider Biasing circuit



$$V_T = R_2 \times V_{CC}$$

$$\frac{R_1 + R_2}{R_1 + R_2}$$

$$R_B = \frac{R_1 R_2}{R_1 + R_2}$$

Applying KVL to base circuit

$$V_T = I_B R_B + V_{BE} + (I_B + I_C) R_E$$

Differentiating wrt I_C

$$0 = \frac{\partial I_B}{\partial I_C} \times R_B + \frac{\partial I_B}{\partial I_C} \times R_E + R_E$$

$$\frac{\partial I_B}{\partial I_C} (R_E + R_B) = -R_E$$

$$\frac{\partial I_B}{\partial I_C} = \frac{-RE}{RE+RB} \rightarrow ①$$

$$S = \frac{1+\beta}{1+\beta} \left(\frac{RE}{RE+RB} \right)$$

$$S = (1+\beta)(RE+RB)$$

$$\frac{RB+RE+\beta RE}{RB+(1+\beta)RE}$$

$$= (1+\beta)(RE+RB)$$

$$\frac{RB+(1+\beta)RE}{RB+(1+\beta)RE}$$

Dividing each term by RE

$$S = \frac{(1+\beta) \cdot 1 + RB/RE}{(1+\beta) + RB/RE} \quad (1+\beta \gg RB/RE)$$

$$= -1 + \frac{RB}{RE}$$

→ The ratio of RB/RE controls value of stability factor S

If $RB/RE \ll 1$


$$S = (1+\beta) \cdot \frac{1}{(1+\beta)} = 1$$

$$= 1 + \frac{RB}{RE}$$

$\therefore 1+\beta \gg RB/RE$

- To keep the Ratio of R_B/R_E small, it is necessary to keep R_B small. This means $R_1 || R_2$ must be small. Due to small value of R_1 and R_2 , potential divider circuit will draw more current from V_{CC} . By reducing R_B will reduce input impedance of circuit. This reduction of input impedance in amplifier circuits is not desirable.
- R_E is another parameter we can use to decrease R_B/R_E . By increasing R_E we can make R_B/R_E small. But as we increase R_E drop $I_E R_E$ will also increase and since V_{CC} is constant drop across R_C will reduce.
- S - small
 R_B - Reasonably small
 R_E - NOT very large
- If Ratio of R_B/R_E is fixed, S increases with β . Therefore stability decreases with increasing β

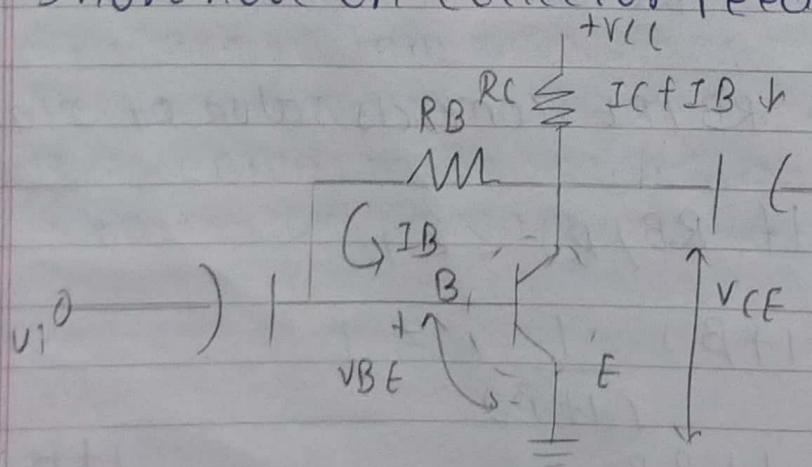5. Short note on collector feedback circuit



- It is improvement in fixed-bias method
- In this biasing resistor is connected between collector and base of transistor to provide feedback path

Applying KVL

$$V_{CC} - (I_B + I_C)R_C - I_B R_B - V_{BE} = 0$$

$$V_{CC} = (R_B + R_C) I_B + I_C R_C + V_{BE}$$

$$= (R_B + R_C) I_B + \beta I_B R_C + V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta R_C}$$

→ Collector circuit

Apply KVL

$$V_{CC} - (I_C + I_B) R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - (I_C + I_B) R_C$$

- If there is change in β and I_{CO} due to change in temperature then collector current I_C tends to increase. As a result, voltage drop across R_C increases since supply voltage V_{CC} is constant due to increase in I_C , R_C , V_{CE} decreases

- In this circuit, R_B appears directly across Input and output. A part of output is fed back to input and increase in collector current decreases the base current. Thus negative feedback exist in circuit so circuit is Voltage feedback bias circuit

Q. How variation in temperature changes location of Q point on DC load line

- The junction temperature of transistor dependent on amount of current flowing through transistor

Due to increase in temperature parameters will change

- 1) V_{BE}
- 2) B_{DC}
- 3) I_{CBO}

1) V_{BE}

- The base to emitter voltage decreases at increase in temperature
- The base current I_B will increase and it will force I_C to change and hence Q point will change position

Date _____

2) change in current gain β_{dc}

- The current gain β_{dc} of transistor is temperature dependent
- As $I_c = \beta_{dc} I_B$, I_B changes in β_{dc} will change collector current I_c . This will change the position of \odot point

3) change in Reverse saturation current I_{cbo}

- The reverse saturation current of reverse biased cB junction flows due to minority carriers hence depend on temperature


$$I_c = \beta_{dc} I_B + (1 + \beta_{dc}) I_{cbo}$$

Therefore change in I_{cbo} due to temperature will force collector current I_c and hence \odot point to change.

Saathi Date _____ Special Purpose Diodes

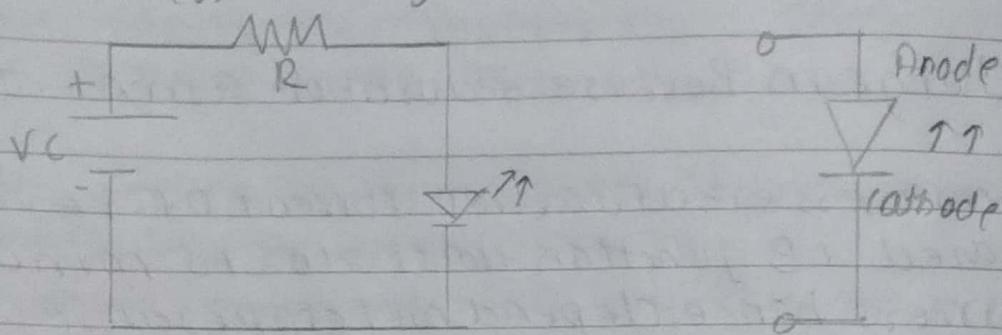
1) Explain LED diode

- An LED emits light when electrical energy is applied to it. It is a two terminal device.
- A PN junction is formed b/w anode and cathode so basically called as PN junction diode. (current limiting Resistor)



- The active region exists b/w p and n region. The light emerges from active side in all directions when electron-hole pairs recombine.
- The disadvantage of this structure is that LED emits light in all directions.
- LED are made of Gallium Arsenide, gallium phosphide. Silicon and germanium are not used because they are essentially heat producing materials and are very poor in producing light.
- When LED is forward biased the electrons in n region will cross junction and recombine with holes in p type.
- When the recombination takes place these electrons return back to valence band which is at lower energy level than conduction band.

- while returning back, the recombining electrons give away excess energy in form of light. This process is called electroluminescence. This is principle for operation of LED
- The colour of emitted light decided by its wavelength
- The wavelength of emitted light depends on forbidden gap and it depends on material used
- Various impurities are added during doping process to get precisely required colour of emitted light.

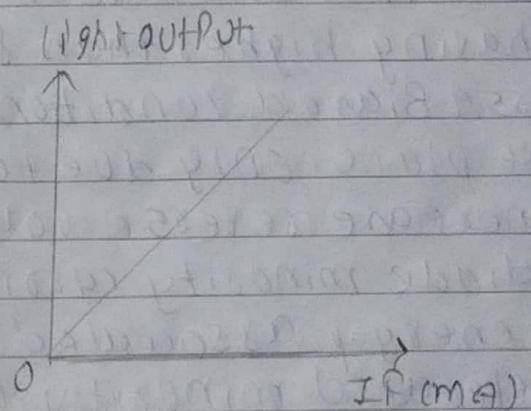

Q) What is zener and avalanche breakdown? Compare b/w them

⇒ Zener Breakdown

- Zener breakdown is observed in zener diodes having V_z less than 5V and $5 \text{ to } 8 \text{ V}$.
- When reverse voltage is applied to zener diode it causes a very intense electric field to appear across narrow depletion region
- This intense electric field is strong enough to pull some of valence electrons into conduction band by breaking their covalent bonds.

- A large no of free electrons will constitute a large reverse current through zener diode and breakdown called zener breakdown
- In zener-breakdown the breakdown voltage depends on temperature of pn junction
Breakdown voltage decreases with increase in junction temperature


⇒ Avalanche Breakdown

- The avalanche breakdown observed in zener diodes having higher than V_Z
- In reverse Biased condition, the conduction will take place only due to minority carriers
As we increase reverse voltage applied to zener diode minority carriers tends to accelerate kinetic energy associated with them increase.
- The accelerated minority carriers will collide with stationary atoms and impart some of kinetic energy to valence electrons present in covalent bonds.
- Due to this additionally acquired energy, these valence electrons will break covalent bond and jump in to conduction band to become free for conduction
- The newly generated free electrons will get accelerated. This will knock out some more valence electrons by means of collision
This phenomenon called as carrier multiplication
- This self sustained multiplication is called Avalanche effect. A large reverse current starts flowing through zener diode and avalanche breakdown occurred

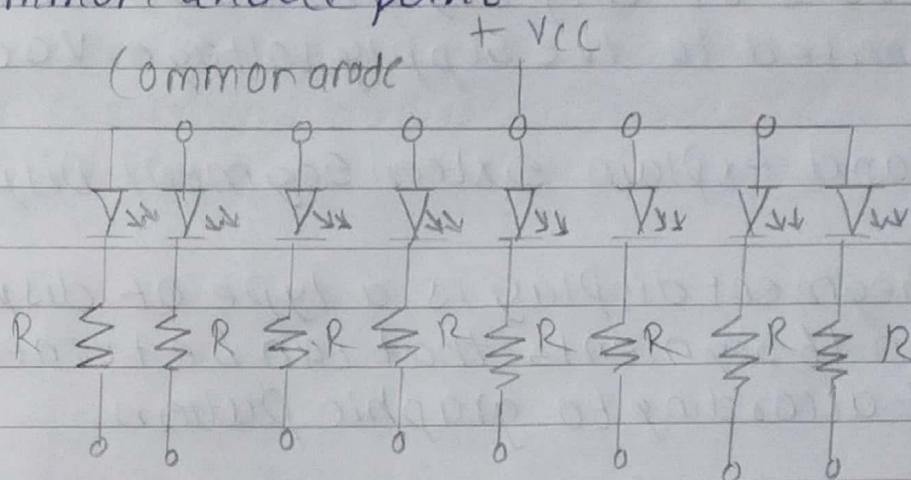4. Draw and explain Seven segment display for common cathode and common anode.


→ Common Anode

- The name suggest the anode terminals of all LED segments are connected together to form common anode point.



- The common anode point connected to V_{CC}.
- A current limiting resistor is externally connected in series with cathode terminal of each segment.
- The cathodes of segments to be turned ON are connected to ground.


→ Common cathode

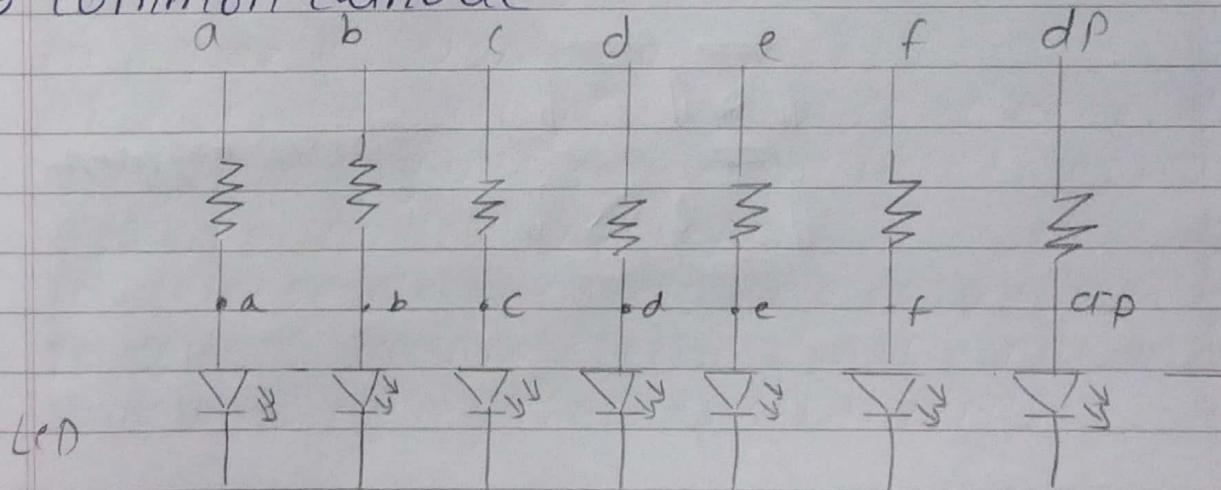

- As name suggest, the cathode terminal is made common to form common cathode point and all anode terminals are brought out separately
- A current limiting resistor is externally connected in series with anode terminal of each segment. The common cathode point is connected to ground and anodes of only segment to be illuminated are connected to the supply voltage V_{CC}

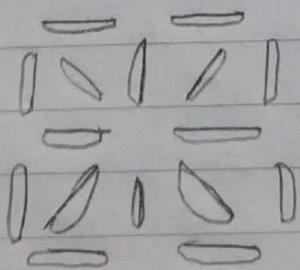5. Draw and explain sixteen Segment Display


- A 16-segment display is a type of display based on 16 segments that can be turned on and off according to graphic pattern
- It is an extension of more common 7 Segment display by adding four diagonal and two vertical segments and by splitting the three horizontal segments into half
- Each of the sixteen segments is an LED in shape of segment




Sixteen Segment

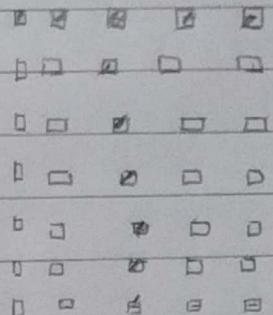6. Draw and explain Dot Matrix LED display

- The dot-matrix displays are used to display numeric and alphanumeric characteristics.
- An LED is connected to each dot and according to number or character to be displayed particular dots are illuminated.
- A 3×5 dot matrix is used for displaying the numeric characters and 5×7 dot matrix used for displaying alphanumeric characters



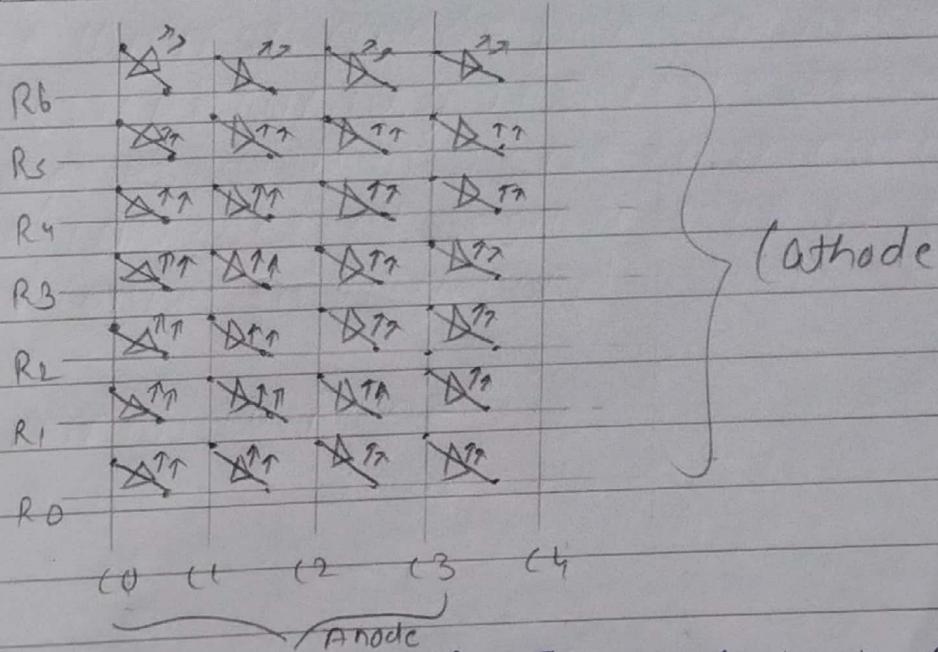- Here 5 columns and 7 rows of LED are arranged



- Due to large no of LED used, it is not practical to use a separate driver for each LED
- Techniques like dynamic displays system can be used to improve brightness of display.

Saath

Date

- In dynamic display systems all required LED are not turned on simultaneously. But they turn on in sequential order fastly.
- Due to sequentially illuminating of LEDs current drawn from DC supply reduces and brightness can be improved.