

Field Effect Transistors (FET) and its biasing

- Q:1 Draw and explain the Fixed bias circuit of FET.
- Q:2 Draw and explain the self bias circuit of FET.
- Q:3 Explain Transconductance and switching in FET.
- Q:4 Explain FET as an Amplifier.
- Q:5 Draw and explain various biasing method in ohmic region.
- Q:6 Draw and explain voltage divider bias of FET.
- Q:7 Write short note on Depletion MOSFET.
- Q:8 What are the advantage of N-Channel MOSFET over P-Channel MOSFET.
- Q:9 Write a short note: E-Type MOSFET.
- Q:10 Comparison of BJT, JFET and MOSFET.

AC Analysis of BJT circuits and small signal

- Q:1 What is use of coupling and bypass capacitor?
- Q:2 Explain the working of Transistor as Switch.

Digital

- Q:1 Among TTL and CMOS digital logic family which one is better and why?
- Q:2 Design and explain NAND gate using DTL logic.
- Q:3 Design and explain NOR gate using DTL logic.
- Q:4 Design and explain basic NAND gate using CMOS logic.
- Q:5 Design and explain basic NOR gate using CMOS logic.
- Q:6 Write short note on Classification of logic families.
- Q:7 Compare TTL, CMOS and ECL