

SILVER OAK COLLEGE OF ENGINEERING & TECHNOLOGY**ADITYA SILVER OAK INSTITUTE OF TECHNOLOGY****BE - SEMESTER-II • MID SEMESTER-I EXAMINATION – SUMMER 2019****SUBJECT: Basic Electronics (3110016) (EE/CE/IT/EC)**

DATE: 14-03-2019

TIME: 12:00 pm to 01:30 pm

TOTAL MARKS: 40

- Instructions:** 1. Q. 1 is compulsory.
2. Figures to the right indicate full marks.
3. Assume suitable data if required.

- Q.1* (a) What is Diode approximation [03]
- (b) Define Peak Inverse Voltage. State PIV of half wave and full wave rectifiers. [03]
- (c) Name the universal gates, Construct all other gates using NAND gates. [04]
- Q.2 (a) Draw and explain unregulated power supply system. [06]
- (b) Draw and explain V-I characteristics of P-N junction diode [05]
- (c) Explain following terms with respect to P-N junction diode [04]
(1) Depletion layer (2) Potential barrier

OR

- Q.2 (a) Describe the rectification and working of bridge rectifier circuit with neat circuit diagram. [06]
- (b) Draw symbol, truth table of all digital logic gates. [05]
- (c) Explain different parameters of Half wave rectifier (1) Ripple factor (2) [04]
Transformer utilization factor (3) Rectification Efficiency (4) I_{rms} V_{rms}
- Q.3 (a) A diode having internal resistance of $20\ \Omega$ is used for half wave rectification. If [06]
the applied voltage $V = 50 \sin(\omega t)$ and load resistance of $800\ \Omega$. Find: (a) I_m ,
 I_{dc} , I_{rms} (b) DC output voltage (c) Efficiency of Rectification.
- (b) Explain different types of Clipping circuits. [05]

- (c) Explain operation of Zener Diode as voltage regulator. [04]

OR

- Q.3 (a) A sinusoidal voltage of peak value of 40 V and frequency 50 Hz is applied at the input of a half wave rectifier, No filter is used. The load resistance is $500\ \Omega$. Diode has $R_f = 5\ \Omega$, $R_r = \infty$. Calculate DC value, rms value of load current, load voltage and rectification efficiency. [06]
- (b) Explain different types of Clamping circuits. [05]
- (c) Compare zener and avalanche breakdown. [04]
-