

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER– I & II (NEW) EXAMINATION – WINTER 2019****Subject Code: 3110005****Date: 11/01/2020****Subject Name: Basic Electrical Engineering****Time: 10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		Marks
<b>Q.1</b>	(a) State Ohm's law and Kirchhoff's Laws in context with DC circuits.	<b>03</b>
	(b) A 100V, 60 Watt bulb is to be operated from a 220V supply. What is the resistance to be connected in series with the bulb to glow normally?	<b>04</b>
	(c) Derive an expression for equivalent resistances of a star connected network to transform into a Delta connected network.	<b>07</b>
<b>Q.2</b>	(a) State Thevenin's and Norton's Theorems.	<b>03</b>
	(b) Compare series and parallel resonance in ac circuit.	<b>04</b>
	(c) A single phase R-L-C circuit having resistance of $8\Omega$ , inductance of 80mH and capacitance of $100\mu\text{F}$ is connected across single phase ac 150 V, 50Hz supply. Calculate the current, power factor and voltage drop across inductance and capacitance.	<b>07</b>
	<b>OR</b>	
	(c) Derive an expression for the voltage across the capacitor during charging through the resistor at any instant $V_C = V(1 - e^{-t/RC})$ . Assume that RC series circuit is connected across a DC supply of voltage V.	<b>07</b>
<b>Q.3</b>	(a) Define the following terms in connection with AC waveforms:- 1. Q-Factor      2. Power Factor 3. Form factor.	<b>03</b>
	(b) Draw impedance triangle, Voltage triangle, Power triangle for single phase R-L series circuit.	<b>04</b>
	(c) Derive the relationship between Phase and Line values of voltages and currents in case of 3-phase Star- connection.	<b>07</b>
	<b>OR</b>	
<b>Q.3</b>	(a) Define the terms:- 1. Real power 2. Reactive power 3. Apparent power.	<b>03</b>
	(b) Derive the EMF equation of single phase transformer.	<b>04</b>
	(c) With neat circuit diagram and a phasor diagram prove that two watt meters are sufficient to measure total power in 3-phase system.	<b>07</b>
<b>Q.4</b>	(a) Explain working principle of single phase Transformer.	<b>03</b>
	(b) Give Merits, Demerits and Applications of Induction Motor.	<b>04</b>
	(c) Explain in detail the construction of an Alternator.	<b>07</b>
	<b>OR</b>	
<b>Q.4</b>	(a) Explain working principle of D.C. Motor.	<b>03</b>
	(b) Compare poly phase Induction Motor and single phase Induction Motor.	<b>04</b>

	(c)	Explain Generation of Rotating Magnetic Field in 3-phase Induction Motor with diagrams and equations.	07
<b>Q.5</b>	(a)	Classify different types of cables with reference to voltage and insulation materials.	03
	(b)	Explain the terms:- 1. Residual magnetism 2. Coercive Force.	04
	(c)	Explain the process of charging and discharging of Lead acid cell.	07
	<b>OR</b>		
<b>Q.5</b>	(a)	Compare MCB and ELCB.	03
	(b)	Write safety precautions for electrical Applications.	04
	(c)	Explain different methods of power factor improvement.	07

\*\*\*\*\*