

**SARDAR VALLABHBHAI PATEL INSTITUTE OF TECHNOLOGY
VASAD**

Digital Fundamental (3130704)

Question Bank

1. Explain why the binary number system is used for most digital systems.
2. Convert the following decimal numbers to binary, octal and hexadecimal:
 - a. 584
 - b. 119.84
 - c. 33.45
3. Convert the following numbers from the given base to the other three bases indicated.
 - a. $(11101.1101)_2 = (_\? _\?)_{10} = (_\? _\?)_8 = (_\? _\?)_{16}$
 - b. $(10001.0001)_2 = (_\? _\?)_{10} = (_\? _\?)_8 = (_\? _\?)_{16}$
 - c. $(623.77)_8 = (_\? _\?)_{10} = (_\? _\?)_2 = (_\? _\?)_{16}$
 - d. $(367.52)_8 = (_\? _\?)_{10} = (_\? _\?)_2 = (_\? _\?)_{16}$
 - e. $(8E47.AB)_{16} = (_\? _\?)_{10} = (_\? _\?)_2 = (_\? _\?)_8$
 - f. $(2AC5.D)_{16} = (_\? _\?)_{10} = (_\? _\?)_2 = (_\? _\?)_8$
4. Convert 128.286 to binary, octal and hexadecimal with an accuracy of 0.001_{10} .
5. Determine the value of base x if $(211)_x = (152)_8$.
6. Find the 9's and 10's complement of the following decimal numbers: 123900, 00980100, 100000, 00000000.
7. Find the 1's and 2's complement of the following binary numbers: 10101110, 0111000, 10000000, 00000000.
8. Convert the following decimal numbers to BCD, Binary-coded octal and binary-coded hex.
 - a. 748
 - b. 29.8125
9. Differentiate between positive and negative logic system.
10. What is Boolean algebra?
11. State and prove De-Morgan's theorem.
12. Define the following:
 - a) Minterm b) Maxterm
13. Differentiate between Canonical form and Standard form. Which form is preferable when implementing a Boolean function with gate? Why?
14. Reduce the expression to simplest terms:
 - a) $F = A' + AB' + BC$
 - b) $F = (A + B' + C') \cdot (A' + B + C) \cdot BC$
 - c) $F = ((AB' + ABC)' + A(B + AB'))'$
15. Prove the following.
 - a) $AB + ABC + AB' = A$

- b) $BCD + AC'D' + ABD = BCD + AC'D' + ABC'$
 - c) $AB + BC + A'C + A'B'C = ABC' + AB + A'C$
 - d) $AB + A'C + BC = AB + A'C$
 - e) $A + B[AC + (B + C')D] = A + BD$
 - f) $AB + CD + A'C' = A' + B + C' + D$
16. If $AB' + A'B = C$ then show that $AC' + A'C = B$
17. Write the expression for F if F is equal to 1 when any of the minterm m_0 , m_3 , m_4 or m_6 is present. Assume A is the MSB.
18. Explain the boolean function in SOP & POS form.
- a) $F = A + B'C$
 - b) $Y = AB + ACD$
 - c) $F = (A' + B).(B' + C)$
 - d) $F = (XY + Z).(Y + XZ)$
19. Plot the K-map for following function:
- a) $F = (A' + B').(C' + D').(B' + D)$
 - b) $F = (AB + CD').(AC' + BD)$
 - c) $F = A'B'C'D + A'BC'D + A'B'CD + ABCD' + ABC'D$
20. Build a minimal hardware system to realize a function F that equals 1 when a 4-bit input code equals 1, 2, 5, 6, 8, 11, 12 and 14. F should be 0 for input 4, 7, 9, and 10. Remaining will never occur.
21. Realize using only NAND Gate only:
- a) $F = AB + CD + E$
 - b) $F = BD + BCD + AB'C'D' + A'B'CD'$
 - c) $F = (AB + A'B')(CD' + C'D)$
22. Realize using only NOR Gate only:
- a) $F = (A + B).(C + D).E$
 - b) $F = X'Y + XY' + Z$
 - c) $F = AB'CD' + A'BCD' + AB'C'D + A'BC'D$
23. What is a digital computer and explain its block diagram with figure.
24. Convert Decimal Number 250.5 to base 3, base 4, base 7, base 16 and base 8
25. Convert Decimal Number 255.225 to binary, octal and hexadecimal
26. Convert the following Number as directed
- a) 52 base 10 = () base 2
 - b) 101001011 base 2 = () base 10
 - c) 11101110 base 2 = () base 8
 - d) 68 base 10 = () base 16
27. Convert following hexadecimal number to decimal : B28, FFF, F28
28. Convert following octal to hexadecimal and binary : 414, 574, 725.25
29. Convert the following number to decimal
- a) 10001.101
 - b) 101011.11101

- c) $(0.365)_8$
- d) A3E5
- e) CDA4
- f) 11101.001
- g) B2D4

30. Write first 10 decimal numbers in base 11, base 7 and base 12 number system.

31. Perform subtraction with following binary number using 1's complement and 2's complement

- a) $11010-1101$
- b) $10010-10011$
- c) $100-110000$
- d) $11010-10000$

32. Explain comparison between 1's and 2's complements with appropriate example

33. Explain different types of binary codes in detail.

34. Simplify the following Boolean function to a minimum no of literal.

- (a) $ABC+A'BC+A'B'C+ABC'+A'B'C'$ (to five literals)
- (b) $xy'+y'z'+x'z'$
- (c) $(A'+C)(A'+C')(A+B+C'D)$
- (d) $(x'y'+z)'+z+xy+wz$
- (e) $(A+C+D)(A+C+D')(A+C'+D)(A+B')$ (to four literals)
- (f) $A'B(D'+C'D)+B(A+A'CD)$
- (g) $BC+AC'+AB+BCD$ (to four literals)
- (h) $[(CD)'+A]'+A+CD+AB$ (to three literals)

35. Implement the Boolean functions.(a) $xyz+x'y+xyz'$ (b) $(A+B)'(A'+B')'$ and $F=xy+xy'+y'z$ with logic gates.

36. Obtain the simplified expression in sum of product for the following Boolean functions.

- (a) $F = \Sigma(0,1,4,5,10,11,12,14)$ and (b) $F = \Sigma(11,12,13,14,15)$.

37. Implement the functions $F = \Sigma(1,3,7,11,15)$ with don't care conditions $d = \Sigma(0,2,5)$
Discuss the effect of don't care conditions

38. Find the complement of the following Boolean function and reduce to a minimum number of literals.

$$B'D + A'BC' + ACD + A'BC$$

39. Obtain the simplified expressions in sum of products using K-map:

$$x'z + w'xy' + w(x'y + xy')$$

40. Given Boolean function

$$F = xy + x'y' + y'z$$

- 1. Implement it with only OR & NOT gates
- 2. Implement it with only AND & NOT gates

41. Simplify the following Boolean function using K-Map.

$$F = A'B'C' + B'CD' + A'BCD' + AB'C'$$

42. Simplify the following Boolean function by using K-Map.

$$F = \Sigma (0,1,2,8,10,11,14,15)$$

43. Simplify Boolean function $F(w,x,y,z) = \Sigma (0,1,2,4,5,6,8,9,12,13,14)$ using K-map and Implement it using (i) NAND gates only (ii) NOR gates only.

44. Simplify the following Boolean function using K-Map and draw logic diagram using NOR gates only.

$$F(w,x,y,z) = \Sigma (0,1,2,8,10,11,14,15)$$

45. Simplify the Boolean function:

$$(1) F(w,x,y,z) = \Sigma (0,1,2,4,5,6,8,9,12,13,14)$$

$$(2) F(w,x,y) = \Sigma (0,1,3,4,5,7)$$

46. Explain with figures how NAND gate and NOR gate can be used as Universal gate.

47. Simplify the Boolean function:

$$(1) F = A'B'C' + B'CD' + A'BCD' + AB'C'$$

$$(2) F = A'B'D' + A'CD + A'BC$$

$$d = A'BC'D + ACD + AB'D' \text{ Where "d" indicates Don't care conditions.}$$

48. Obtain the simplified expressions in sum of products for the following Boolean functions:

$$F(A,B,C,D,E) = \Sigma (0,1,4,5,16,17,21,25,29)$$

49. Simplify the Boolean functions using K-map

$$F(A,B,C,D,E,F) = \Sigma (6,9,13,18,19,25,27,29,41,45,57,61).$$

$$F(A,B,C,D,E,F,G) = \Sigma (20,28,52,60)$$

50. Implement the following Boolean functions using don't care conditions.

$$F(A,B,C,D) = \Sigma (0,1,2,9,11) \quad d(A,B,C,D) = \Sigma (8,10,14,15)$$

$$F = B'D + B'C + ABCD \quad d = A'BD + AB'C'D'$$