

# CHAPTER-1 (BASIC ELECTRONICS)

(By Amit A. Patel)

## DIODE THEORY & APPLICATIONS

\* Linear device: graph of current & voltage is a straight line then device is linear device. Simple resistor is a linear device. I ✓

\* Non-linear device: Graph of current & voltage is not a straight line, then device is nonlinear device. Diode is nonlinear device. I ✓

### Intrinsic Semiconductor:


It is a pure semiconductor. A silicon crystal is an intrinsic semiconductor if every atom in the crystal is a silicon.

### Extrinsic Semiconductor:

If semiconductor is doped with impurities to have excess of free electrons or holes is called extrinsic semiconductor

→ n-type Semiconductor: If silicon is doped with penta valent impurities is called n-type semiconductor, where n- stands for negative. Here there are number of free electrons ie. majority charge carriers. and less amount of holes are called minority charge carriers.

n-type

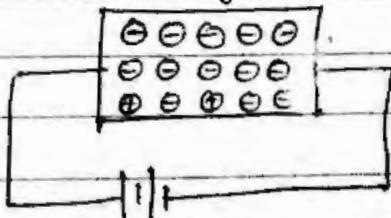


→ p-type Semiconductor:

Silicon has been doped with trivalent impurity is called p-type semiconductor. Holes are more in number, so majority charge carrier & electrons are minority charge carriers.
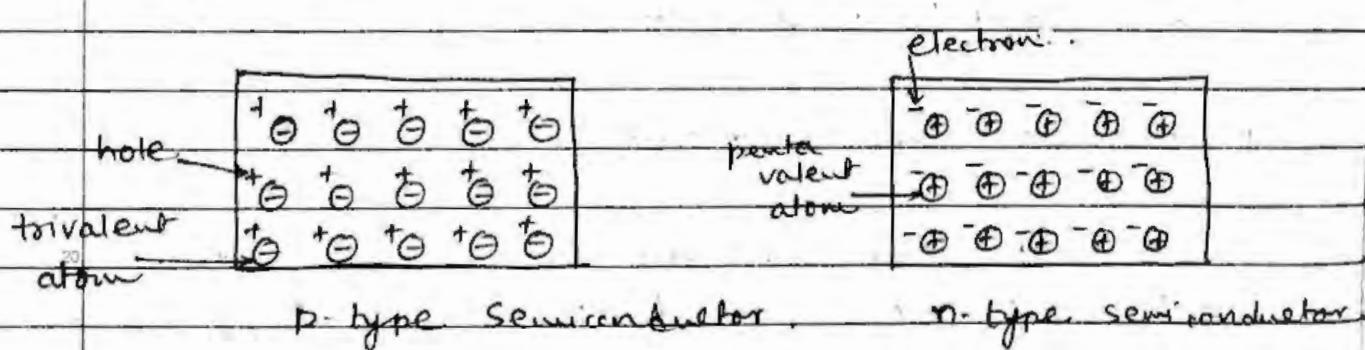
### UNBIASED DIODE


10 A p-type semiconductor & n-type semiconductor are joined together with the help of special fabrication technique to form a p-n junction.

→ piece of p-type semiconductor has trivalent impurities, so it has hole in its valence orbit.




→ piece of n-type semiconductor has pentavalent impurities, so it has electron in its valence orbit. electrons as majority charge carriers.

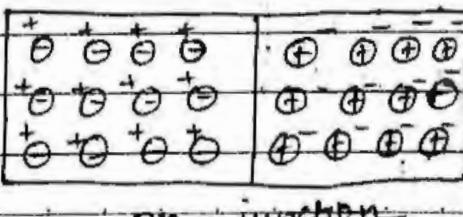→ When p-type & n-type material joined it forms p-n junction. This semiconductor device is called diode.



- Free electrons on n-side has repulsion for each other, so they tend to spread in all directions. Some of free electrons diffuse (spread) across the junction. When free electrons enter the p-region (electrons are minority charge carrier in p-region), it recombines with a hole.
- When electron diffuse across junction, it creates a pair of ions. On n-side near junction large number of positive ions generated (As electron leaves n-side, pentavalent atom becomes positive ion).
- On p-side, electron recombines with holes of trivalent atoms, it generates negative ions near junction.
- This is shown in the figure below:

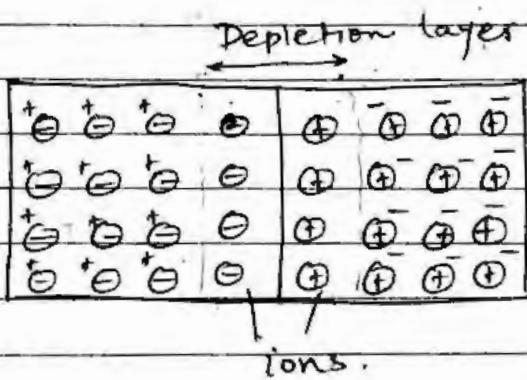

### Depletion layer: (Depletion Region):

- Region on both the side of junction, which contains only immobile ions & no free carriers (electrons or holes) is called depletion region.
- Depletion Region is also known as "space charge Region".


Due to depletion region electrons or holes can not diffuse (spread) to the other side. So, depletion region acts as barrier.

- width of depletion region is very small, of the order of 0.5 to 1  $\mu\text{m}$ .
- electric field generated near junction by positive & negative ions.
- electric field between the ions is equivalent to a difference of potential called barrier potential.
- At  $25^\circ\text{C}$ , the barrier potential equals to approximately 0.3 V for Ge (germanium) & 0.7 V for Si (Silicon).

Q. 1 Give basic idea about forward bias and reverse bias of p-n junction diode.

Q. Biasing of a p-n junction diode. (5 or 7 marks)

A. p-n junction diode :

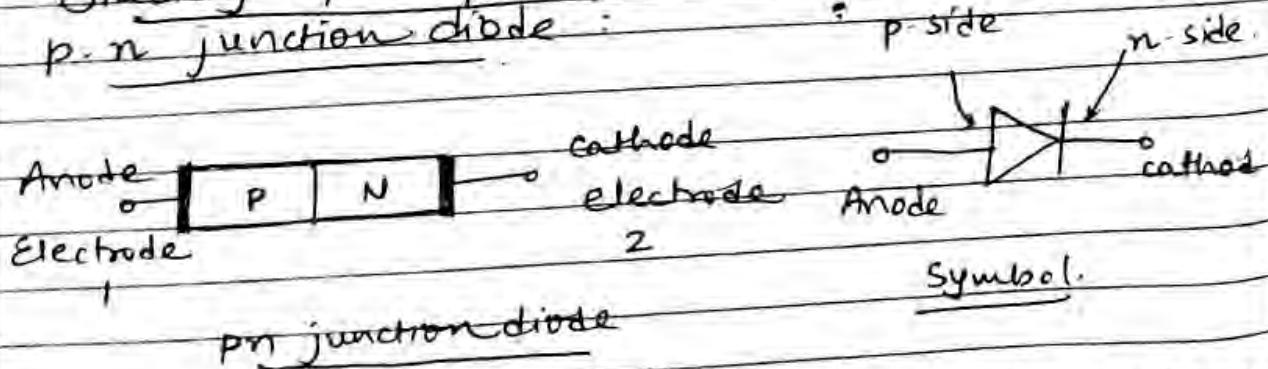


- When p-n junction is formed, depletion region gets created and movement of electron & holes through junction stops.
- Thus current flowing to unbiased (not connected to power supply) p-n junction is zero.
- To make current to flow we have to bias (Give external supply) the p-n junction diode.
- Biasing is the process of applying d.c. supply (voltage) to semiconductor diode.

- When no external voltage applied, diode will remain in the state of equilibrium. So, no current flowing through it.
- Biasing can be of two types:


1) Forward Bias.    2) Reverse Bias.
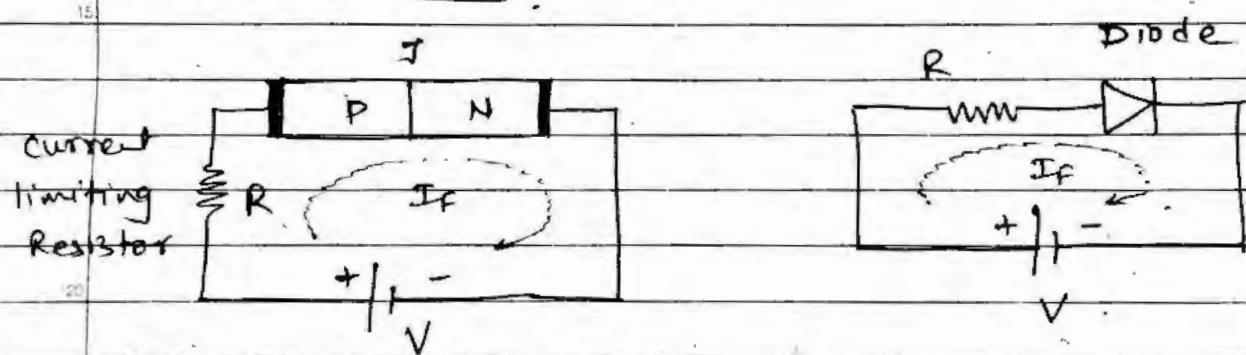
### 1) FORWARD BIAS.

- If the p-side (Anode) connected to the positive terminal of the external DC supply & n-side (Cathode) is connected to negative terminal of DC supply then biasing is said to be "forward biasing".




- When battery is connected to diode, it pushes electrons & holes towards junction.
- If battery voltage is less than barrier potential depletion layer will not allow them to pass through it & junction.
- But if battery voltage is greater than barrier potential, electrons will pass through junction & recombines with holes.
- Large number of majority charge carriers crossing the junction constitute a current called a forward current.

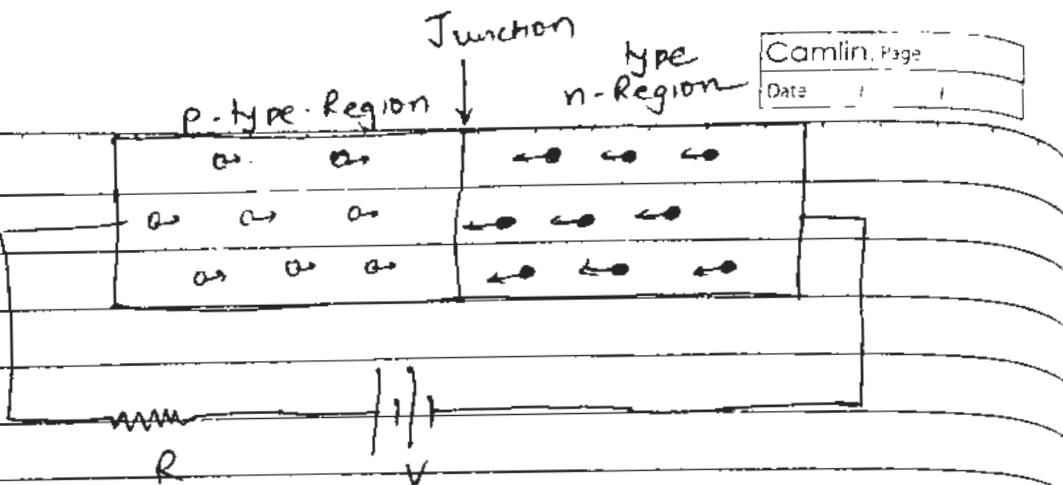

- electrons from n side will move towards the positive end of battery & holes will move towards junction.
- movement of carriers will cause current & that is due to majority charge carriers (Electrons in n-type region & holes in p-type region)
- Forward current of diode is due to majority carriers.
- Due to large forward current ( $I_F$ ), forward resistance of diode is very small.

Voltage drop across forward biased Diode ( $V_F$ )

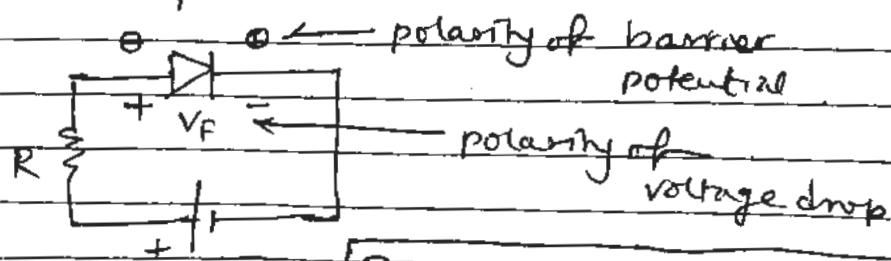- There is a potential drop across conducting forward bias diode to overcome barrier potential, which has opposite polarities to barrier potential & has value equal to barrier potential.




$$\boxed{\text{Barrier potential} = \text{Knee voltage}}$$

Knee Voltage: In forward region, the voltage at which the current starts to increase rapidly is called the knee voltage.
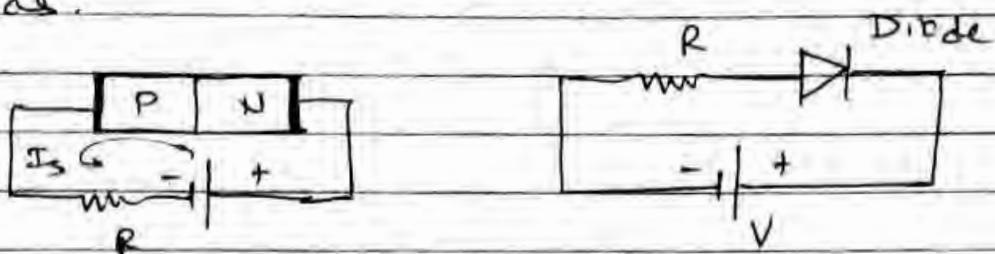
## 2) REVERSE BIAS:


If p-region of diode is connected to the negative terminal of the external DC supply & n-region is connected to the positive terminal of DC supply then diode is said to be reverse biased.



Diode is

→ When reverse biased holes in p-region attracted to +ve terminal of battery & electrons in n-type region attracted towards +ve terminal of battery, so majority carriers of both regions try to move away from junction. This will widen the depletion region.

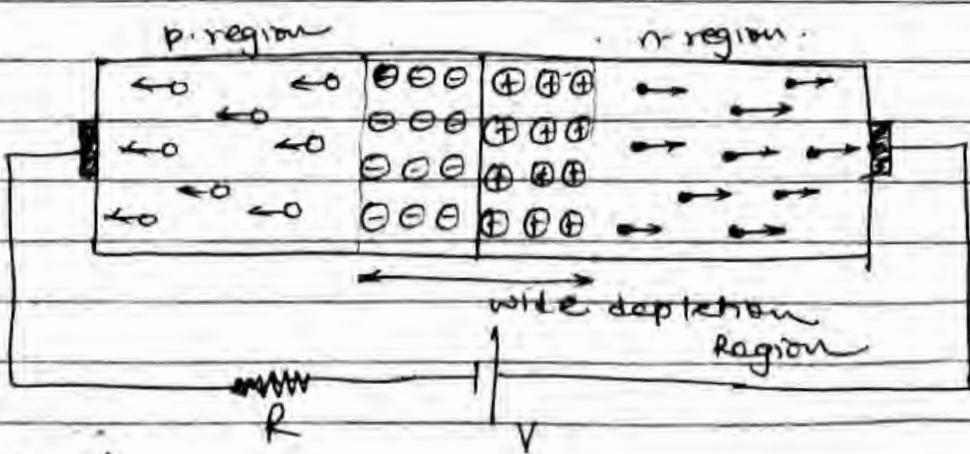→ As carriers try to move away from junction more number of ions present near junction on both the side (no carriers near junction), so barrier potential will increase.



- \* Minority carrier current (Reverse Saturation current)
- p-region consists of a small number of electrons & n-region contains a small number of holes. These are minority carriers generated thermally.
- Minority electrons in p-region are attracted by positive end of the dc supply. These electrons will cross the junction & constitute the reverse current  $I_s$  of the diode.
- Reverse current is also called Reverse saturation current.
- These current is due to the minority carriers. for Ge it is of the order of  $\mu A$  & for Si it is in nano ampere range.
- Reverse saturation current increase with temperature increase.


Q. Write short Note on: V-I characteristics of P-N Junction diode: (JAN.'19, 7 marks).

A. VI characteristics of p-n junction diode is graph of voltage across the diode versus the current flowing through it.


→ VI characteristics can be divided into two parts:

1. Forward Characteristics
2. Reverse Characteristics

Forward Characteristics:

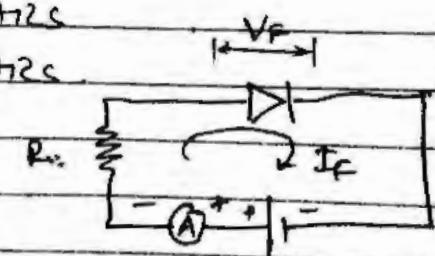

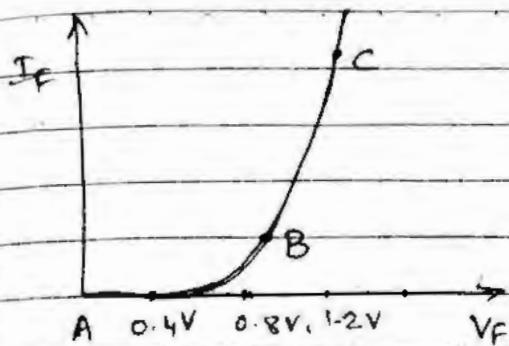→ Forward characteristics is shown in the fig.



→ Current flowing through diode is approximately 0 until the diode voltage approaches the barrier potential.

$V_f$  = voltage across forwards bias diode

$I_f$  = current flowing through diode.


→ When diode voltage is greater than 0.7V diode current is significant & then graph is almost linear.

→ When diode voltage reaches 0.6 to 0.7V, diode current increases.

### 15 Cut-in Voltage (Knee voltage):

The voltage at which the forward diode current starts increasing rapidly is known as the cut-in (knee) voltage.


### 20 Reverse Characteristics:

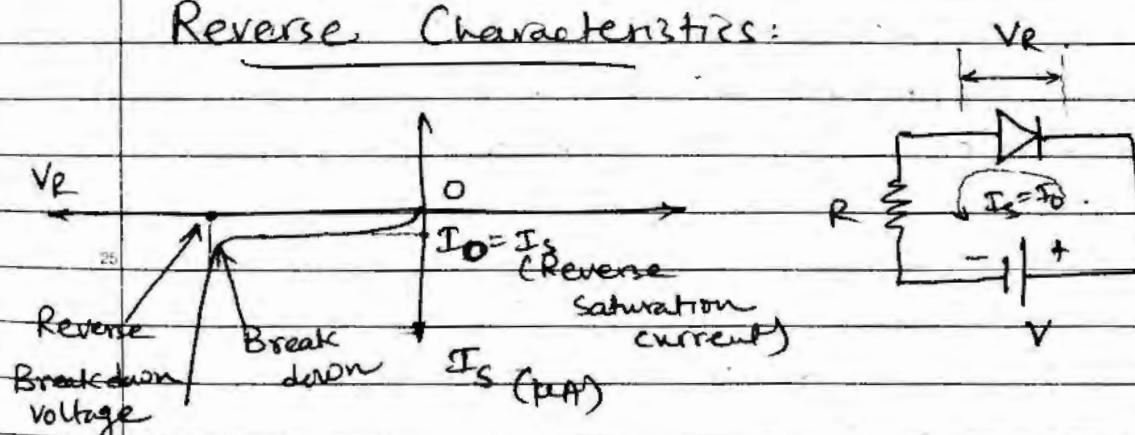

→ Current flowing through a diode in the reverse biased state is the reverse saturation current which flows due to minority carriers.


- As reverse voltage is increased, reverse saturation current remains constant equal to  $I_0$  if the temperature is constant.
- As reverse voltage reaches breakdown voltage value, large current flows through diode and diode may get damaged.

Complete V-I characteristic.

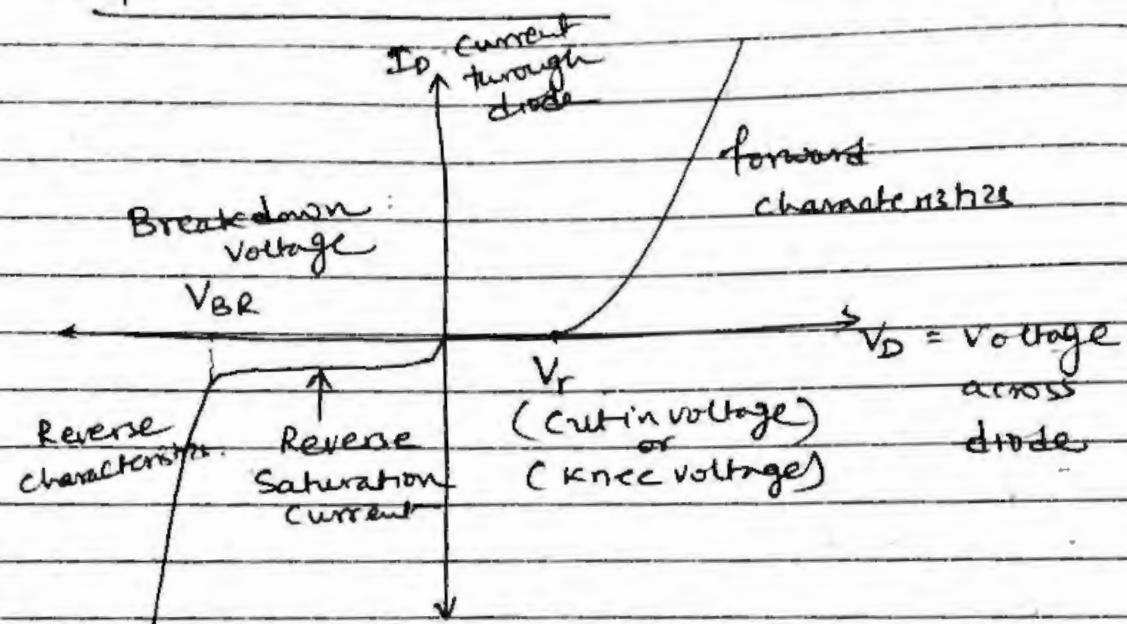

- Q. Write short note on ideal diode.  
(ideal approximation of diode) (3 or 4 marks)
- Ideal diode is the simplest approximation of diode.
  - "What does a diode do?" It conducts well in the forward direction and poorly in the reverse direction.
  - Ideally diode acts like a perfect conductor (zero resistance) when forward biased and perfect insulator in reverse biased condition.

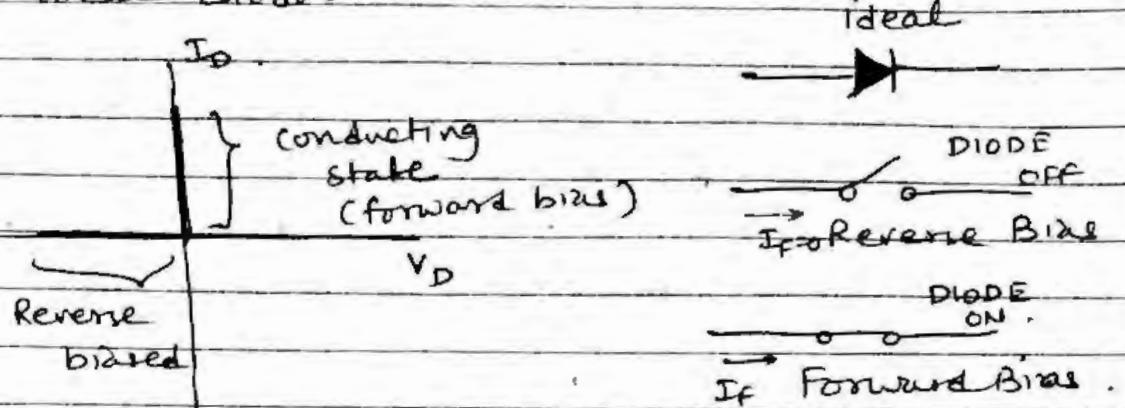Below figure shows the current-voltage graph of an ideal diode.



- When diode is in forward biased condition it acts as closed switch with zero resistance.
- When diode is in Reverse Bias condition it acts as open switch with infinite resistance.
- So ideal diode behave as switch.

15

Q. Define following terms: (1-mark each)

1) Reverse Saturation current: Current flowing through diode in reverse biased state due to minority carriers is called reverse saturation current.

Reverse saturation current for Ge is few  $\mu\text{A}$   
" " " " " Si is few nA.

2) Surface Leakage Current: It is a reverse current at the surface of the crystal. Surface leakage current is directly proportional to the reverse voltage.


Surface leakage current is due to surface impurities & imperfections in the crystal structure.

3) Cut-in voltage (knee voltage): When diode is forward biased, voltage across diode at which current starts flowing through diode is called cut-in voltage or knee voltage.

4) Bulk Resistance: When diode is in forward biased condition, above cut in (knee) voltage current starts rapidly. Above knee voltage, all that impedes current is ohmic resistance of the p & n regions.

Sum of ohmic resistance of p-type & n-type material is called bulk resistance.

$$R_B = R_p + R_N$$

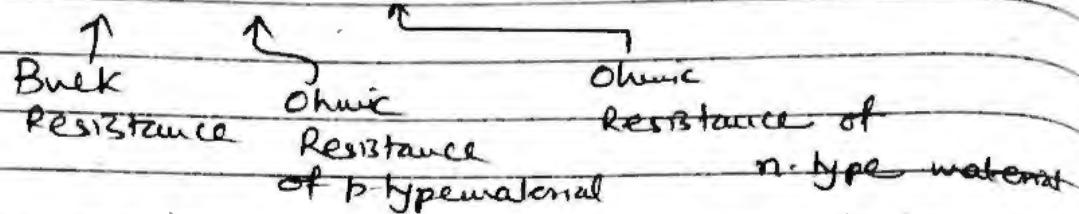

5) Barrier Potential:

When diode is unbiased, due to presence of immobile positive & negative ions on both side of junction an electric field is created across junction. This electric field is known as barrier potential.


Q. Write short note on second & third approximation of diode. (5 or 7 marks)

#### SECOND APPROXIMATION.

A ideal diode approximation is used for trouble shooting applications. But for some other applications we need more accurate equivalent circuit.

→ Graph of current versus voltage for second approximation is shown in fig.

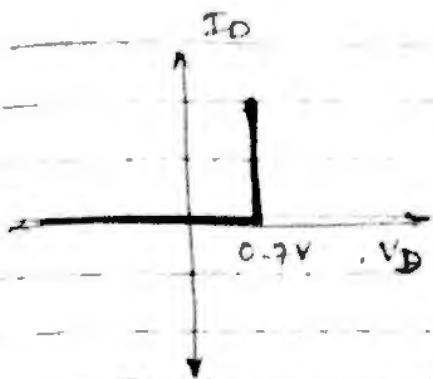→ Graph says no current exists until 0.7V appears across diode.



2<sup>nd</sup> approximation



0.7V

Perverse bias ( $V_D < 0.7V$ )


Diode curve for

second approximation. Forward Bias ( $V_D > 0.7V$ )


- Here in 2<sup>nd</sup> approximation we consider diode as a switch in series with a barrier potential of 0.7V.
- if diode voltage  $V_D > 0.7$  it acts as closed switch.
- if diode voltage  $V_D < 0.7$  " " " open "
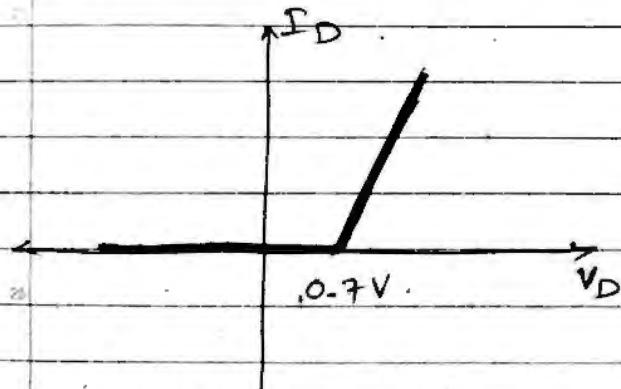
### THIRD APPROXIMATION

- In third approximation of a diode, we include the bulk resistance  $R_B$ .
- V-I characteristics of diode considering third approximation is shown bel.



3<sup>rd</sup> approximation  
diode

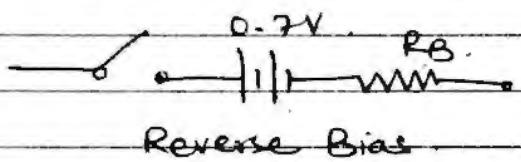

0.7V

$R_B$

Reverse Bias

0.7V

$R_B$

Forward Bias

Diode curve for  
third approximation

- After diode turn on, voltage increase linearly with an increase in current.
- equivalent circuit for the third approximation is a switch in series with barrier potential

0.7V & bulk resistance  $R_B$ .

- When diode voltage is greater than 0.7V diode conducts & voltage across diode is

$$V_D = 0.7V + I_D R_B$$

- often bulk resistance is of the order of 1Ω.


### Diode Approximations Summary.

	First or Ideal	Second or Practical	Third
When used	trouble shooting or quick analysis	Analysis at technician level.	High level or Engineering level
Diode Curve			
Equivalent Circuit	Reverse Bias: Forward bias:	Reverse Bias: Forward bias:	Reverse Bias: Forward bias:
Circuit Example			

Q. Write short note on Surface mount diodes.

- Surface mounted (SM) diodes can be used in almost all the applications of diodes.
- surface mount diodes have following advantages over conventional diode.
  - They are small
  - They are efficient
  - They are easy to test, remove & replace on circuit board.
- Two most popular package types are.
  - 1) SM (Surface Mount)
  - 2) SOT (small outline transistor)

### D) SM Package:

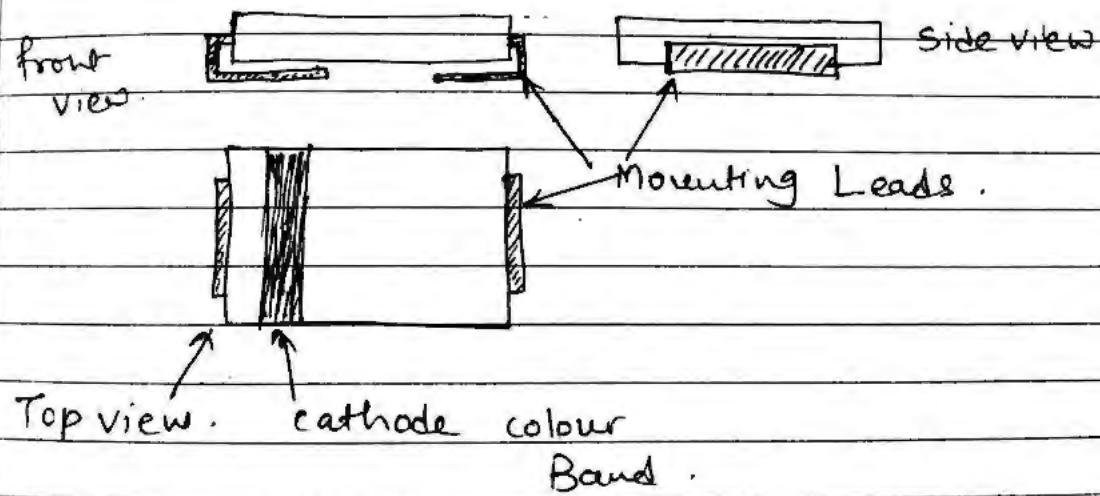


→ above figure shows SM style package for SM diode. It has two L-bend leads & a coloured band on one end of body to identify the cathode terminal.

→ dimension of SM diodes depends on current ratings.

→ as surface area of diode increase, their current goes on increasing.

→ with increase in the surface area of SM package, ability to dissipate heat also increases.

## 2) SOT Package:

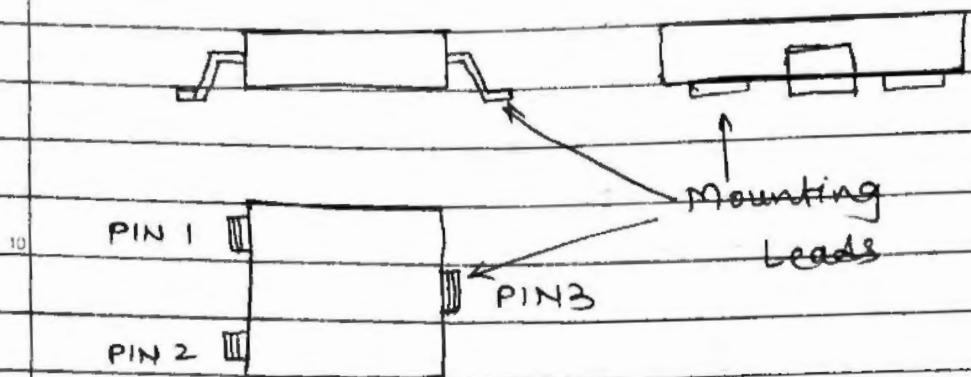


SOT-23 style package for SM diodes.

- SOT-23 package has three gull-wing terminals.
- PIN numbers are shown in fig. (It is three terminal packages)
- There is no marking for anode & cathode, to identify, we need to refer manufacturer's datasheet (datasheet).
- Some SOT-style package includes two diodes, which have common cathod or common anode.
- Diodes in SOT-23 packages are small, no dimension being greater than 0.1 inch.
- It's small size makes it difficult to dissipate large amount of heat, so diodes are rated at less than 1A.

Q. Write short Note on Testing of diode with multimeter.

- We know that Forward resistance of a pn junction diode is small as compared to its reverse bias resistance.

- We use this principle in testing diode using multimeter.
- Step for testing diode using a multimeter is as follows.
  - 1) Put multimeter on the resistance range.
  - 2) Select highest range.
  - 3) Connect the positive (Red) probe of multimeter to one end of the diode & negative probe to the other end of the diode. Measure Resistance.
  - 4) Now interchange the probes & measure the resistance again.
  - 5) By following above step 3 & 4, we are forward biasing & reverse biasing the diode, so once resistance should be low & after interchanging resistance should be high.
  - 6) If diode is faulty then in both step 3 & 4, resistance would be low.
  - 7) Same procedure can be used for identification of diode terminals.

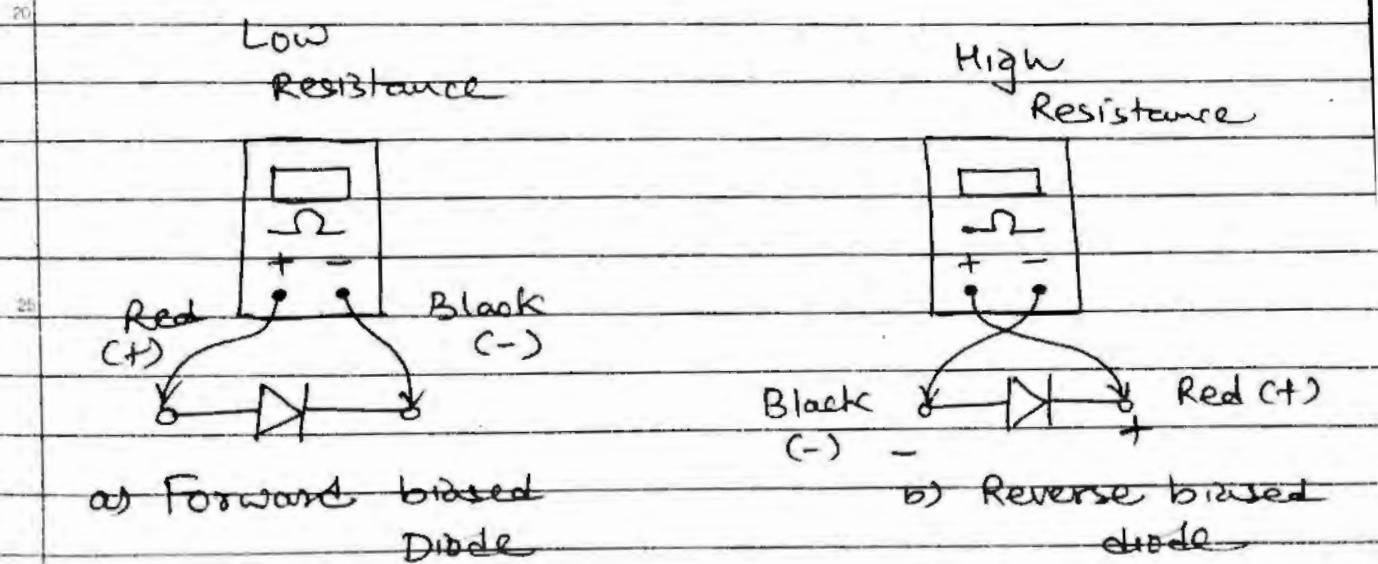


## \* Rectification:

→ Rectification is the process of converting the alternating voltage or current into corresponding direct (Dc) quantity. (Direct voltage or current)

## \* Rectifiers:

→ Rectifier is an electronic device which is used for converting an alternating (Ac) voltage or current into a unidirectional (Dc) voltage or current.

Block Diagram for Rectifier:

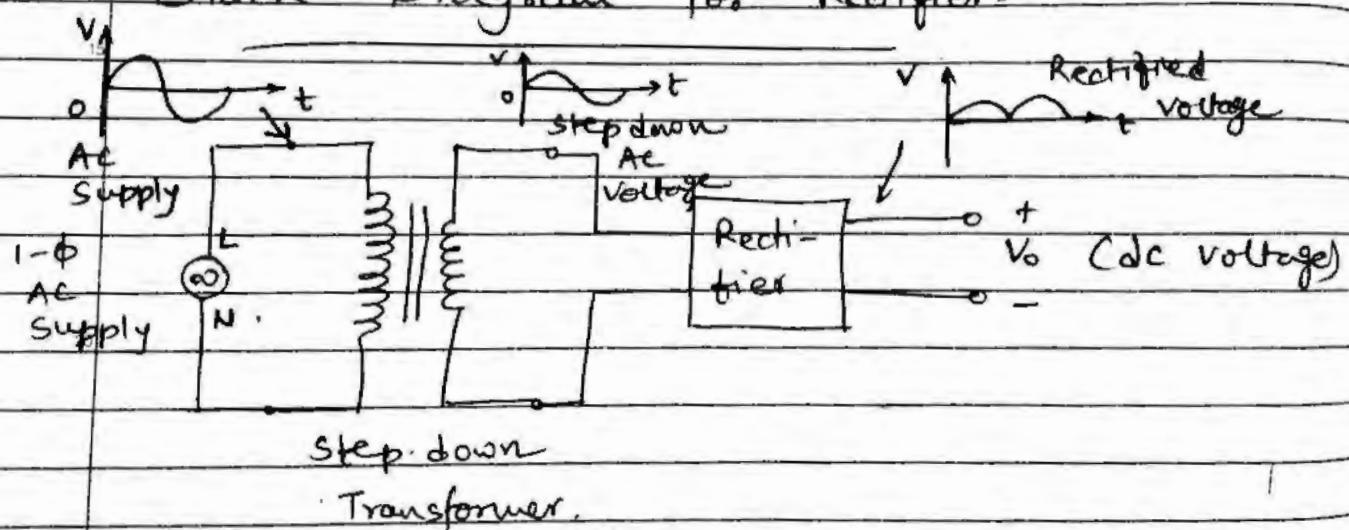


- Step down transformer is used to reduce the ac mains voltage to adequately small value.
- This voltage is converted into a pulsating dc voltage by the rectifier.
- Types of Rectifiers used are half wave rectifier, full wave rectifier or Bridge rectifier.
- Every Electronic circuit such as amplifiers, needs

a dc power supply for its operations.

This dc voltage has to be obtained from the ac supply. So rectification process is required.


## Types of Rectifiers:

### Rectifier Circuits.

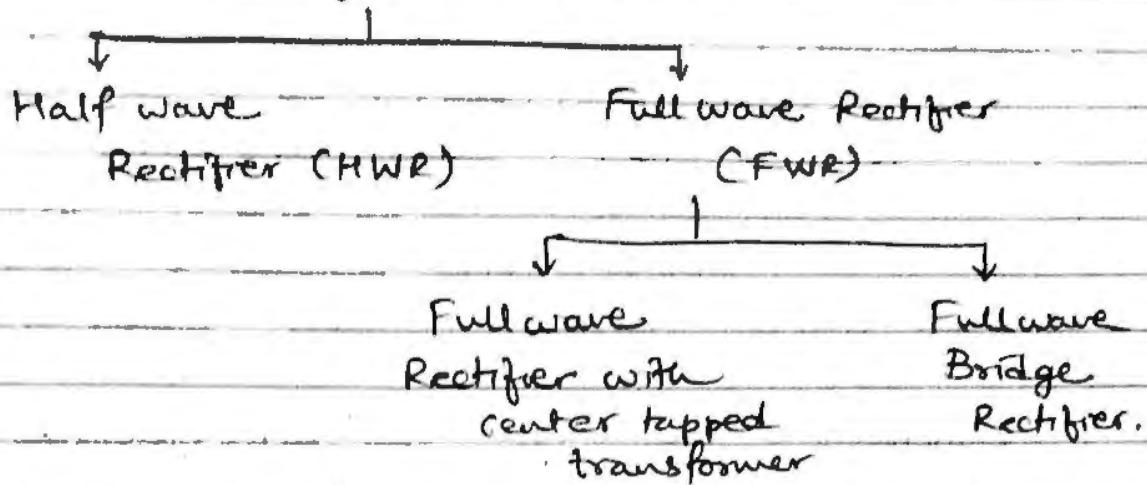


Q. Write short note on "Half wave Rectifier".

### Circuit Diagram:

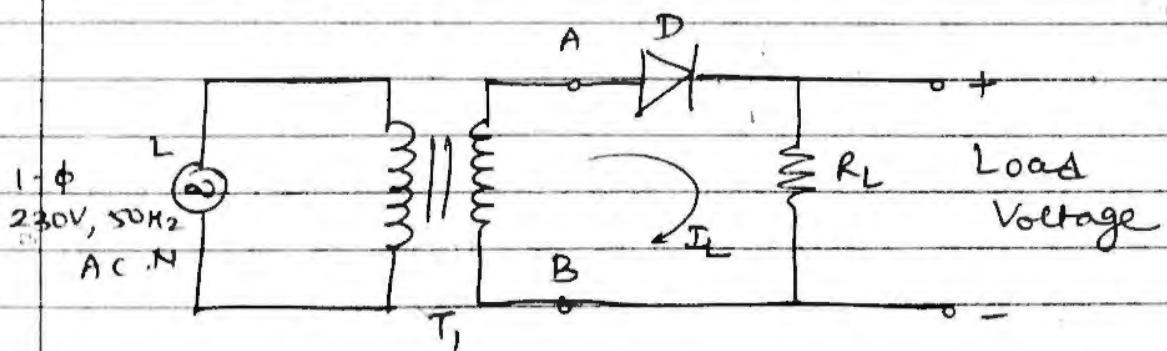


- In half-wave rectifier, the rectifier is on only during one half cycle of the Ac supply.
- So output is produced in half cycle only, output is zero in other half cycle, so name is Half wave Rectifier.

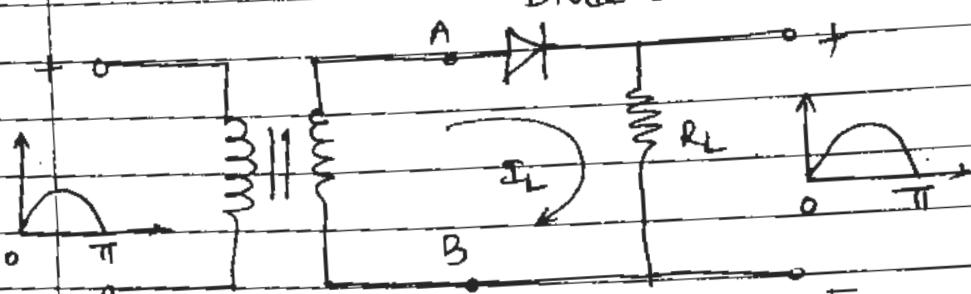Operation in positive half cycle of Supply: Let  
Diode ON.




- In positive half cycle of ac supply, terminal A is positive with respect to B, so Diode is in forward bias, & starts conducting.
- $V_{AB}$  is secondary voltage, and it appears almost as it is across load resistance. (As voltage drop across conducting diode is very small.)

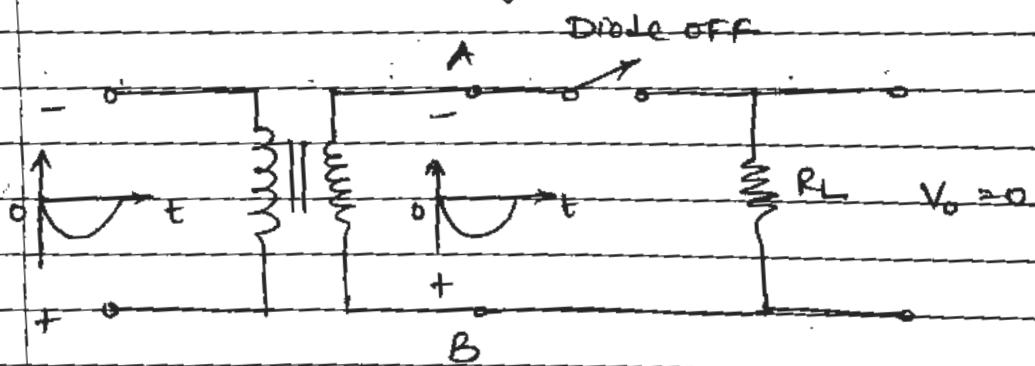Operation in negative half cycle of Supply.




- In negative half cycle of the ac supply ( $\pi$  to  $2\pi$ ) secondary voltage  $V_{AB}$  is negative, i.e. A terminal is negative with respect to B.
- Hence diode is reverse biased and offers a very high resistance. Hence we can replace it by open-circuited switch.
- Load is disconnected from the secondary, hence the load voltage & load current both are zero.

## Wave forms:

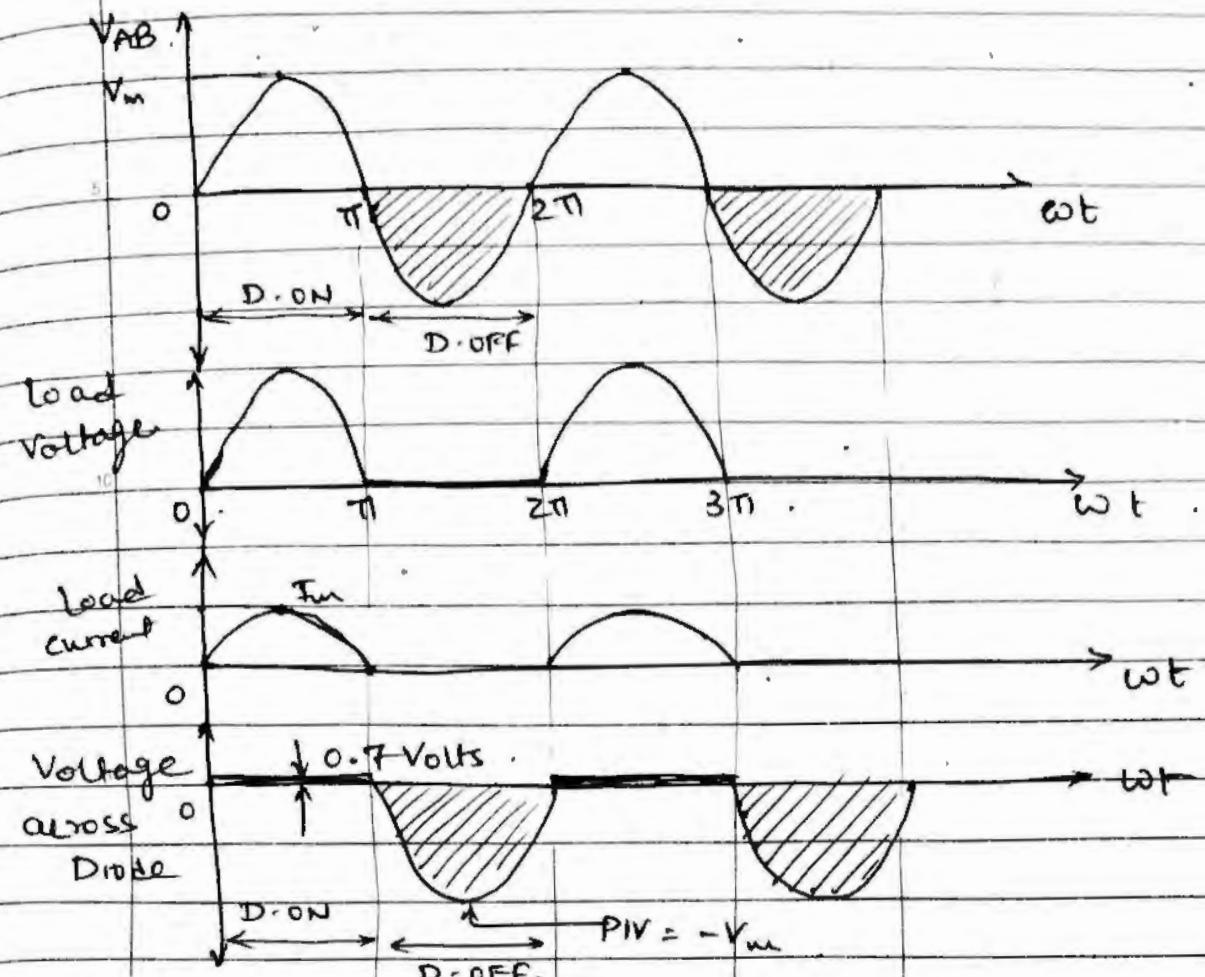

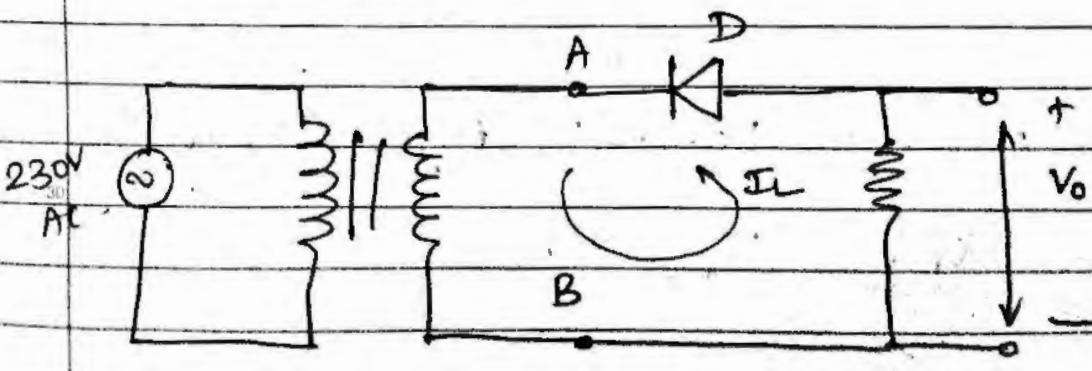
## \* Negative Halfwave Rectifier:

- In Half wave rectifier if diode conducts only during negative half cycle of the ac supply, then it is called negative halfwave Rectifier.
- Circuit Diagram is shown below.



## Analysis of Halfwave Rectifier:
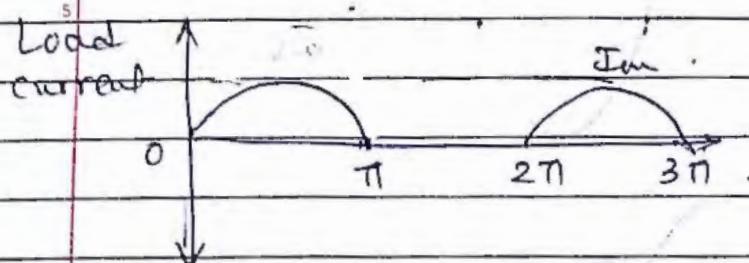
### 1) DC or Average Load Current ( $I_{Ldc}$ )



$$I_{av} = I_{Ldc} = \frac{1}{2\pi} \int_0^{\pi} I_m \sin \omega t \, d\omega t$$

$$= -\frac{I_m}{2\pi} [\cos \omega t]_0^{\pi}$$

$$= -\frac{I_m}{2\pi} (\cos \pi - \cos 0)$$

$$= -\frac{I_m}{2\pi} (-1 - 1)$$

$$\boxed{I_{Ldc} = \frac{I_m}{\pi}}$$

$R_s$  = Transformer secondary resistance

$$I_m = \frac{V_m}{R_s + R_f + R_L}$$

$R_f$  = Diode forward Resistance

$V_m$  = Maximum or peak Secondary voltage

$R_L$  = Load Resistance

### 2) DC or Average Load Voltage ( $V_{Ldc}$ )

$$V_{Ldc} = I_{Ldc} \times R_L$$

$$V_{Ldc} = \frac{I_m}{\pi} \times R_L$$

$$V_{dc} = \frac{V_m}{\pi(R_s + R_L + R_f)} \times R_L \quad \underline{\text{exact}}$$

usually  $R_s$  &  $R_f$  are small.

$$R_s + R_f \ll R_L$$

$$\text{so, } (R_s + R_f + R_L) \approx R_L$$

$$V_{dc} = \frac{V_m}{\pi \cdot R_L} \times R_L$$

$$V_{Ldc} = \frac{V_m}{\pi}$$

### 3) AC or RMS Load Current ( $I_{Lrms}$ )

$$I_{Lrms} = \left[ \frac{1}{2\pi} \int_0^{\pi} I_m^2 \sin^2 \omega t dt \right]^{1/2}$$

$$= \left[ \frac{I_m^2}{2\pi} \int_0^{\pi} \left( \frac{1 - \cos 2\omega t}{2} \right) dt \right]^{1/2}$$

$$= \frac{I_m}{2} \left[ \frac{1}{\pi} (\pi - \frac{1}{2} \sin 2\pi) \right]^{1/2}$$

$$= \frac{I_m}{2} \left[ \frac{1}{\pi} \times \pi \right]^{1/2}$$

$$I_{Lrms} = \frac{I_m}{2}$$

#### 4) AC or RMS value of Load Voltage: ( $V_{L\text{rms}}$ )

$$V_{L\text{rms}} = I_{L\text{rms}} \times R_L = \frac{I_m}{2} \times R_L$$

$$= \frac{V_m}{2(R_s + R_f + R_L)} \times R_L$$

$(R_s + R_f) \ll R_L$

So,  $V_{L\text{rms}} \approx \frac{V_m}{2}$

#### 5) Ripple Factor (RF):

##### Ripple Factor

- Ripple factor indicate how close rectified output is to the pure dc.
- Ripple factor is amount of AC component present in DC output.

$$\text{Ripple factor} = \sqrt{\left(\frac{V_{L\text{rms}}}{V_{L\text{dc}}}\right)^2 - 1}$$

$$\text{rf} = \sqrt{\left(\frac{V_{L\text{rms}}^2 - V_{L\text{dc}}^2}{V_{L\text{rms}}^2}\right)}$$

$$\text{rf} = \sqrt{\frac{(V_m/2)^2 - (V_m/\pi)^2}{(V_m/\pi)^2}}$$

$$\text{rf} = 1.21 \text{ or } 121\%$$

### 6) DC output Power $P_{LDC}$ :

$$P_{LDC} = I_{LDC}^2 \times R_L = \left(\frac{I_m^2}{\pi^2}\right) R_L$$

But,  $I_m = \frac{V_m}{(R_s + R_L + R_f)}$

$$(R_s + R_L) \ll R_L \text{ so, } I_m = \frac{V_m}{R_L}$$

$$\text{so, } P_{LDC} = \frac{V_m^2}{\pi^2 R_L} \cdot R_L = \frac{V_m^2}{\pi^2 R_L}$$

$$P_{LDC} = \frac{V_{LDC}^2}{R_L}$$

### 7) AC Input Power ( $P_{AC}$ )

$$P_{AC} = I_{SRMS}^2 \times (R_s + R_f + R_L)$$

$I_{SRMS}$  = RMS value of secondary current.

$$I_{SRMS} = I_{ARMS} = \frac{I_m}{2}$$

$$P_{AC} = \frac{I_m^2}{4} (R_s + R_f + R_L)$$

### 8) Rectification Efficiency or Power Conversion

Efficiency:

$$\eta = \frac{\text{DC output power}}{\text{AC input power}} = \frac{P_{LDC}}{P_{AC}}$$

$$\begin{aligned} \eta &= \frac{I_{LDC}^2 R_L}{I_{SRMS}^2 (R_s + R_f + R_L)} \\ &= \frac{\left(\frac{I_m^2}{\pi^2}\right)^2 \cdot R_L}{\left(\frac{I_m^2}{4}\right)^2 (R_s + R_f + R_L)} \end{aligned}$$

$$\eta = \frac{4}{\pi^2} \frac{R_L}{(R_s + R_f + R_L)}$$


$$(R_s + R_f) \ll R_L$$

$$\eta = \frac{4}{\pi^2} = 0.4 \text{ or } 40\%$$

→ Efficiency of Rectifier Should be as high as possible.
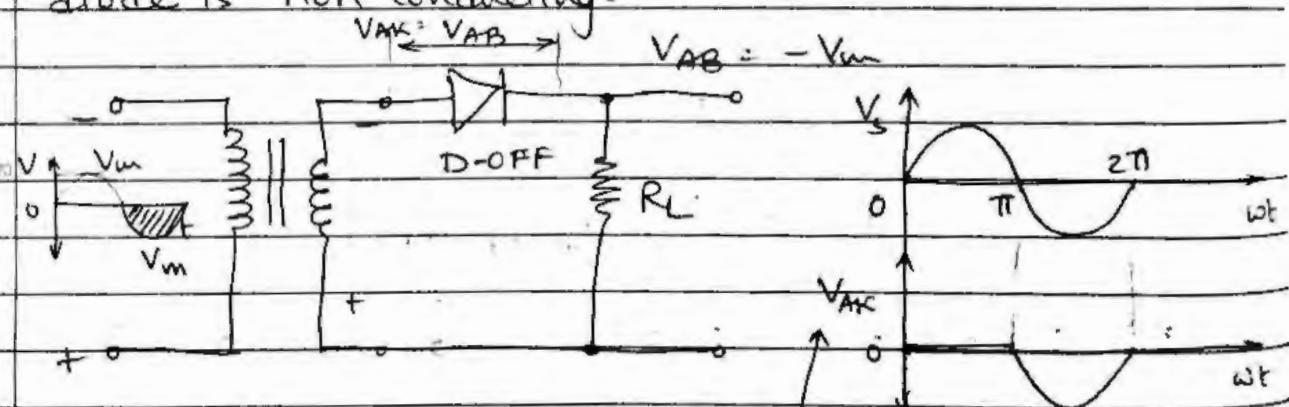
### g) Peak Inverse voltage (PIV):


- This is the maximum negative voltage which appears across a non conducting reverse biased diode.
- As shown in figure , the maximum negative voltage across the diode is  $-V_m$  volt, when diode is non conducting.



Voltage across diode


- PIV has been used to denote the maximum reverse voltage capability of a diode

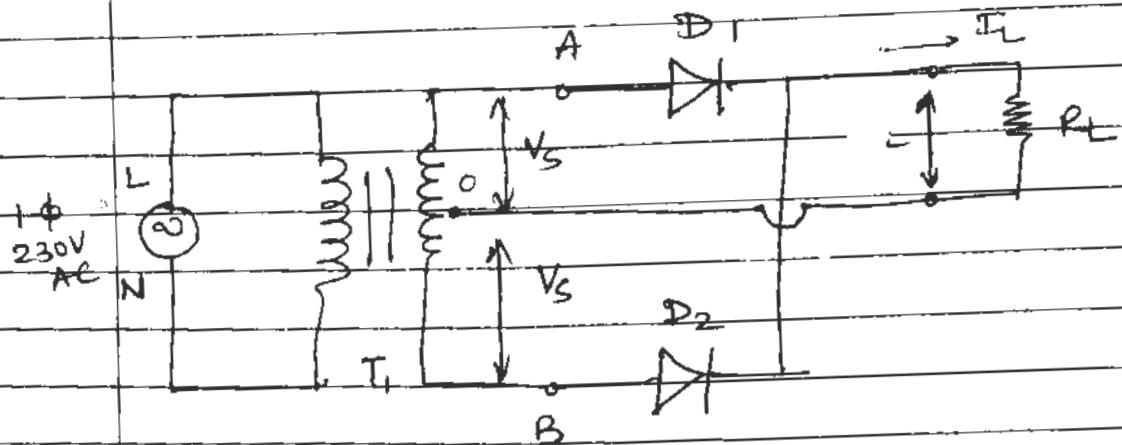Q. Write short note on Full wave Rectifier.




→ In Fullwave rectifier Load current flows in both half cycle of an AC supply.


### 1) Center tapped Transformer:

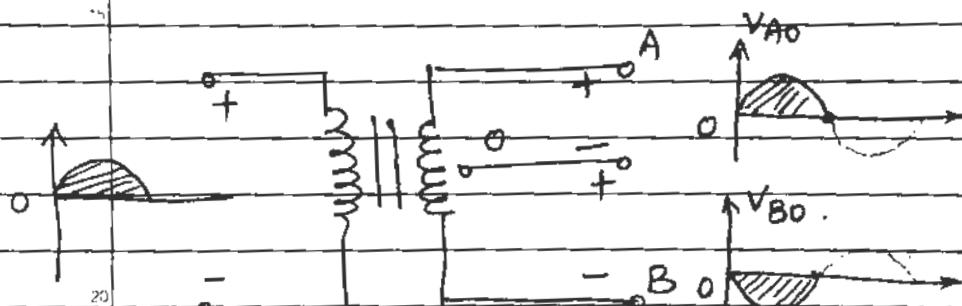

During positive half cycle

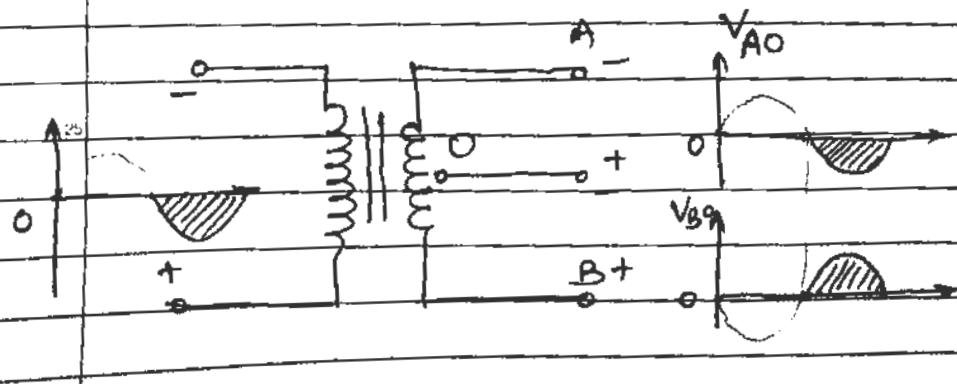

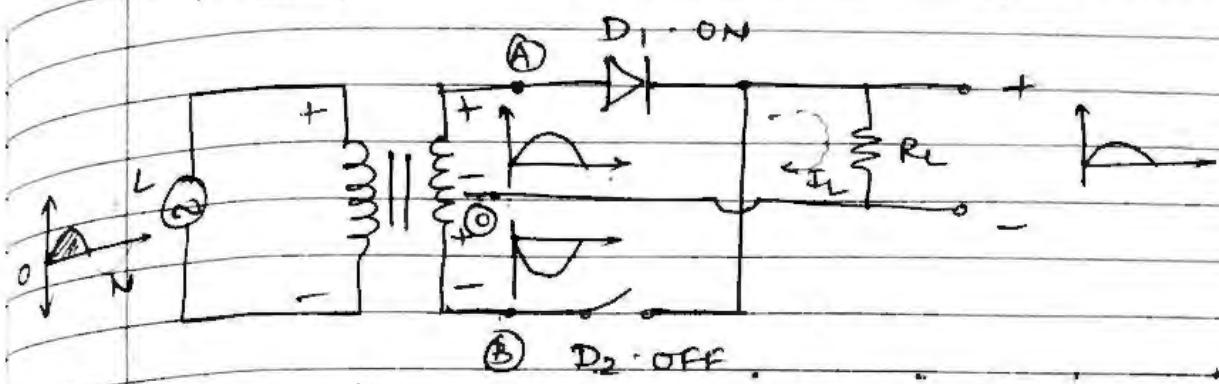
### Operation in positive half cycle: (0 to π)



- Due to center tapped transformer,  $V_{AO}$  &  $V_{BO}$  are always equal & opposite to each other.
- So,  $D_1$  is forward biased &  $D_2$  is reverse biased, Load current starts flowing from A through  $D_1$ , through  $R_L$  & back to point O.

### Operation in Negative half cycle:

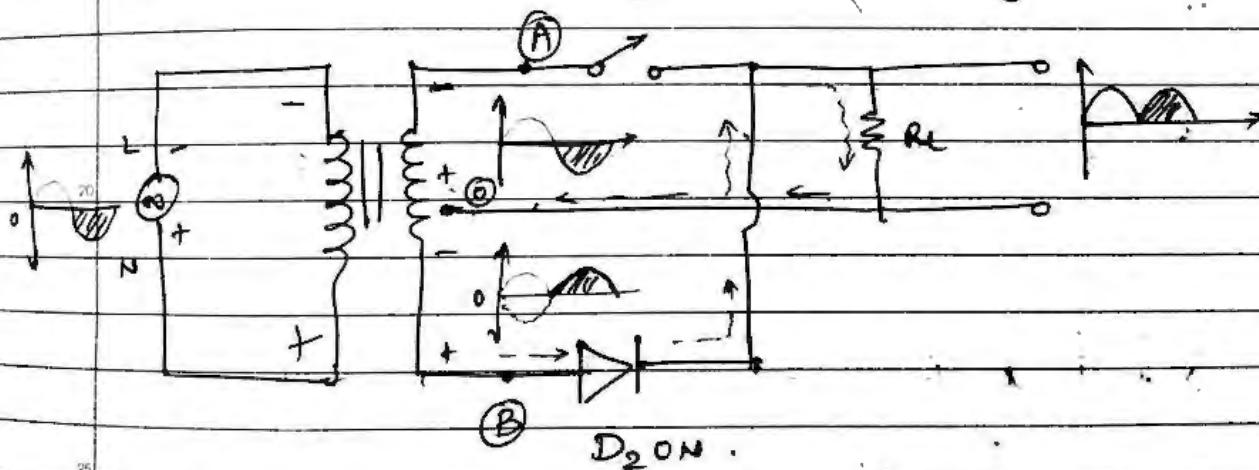


- for negative half cycle of supply, polarities for secondary induced voltages are shown as fig.
- Diode  $D_1$  is reverse biased &  $D_2$  is forward biased.
- Current flows from B, through  $D_2$ , then Resistor to terminal O. Current through

Load B in same direction as in positive half cycle.


### Waveforms:

Input voltage

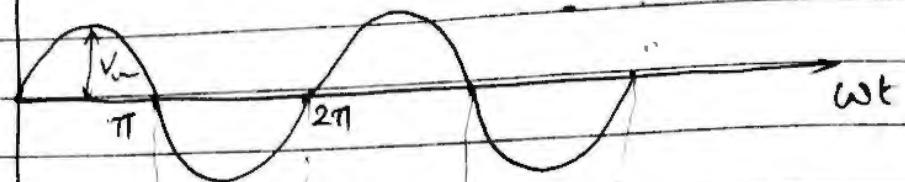


Load voltage

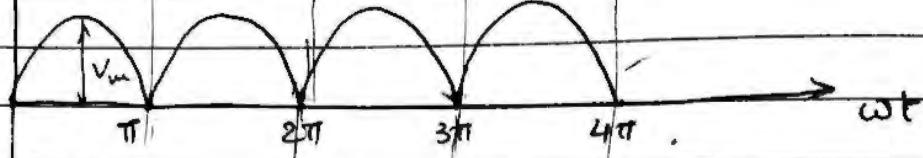$D_1$  - ON  $D_2$  - ON  $D_1$  - ON  $D_2$  - ON  
 $D_2$  - OFF  $D_1$  - OFF  $D_2$  - OFF  $D_1$  - OFF



$I_L$   
load current

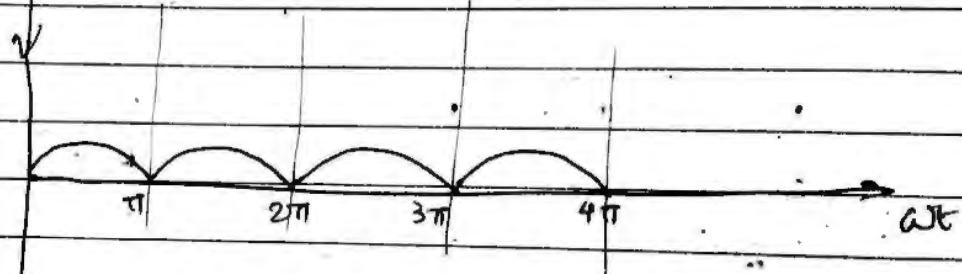

Voltage across

$D_1$

$\downarrow 0.7V$

$\uparrow$

$\uparrow$   $\pi$

$\uparrow$   $2\pi$

$\uparrow$   $3\pi$

$\uparrow$

$\uparrow$   $2V_m$

$\uparrow$


$\uparrow$  PIV.

$\rightarrow$

Full wave rectifier consist of two half wave rectifiers, which work independently & feed the common Load.

## Analysis of the Fullwave Rectifier.
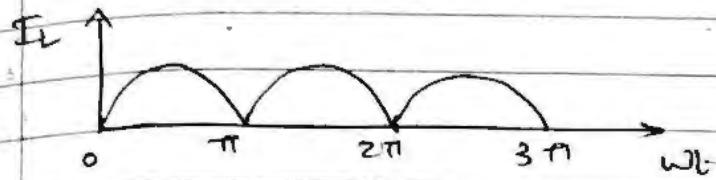
### 1) Average Load Current ( $I_{Ldc}$ )



$$I_{Ldc} = \frac{1}{\pi} \int_0^{\pi} I_m \sin \omega t \, d\omega t$$

$$= \frac{I_m}{\pi} [-\cos \omega t]_0^{\pi} = \frac{-I_m}{\pi} (\cos \pi - \cos 0)$$

$$= -\frac{I_m}{\pi} (-1 - 1)$$

$$\boxed{I_{Ldc} = \frac{2 I_m}{\pi}}$$

### 2) Average Load Voltage: ( $V_{Ldc}$ )

→ As Load is purely Resistive

$$V_{Ldc} = I_{Ldc} \times R_L$$

$$V_{Ldc} = \frac{2 I_m}{\pi} \times R_L$$

$$I_m = \frac{V_m}{(R_s + R_f + R_L)}$$

$$V_{Ldc} = \frac{2 V_m}{\pi (R_s + R_f + R_L)} \times R_L = \frac{2 V_m R_L}{\pi \cdot R_L}$$

$$(R_s + R_f) \ll R_L \text{ so, } V_{Ldc} \approx \frac{2 V_m}{\pi}$$

3) RMS Load Current ( $I_{L\text{rms}}$ ):

$$I_{L\text{rms}} = \left[ \frac{1}{\pi} \int_0^{\pi} (I_m \sin \omega t)^2 d\omega t \right]^{1/2}$$

$$= \left[ \frac{I_m^2}{2\pi} \int_0^{\pi} (1 - \cos 2\omega t) d\omega t \right]^{1/2}$$

$$= \left[ \frac{I_m^2}{2\pi} \left\{ (\omega t)_0^{\pi} - \frac{1}{2} (\sin 2\omega t)_0^{\pi} \right\} \right]^{1/2}$$

$$= \frac{I_m}{\sqrt{2}} \left[ \frac{1}{\pi} \left\{ (\pi) - \frac{1}{2}(0) \right\} \right]^{1/2}$$

$$\boxed{I_{L\text{rms}} = \frac{I_m}{\sqrt{2}}}$$

4) RMS Load Voltage: ( $V_{L\text{rms}}$ )

$$V_{L\text{rms}} = I_{L\text{rms}} R_L$$

$$= \frac{I_m}{\sqrt{2}} \times R_L$$

$$V_m = V_m R_L$$

$$\boxed{V_{L\text{rms}} = \frac{V_m}{\sqrt{2}}}$$

### 5) Ripple factor:

$$\text{Ripple factor (RF)} = \sqrt{\left(\frac{V_{L\text{rms}}}{V_{L\text{DC}}}\right)^2 - 1}$$

$$= \sqrt{\frac{(V_{L\text{rms}})^2 - (V_{L\text{DC}})^2}{(V_{L\text{DC}})^2}}$$

$$= \sqrt{\frac{\left(\frac{V_m}{\sqrt{2}}\right)^2 - \left(\frac{2V_m}{\pi}\right)^2}{\left(\frac{2V_m}{\pi}\right)^2}}$$

$$= \sqrt{\frac{\frac{1}{2} - \frac{4}{\pi^2}}{4/\pi^2}}$$

$$= \sqrt{\frac{\pi^2}{8}} = + = 0.48$$

= 48%

Value of Ripple factor for Full wave rectifier is much less (i.e. 0.48) than halfwave Rectifier (i.e. 1.21)

### 6) DC Output Power ( $P_{L\text{DC}}$ ):

$$P_{L\text{DC}} = I_{L\text{DC}}^2 \times R_L$$

$$I_{L\text{DC}} = \frac{2V_m}{\pi}$$

$$P_{L\text{DC}} = \frac{2V_m}{\pi} \times R_L$$

7) AC Input Power ( $P_{ac}$ ):

$$P_{ac} = I_{L_{rms}}^2 \times R_L$$

$$I_{L_{rms}} = I_{S_{rms}}$$

$$P_{ac} = I_{S_{rms}}^2 \times R_L$$

$$= \left( \frac{I_m}{\sqrt{2}} \right)^2 \times R_L$$

$$P_{ac} = \frac{I_m^2}{2} R_L$$

8) Rectifier Efficiency:

$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{I_{L_{dc}}^2 \times R_L}{I_{L_{rms}}^2 \times R_L}$$

$$= \frac{\left( 2 \frac{I_m}{\pi} \right)^2 \times R_L}{\left( \frac{I_m}{\sqrt{2}} \right)^2 \times R_L}$$


$$= \frac{4/\pi^2}{1/2} = \frac{8}{\pi^2}$$

$$\eta = \frac{8}{\pi^2} = 0.812 = 81.2\%$$

→ FWR efficiency is almost twice the HWR efficiency.
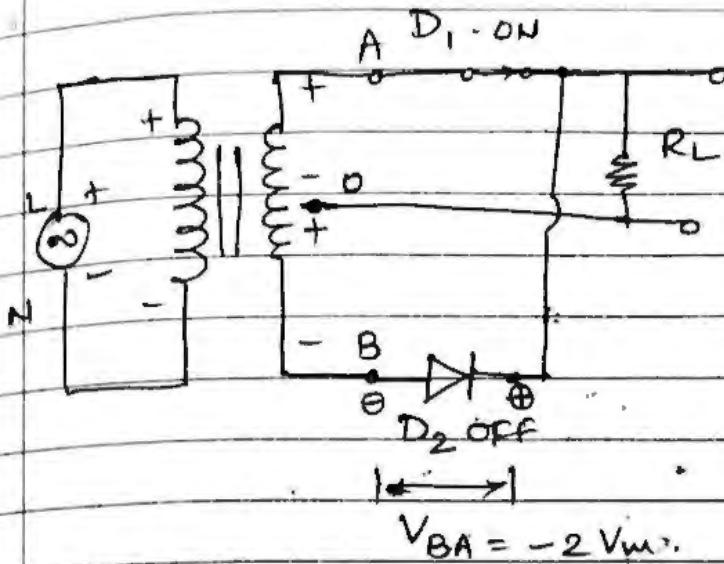
### g) Peak Inverse Voltage (PIV)

- To obtain PIV consider circuit shown below.
- D<sub>1</sub> is FWR in positive half cycle.



→ above figure shows in positive half cycle, D<sub>1</sub> is ON, so closed switch and D<sub>2</sub> is OFF, in reverse biased.

→ Voltage across D<sub>2</sub> is  $V_{BA}$  and i.e.  $-2V_m$

so  $PIV = 2V_m$ .


→ In FWR, PIV is high  $2V_m$ , as compare to HWR (i.e.  $V_m$ ); we need to select diodes of higher PIV ratings, which are costly.

### 25 Applications of FWR:

- Laboratory power supply
- High current power supply
- Battery chargers
- Power supplies for various electronic circuits.

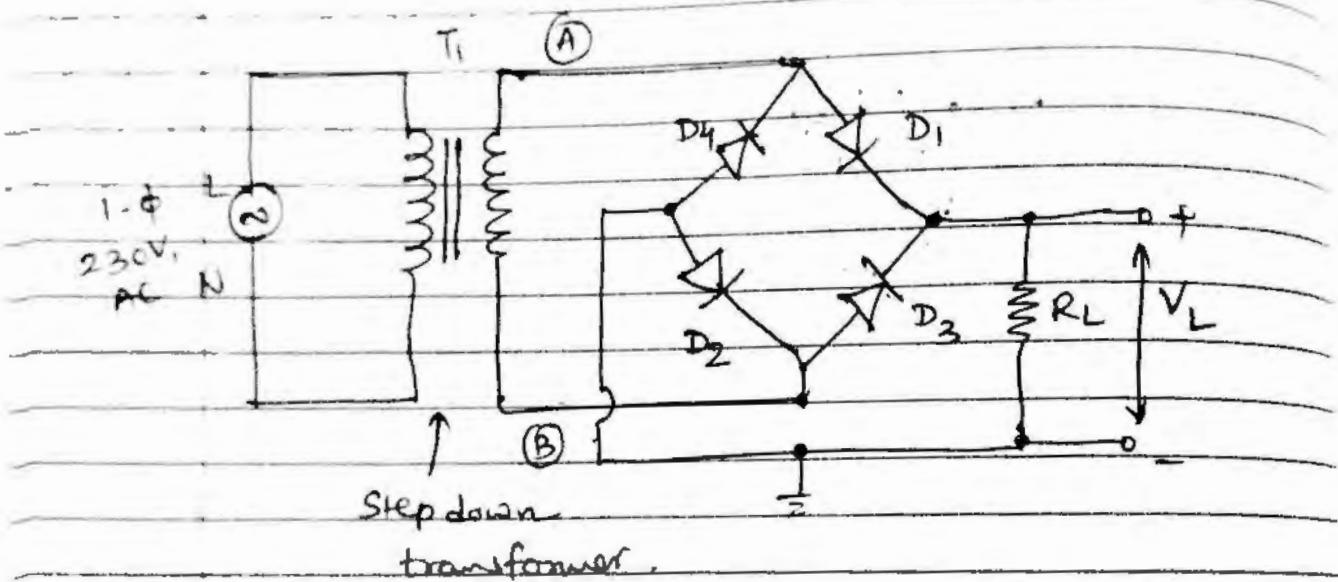
G. Write short Note on: Bridge Rectifier.

- Disadvantages of Full wave rectifier are high PIV & compulsory use of center tapped transformer.
- Above disadvantages are overcome in Bridge rectifiers.
- Circuit Diagram:




→ Center tapped transformer is not required.

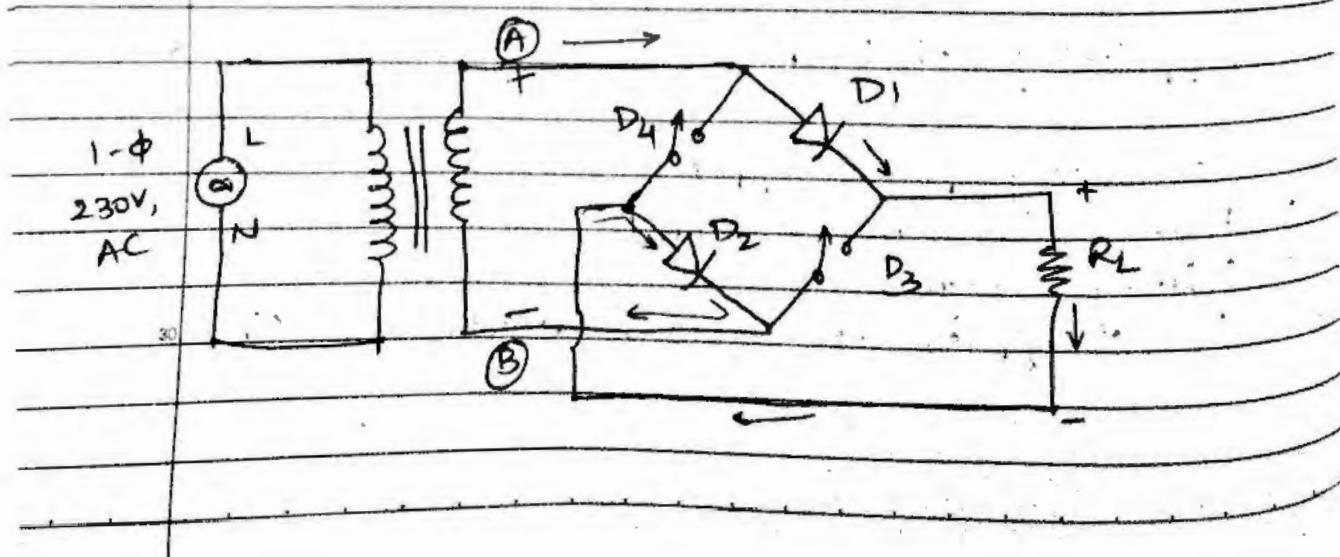\* Operation of Bridge Rectifier during positive half cycle ( $0 \leq wt \leq \pi$ ):




- During positive half cycle of the ac supply, secondary voltage  $V_{AB}$  is positive. Therefore diodes  $D_1$  &  $D_2$  are forward biased & Diodes  $D_3$  &  $D_4$  are reverse biased.
- Load current & Load voltage are positive.

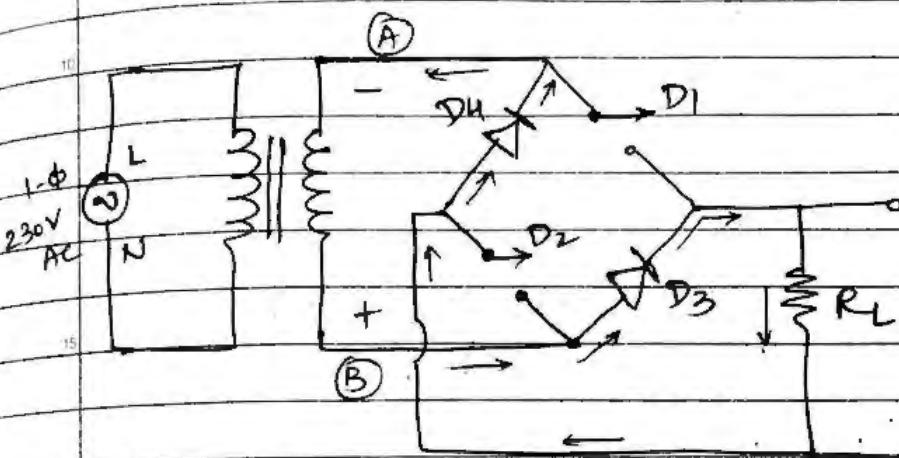\* Operation of Bridge Rectifier During negative half cycle: ( $\pi \leq \omega t \leq 2\pi$ ).



- During negative half cycle, secondary voltage  $V_{AB}$  is negative.
- Diode  $D_1$  &  $D_2$  are reverse biased &  $D_3$  &  $D_4$  are forward biased.

Waveforms

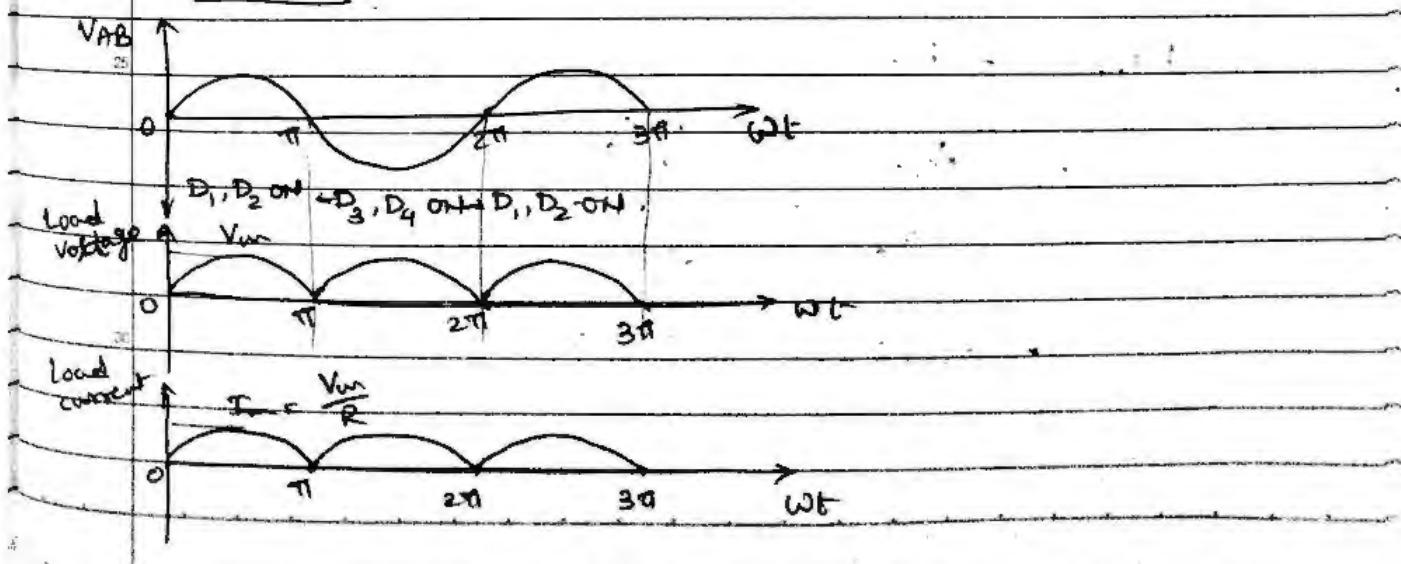

## Performance Parameters of a Bridge Rectifier

- Bridge rectifier is fullwave rectifier only.
- So,  $V_{Ldc}$ ,  $I_{Ldc}$ ,  $V_{Lrms}$  &  $I_{Lrms}$  have expressions as FWR
- only change in  $I_m = \frac{V_m}{(R_s + 2P_f + R_L)}$

1) DC output voltage:

$$V_{Ldc} = \frac{2V_m}{\pi}$$

2) DC output Current:

$$I_{Ldc} = \frac{V_{Ldc}}{R_L} = \frac{2V_m}{\pi \cdot R_L} = \frac{2I_m}{\pi}$$

3) RMS output voltage:

$$V_{Lrms} = \frac{V_m}{\sqrt{2}}$$

4) RMS output current:

$$I_{Lrms} = \frac{I_m}{\sqrt{2}}$$

5) Ripple factor:

$$\gamma = \left[ \left( \frac{V_{Lrms}}{V_{Ldc}} \right)^2 - 1 \right]^{1/2}$$

$$= 0.482 = 48.2\%$$

### 6) Rectification Efficiency:

$$\eta = \frac{P_{Ldc}}{P_{ac}}$$


$$= \frac{I_{Ldc}^2 \cdot R_L}{I_{Srms}^2 (R_L + R_f + R_L)}$$

$$\eta_{max} = \frac{I_{Ldc}^2 \cdot R_L}{I_{Lrms}^2 \cdot R_L}$$

$$= \frac{(2Im/\pi)^2}{(Im/\sqrt{2})^2} = \frac{8}{\pi^2} = 0.812$$

$$\boxed{\eta = 81.2\%}$$

### 7) Peak Inverse Voltage (PIV):

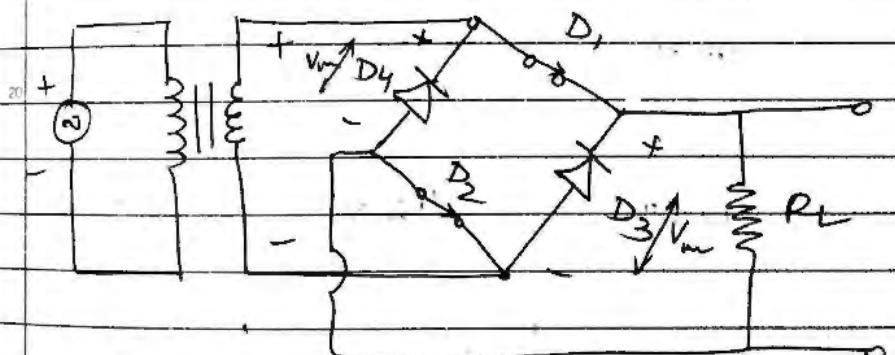

$$\boxed{PIV = V_m}$$

### Applications of Bridge Rectifier:


- Laboratory dc power supply
- High current power "
- Battery charger
- DC Power Supply for various Electronic circuits

Q. Comparison of the Rectifier Circuits.

Parameters	HWR	FWR	Bridge Rectif.
1. DC or Average load current	$\frac{I_m}{\pi}$	$\frac{2I_m}{\pi}$	$\frac{2I_m}{\pi}$
2. Maximum average load voltage	$\frac{V_m}{\pi}$	$\frac{2V_m}{\pi}$	$\frac{2V_m}{\pi}$
3. RMS load current $I_{L_{rms}}$	$\frac{I_m}{2}$	$\frac{I_m}{\sqrt{2}}$	$\frac{I_m}{\sqrt{2}}$
4. RMS load voltage $V_{L_{rms}}$	$\frac{V_m}{2}$	$\frac{V_m}{\sqrt{2}}$	$\frac{V_m}{\sqrt{2}}$
5. DC load Power $P_{dc}$	$\frac{I_m^2}{\pi^2} R_L$	$\frac{4I_m^2 R_L}{\pi^2}$	$\frac{4I_m^2 R_L}{\pi^2}$
6. Rectification efficiency	40 %	81-2 %	81-2 %
7. Ripple factor	121 %	118 %	118 %
8. No. of diodes used	one	two	four
9. Center tap transformer	Not required	required	Not required
10. Peak Inverse Voltage (PIV)	$V_m$	$2V_m$	$V_m$
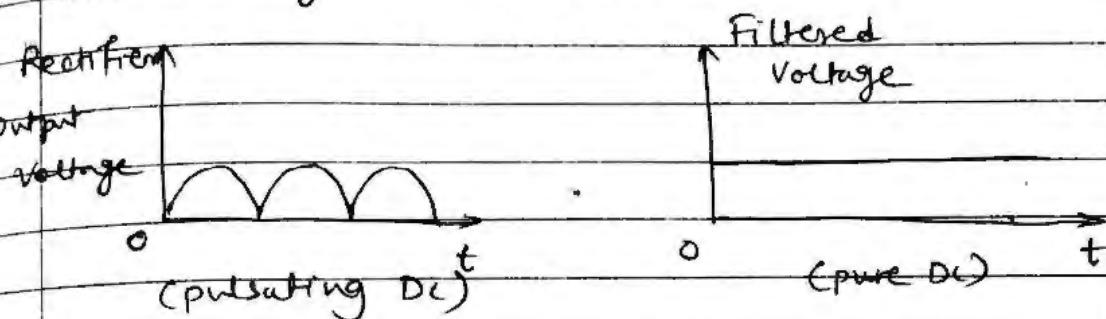
## \* Filters:

- Filters are electronic circuits used along with rectifiers in order to get a pure (ripple free) DC output.
- Till now we have seen that all rectifiers's output is "pulsating" DC voltage. But we want pure DC voltage, so we use filters.




## Types of Filters:

- 1) RC filters (Capacitor input filters).
- 2) LC filters.




Q. Write short Note on "RC filters".

- Shunt capacitor filter (RC filter) is used to reduce the ripple contents in the output of a rectifier, to obtain pure DC.


## Connection of RC filter.

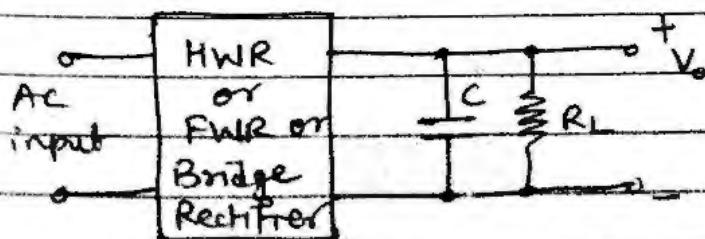
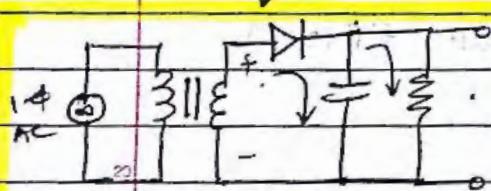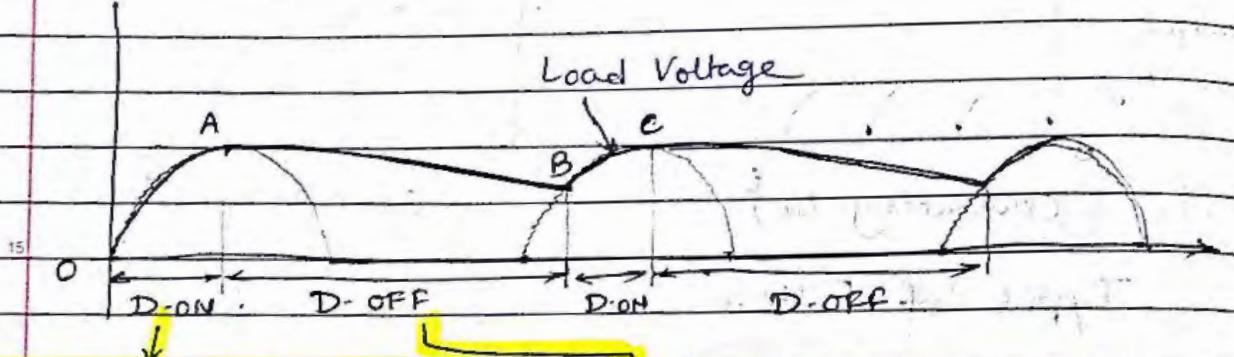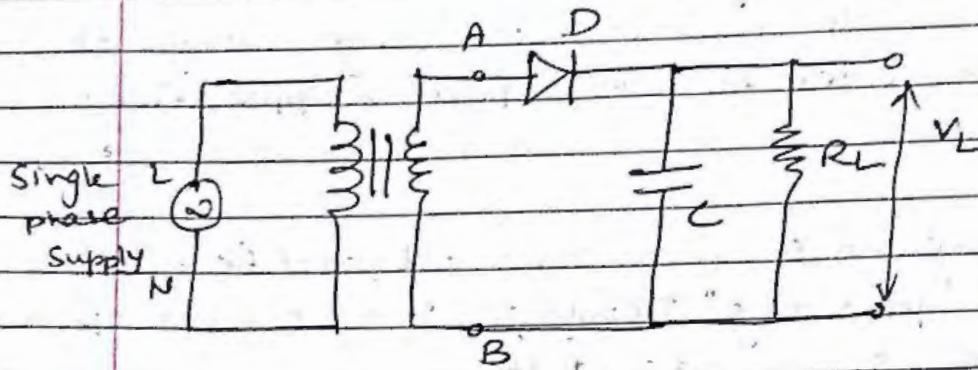
## Halfwave Rectifier with capacitor Input Filter (RC filter)



Capacitor charge to  
 $V_{max}$

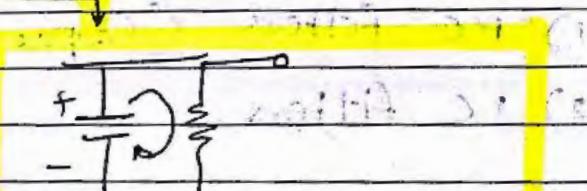

D is OFF

& as cathode

voltage (capacitor voltage)

is higher than

anode (input voltage)

Voltage


- For interval 0 to A, diode is in forward bias & capacitor will charge to  $V_{max}$ .
- for A to B, diode anode voltage is less than capacitor voltage (due to negative half cycle) so, diode is in reverse bias condition, so

capacitor will discharge through Resistor.


from B to C, capacitor, diode D<sub>3</sub> is in forward bias & capacitor charge.

Output voltage (Load Voltage) is shown in figure.

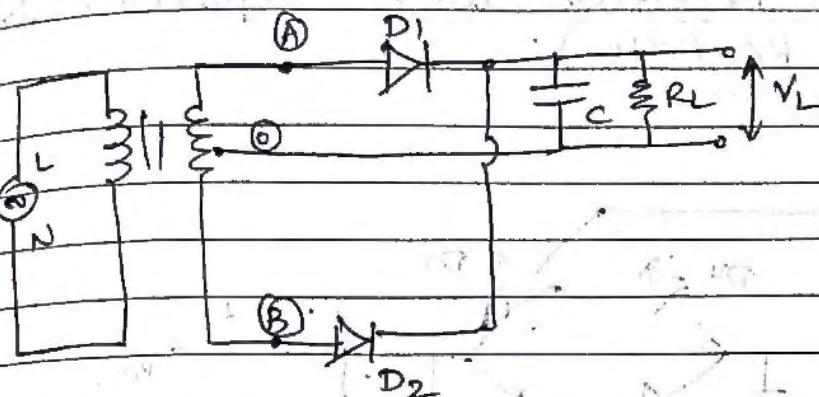
### \* Fullwave Rectifier with Capacitor filter



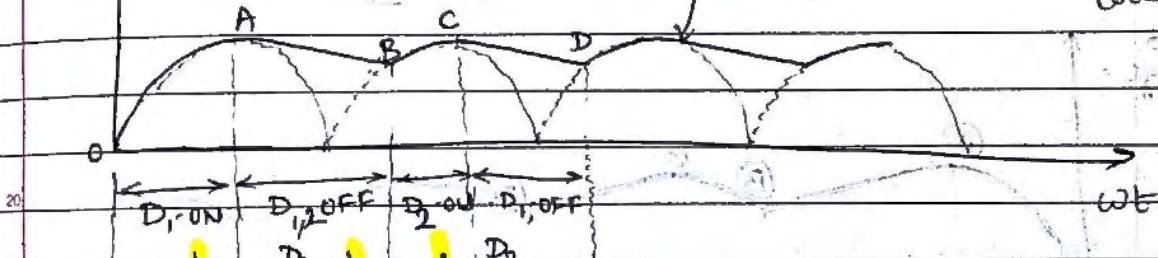
V<sub>L</sub> → Voltage across capacitor or load



D<sub>1</sub> ON

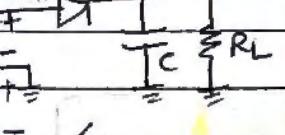

i<sub>t</sub>

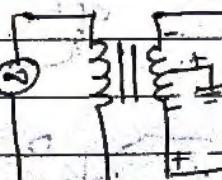

D<sub>2</sub> ON

- from 0 to A, D<sub>1</sub> is in forward bias & D<sub>2</sub> is in reverse biased; capacitor will charge to V<sub>m</sub>
- from A to B, D<sub>1</sub> is in reverse bias & D<sub>2</sub> is also in reverse biased condition so, capacitor will discharge the load. Resistor



## LC Filters:

- When the load current is large, LC filter are an improvement over RC filters.
- Using LC filter we can reduce the ripples so low ripple factor.
- Diodes don't have to carry surge currents.

## Surge Current:


"The initial rush of current when power is turned on is called surge current." So, diodes must be selected with enough current rating to withstand surge current.

## LC Filter with HWR:

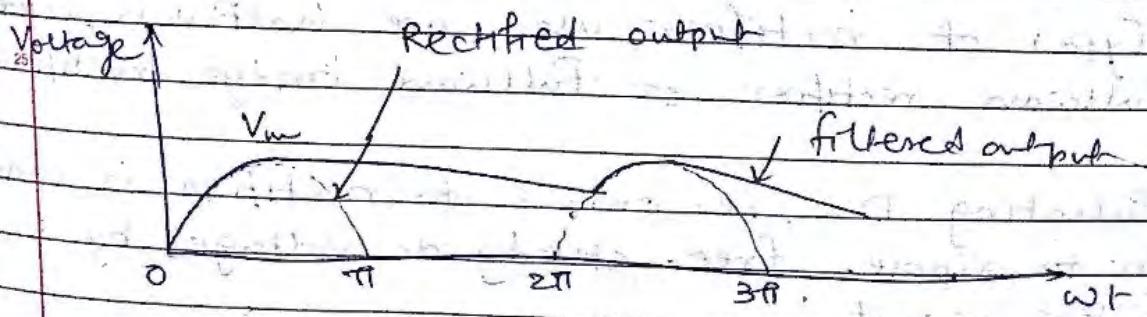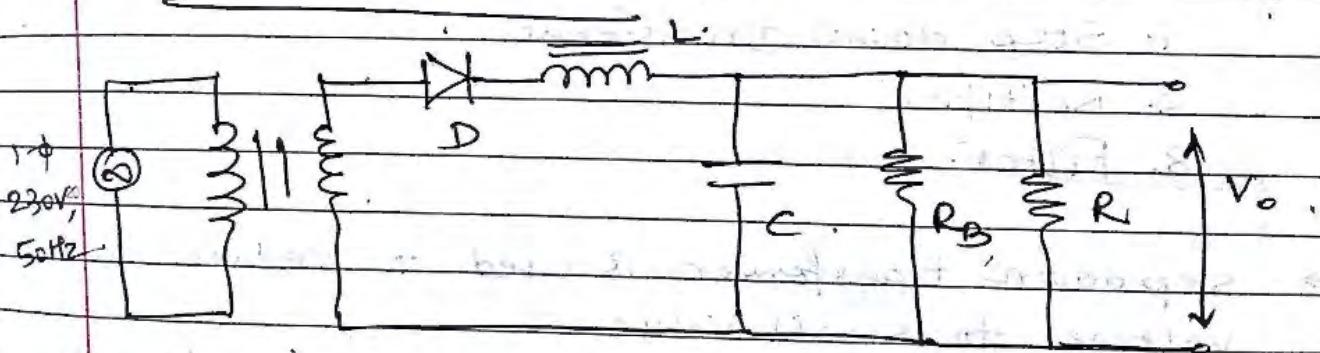

- R<sub>B</sub> is called bleeder resistance, it is used to maintain continuous current through inductor.

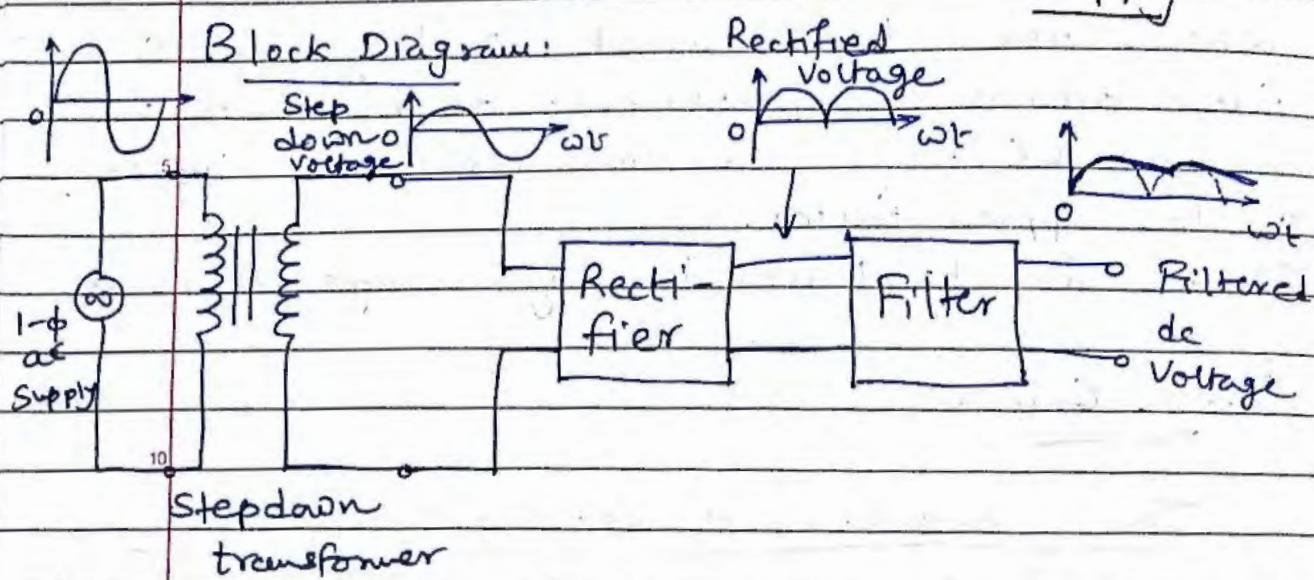Q. Write Short note on "Unregulated Power Supply"



Basic Building blocks of an unregulated dc power supply are:

1. Step down transformer
2. Rectifier
3. Filter.

- Step down transformer is used to reduce ac main voltage to small value.
- Then rectifier converts Ac to pulsating dc. Types of rectifier used are halfwave rectifier, fullwave rectifier or Full wave bridge rectifier.
- Pulsating DC, i.e. output of rectifier is converted into ripple free steady dc voltage by filter circuit.
- Filtered output is very close to pure dc.

## Clippers or Limiter:

→ A diode clipper or limiter is a wave shaping circuit that takes the input waveform & cutoff or clips its top half or bottom half or both.

### Classification of Clippers

#### Clippers

Unbiased  
Clipper

Biased  
Clipper

Series  
Clipper


Parallel  
Clipper

Series  
Clipper

Parallel  
Clipper

Q. Write short note on Series clipper.

#### Series Negative Clipper:

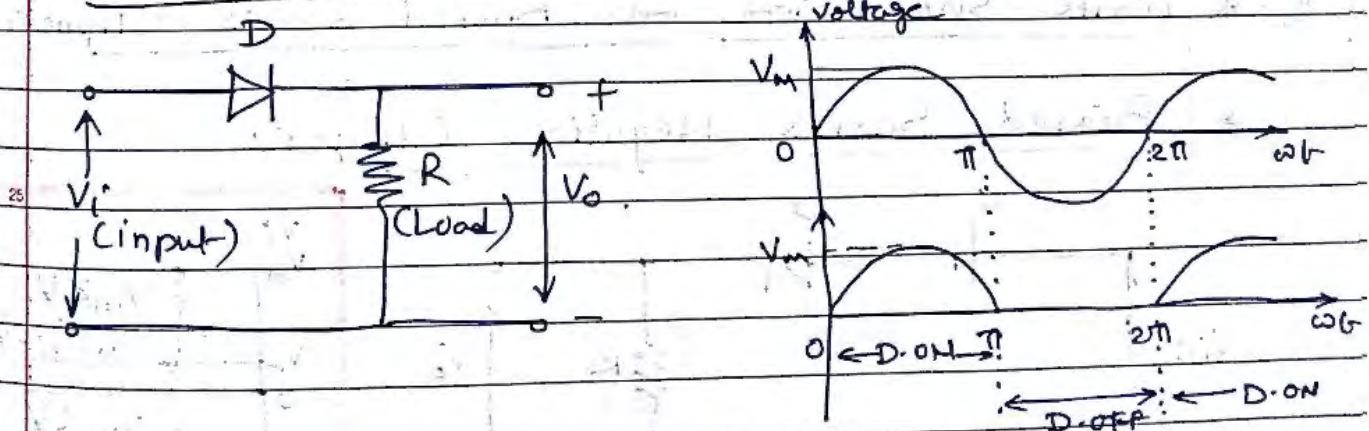


→ Negative clipper is same as half wave rectifier.

→ During the half cycle of input D is on & output  $V_o$  is same as  $V_i$ .

- During Negative half cycle of input Diode is OFF (reverse bias) and output voltage is 0.
- So negative cycle of input is clipped off.

### \* Series Positive Clipper:

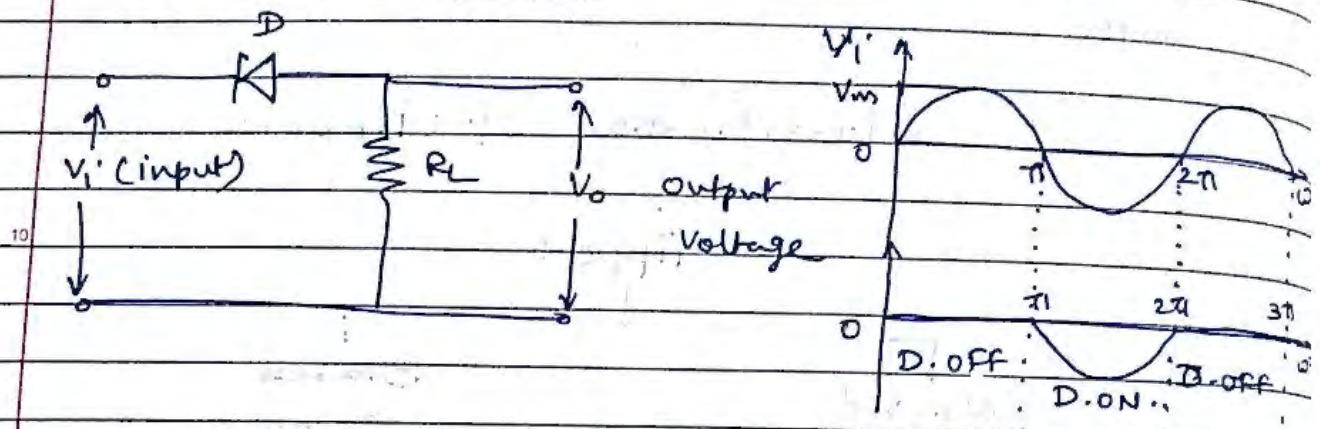


→ When positive half cycle of input is there, diode is in reverse biased condition, so Diode is open circuited & output voltage is zero.

→ When negative half cycle of input, diode is in forward biased condition, so diode is closed circuited & output voltage is same as input.


### Q. \* Write short note on Biased series Clipper:

#### \* Biased Series Negative Clipper:

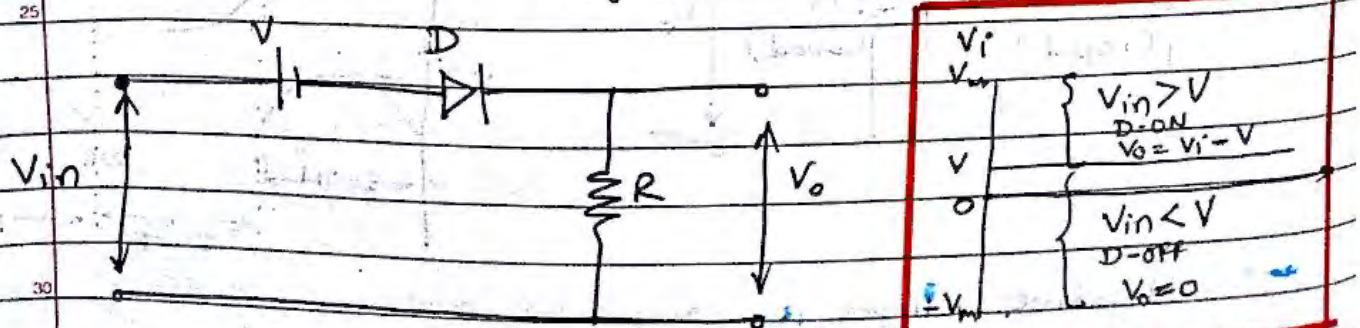


Just to remember.

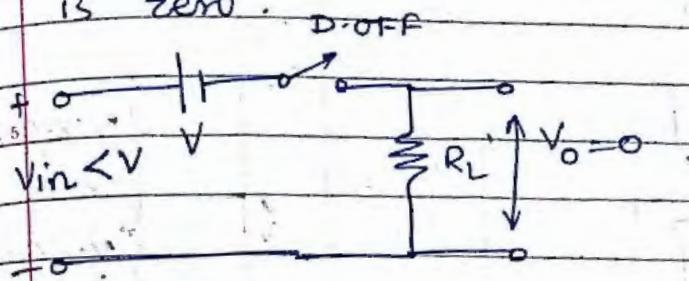
→ When  $V_{in}$  is positive, But  $V_{in} < V$ , then diode is in reverse bias condition and output voltage is zero.



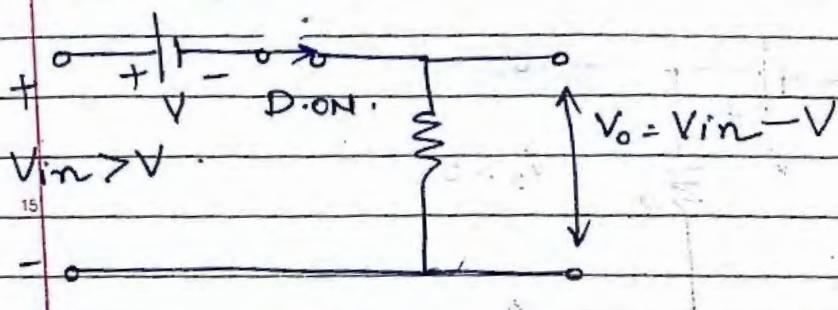
→ When  $V_{in}$  positive, But  $V_{in} > V$ , then diode is forward bias and so output voltage is same as input



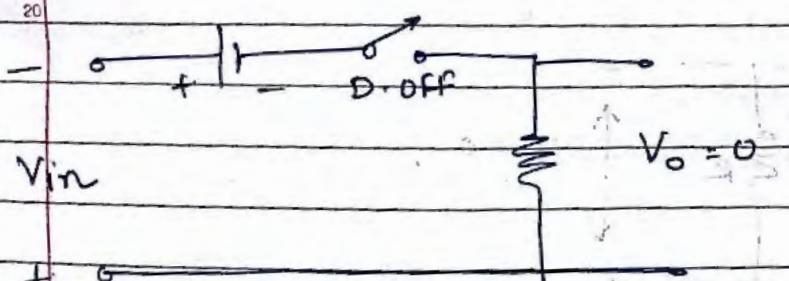→ When  $V_{in}$  is negative, Diode is in reverse bias condition, so diode is open circuit.




Waveforms.

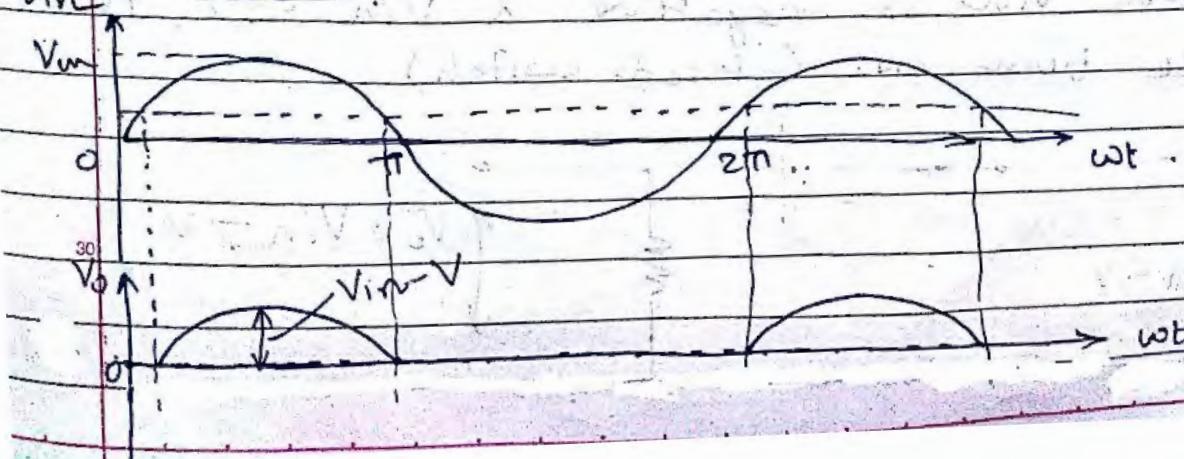


## \* Biased Series positive clipper

To Remember

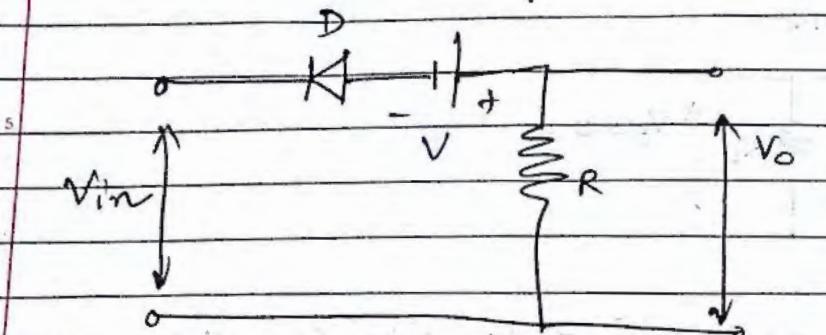


$V_i > (-V)$	D-OFF	$V_o = 0$
$V_i < (-V)$	D-ON	$V_o = V_i - V$

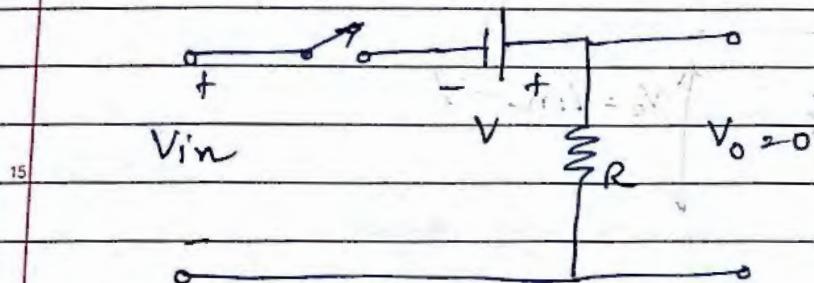- When  $V_{in}$  positive diode is in reverse bias  
so  $V_o = 0$ .




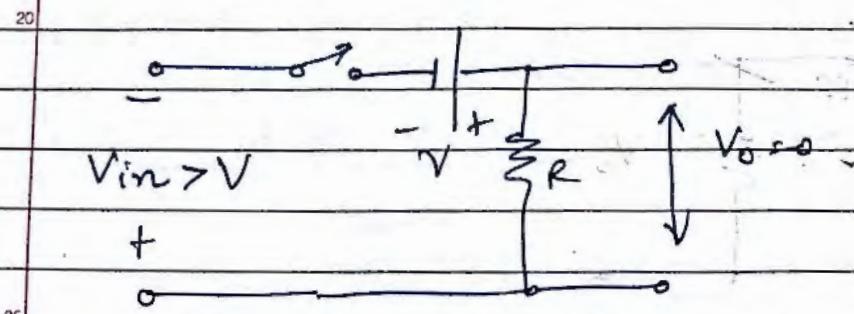- When  $V_{in}$  is negative but  $V_{in} > V$  then diode remains off



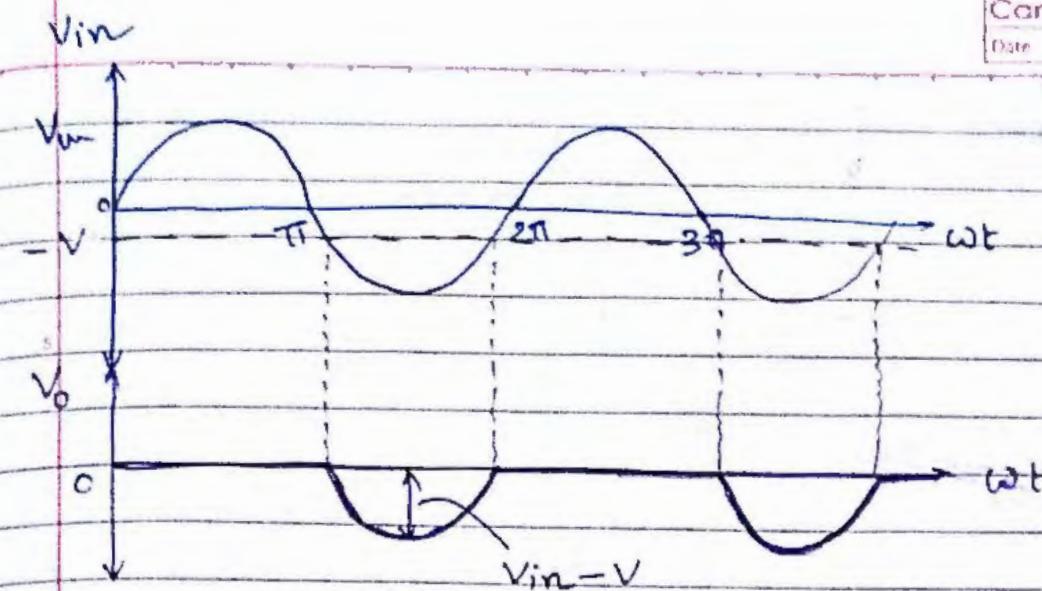- When  $V_{in}$  is negative &  $V_{in} < V$ , then diode turns on. (closed switch)






## \* Parallel Clipper Circuit:

(Parallel Positive Clipper)

To Remember.


Circuit Diagram:

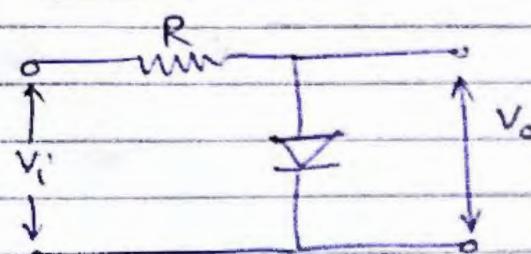

$V_i$	$V_o$
$+V_m$	{ +ve halfcycle D-O.N. $V_o = 0.7V$
$-V_m$	{ -ve halfcycle D-O.F. $V_o = V_i$


→ Operation with positive half-cycle:

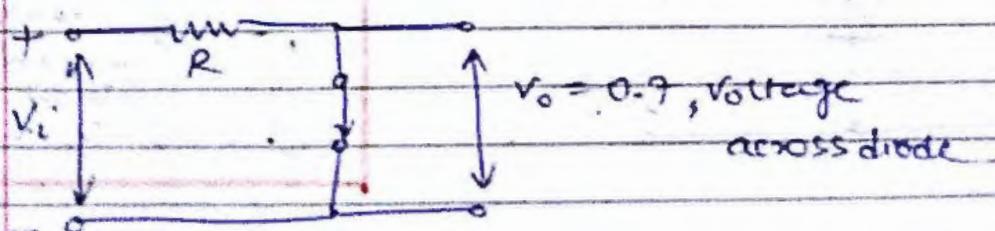when  $V_{in}$  is positive diode is in forward bias  
(diode is ON).




→ Operation with Negative half cycle

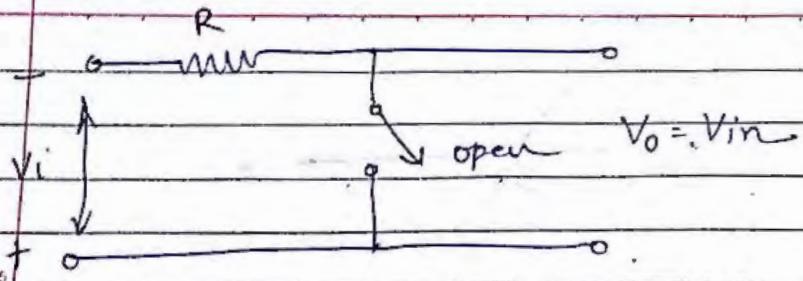when  $V_{in}$  is negative, diode is in reverse bias  
(diode is OFF).




Waveforms.

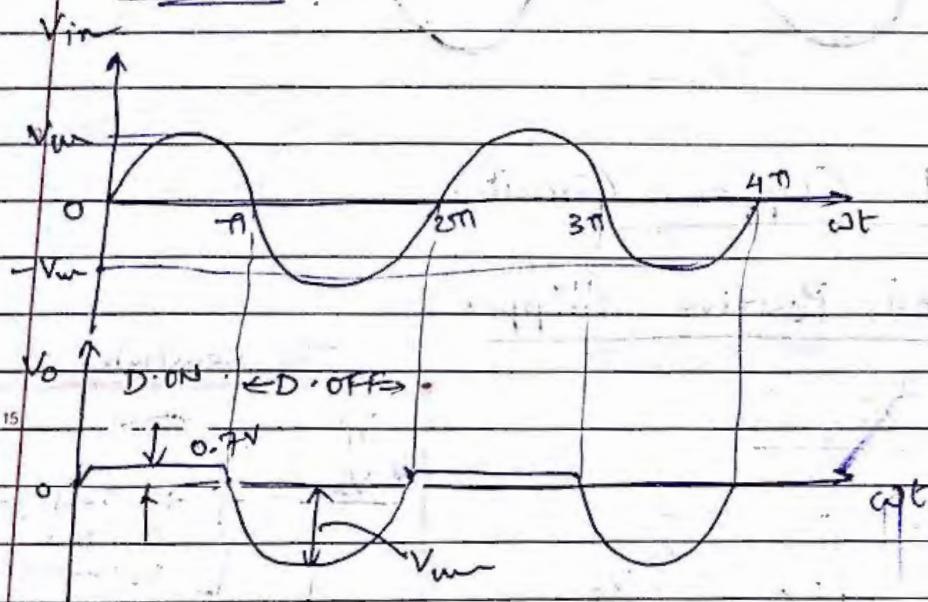

### Parallel Negative Clipper:

To Remember:

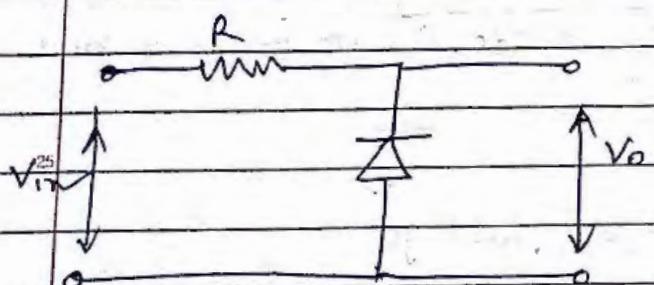


$V_i$	$\left\{ \begin{array}{l} +ve \text{ halfcycle} \\ D-\text{off} \end{array} \right.$
$V_o$	
0	$\left\{ \begin{array}{l} -ve \text{ halfcycle} \\ D-\text{on} \end{array} \right.$
$-V_o$	

→ Operation During positive half cycle.


→ When  $V_{in}$  is +ve, Diode is off

$$\text{So, } V_o = V_{in}$$

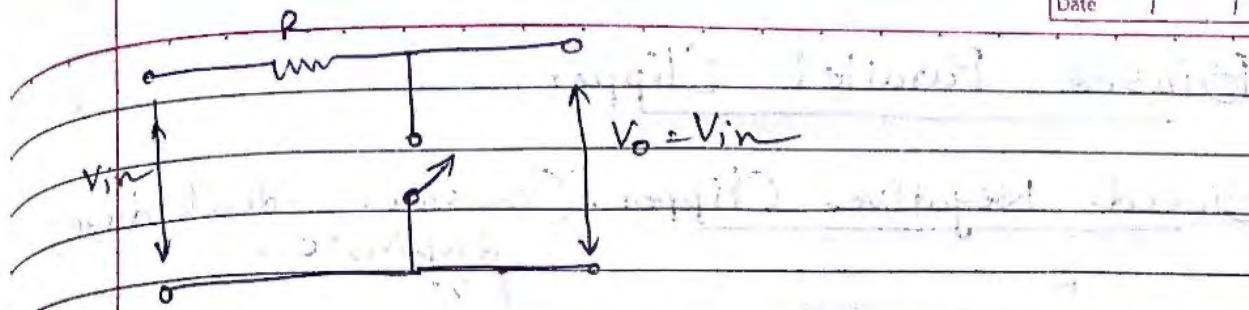


→ Operation During Negative half-cycle:

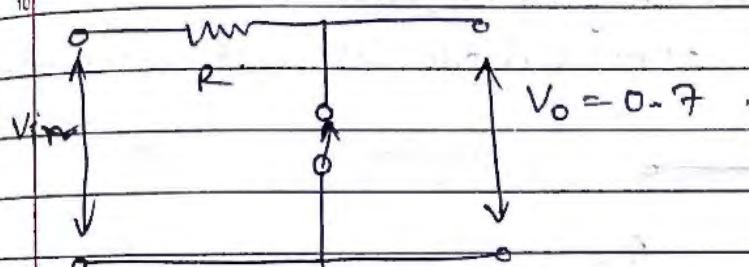When  $V_{in}$  is -ve diode  $D$  is off. &  $V_o = 0.7$ , i.e., voltage across diode





Waveforms:

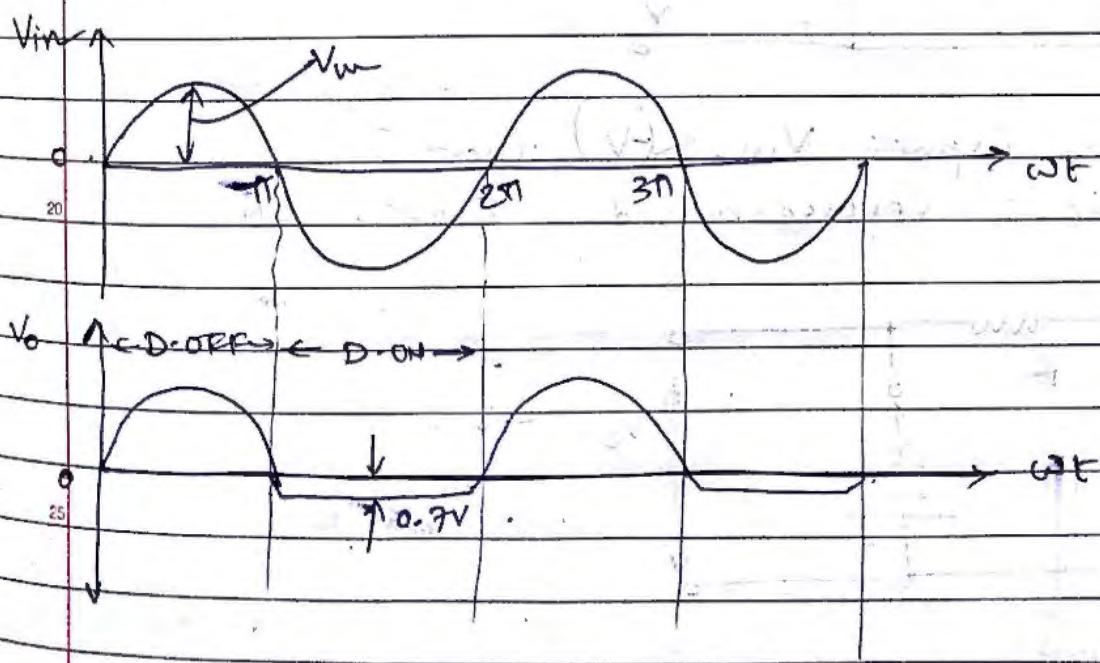

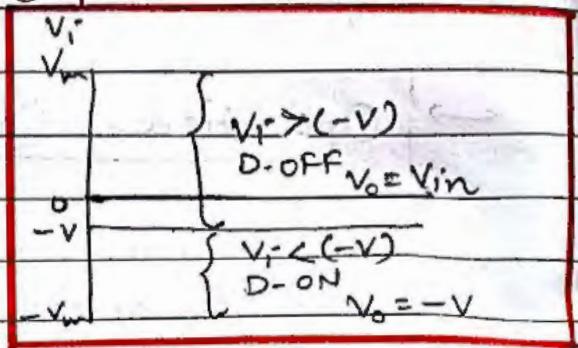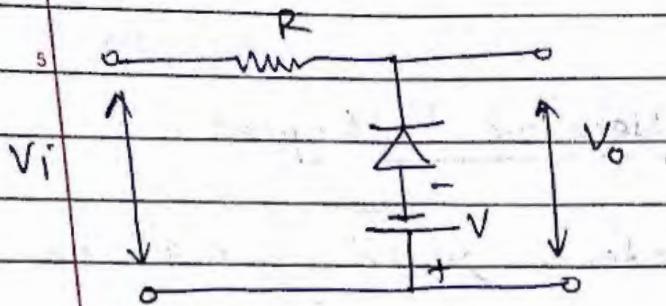
# \* Biased Parallel Clipper.

\* Biased Negative Clipper. (consider ideal diode)  
drop  $V_D = 0$ .



→ When input  $V_{in}$  is greater than  $V$ .

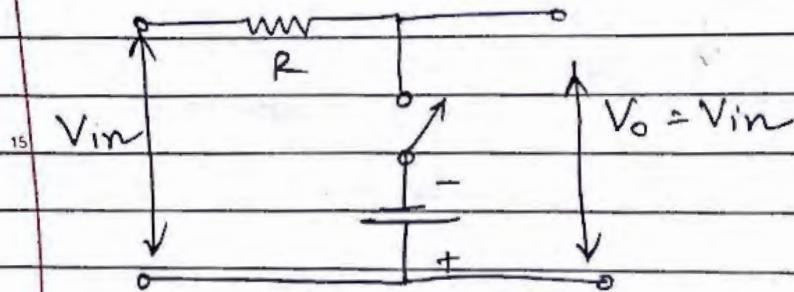
( $V_{in} > V$ )) diode OFF Diode is in Reverse Biased  
so,




→ When input  $V_{in} < (-V)$  then

Diode is forward-biased Diode - ON.

so,

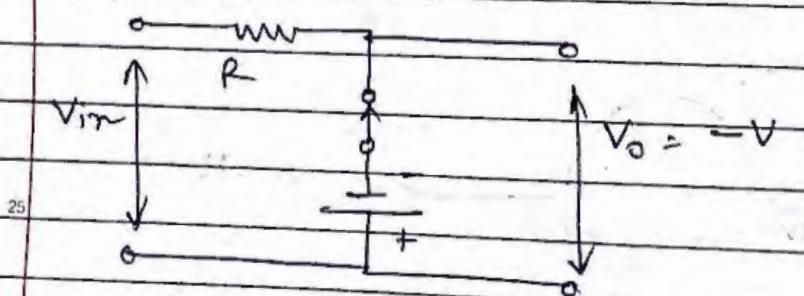


Waveforms:

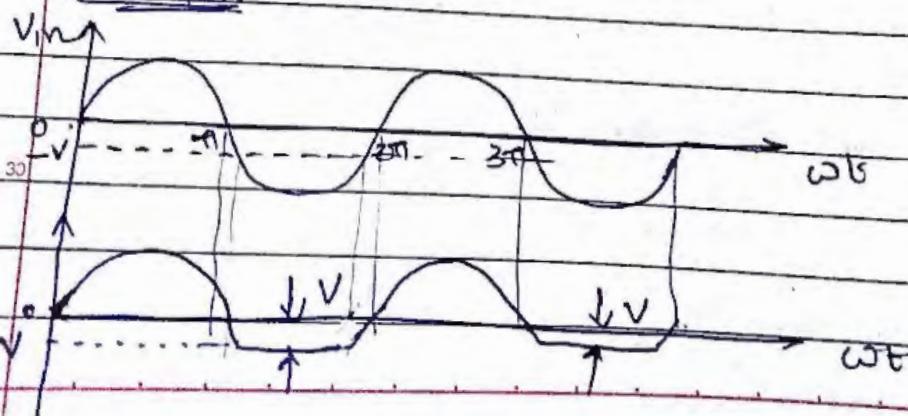


## Biased Positive Clipper (Consider ideal diode)

drop.  $V_D = 0$

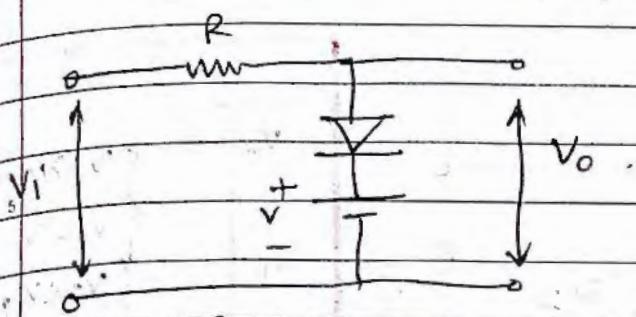


$V_i$	$V_{in}$	$V$	$0$	$-V_m$
$\left\{ \begin{array}{l} V_i > V, D\text{-ON} \\ V_o = V \end{array} \right.$				
$\left\{ \begin{array}{l} V_i < V, D\text{-OFF} \\ V_o = V_{in} \end{array} \right.$				

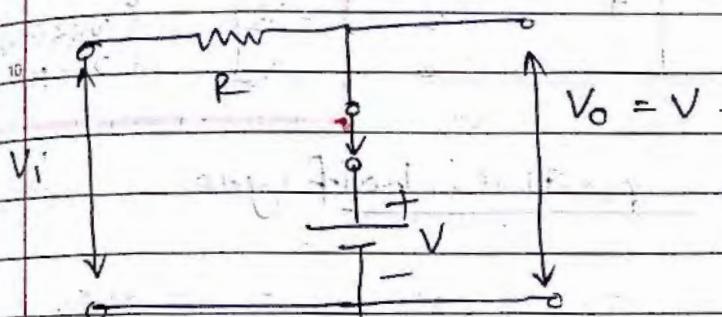
→ When  $V_{in} > V$  then diode is on. (forward bias)



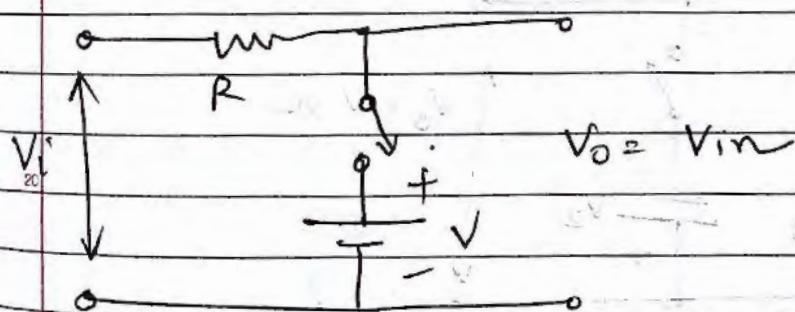→ When  $V_{in} < V$  then diode is in Reverse bias.




### Waveforms:

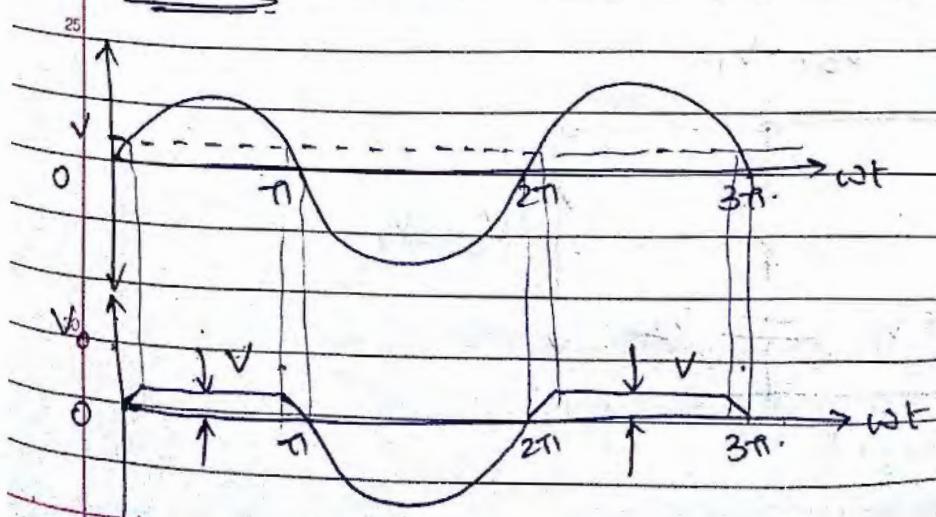

## Two Way Parallel Clipper Circuit:

Circuit Diagram:

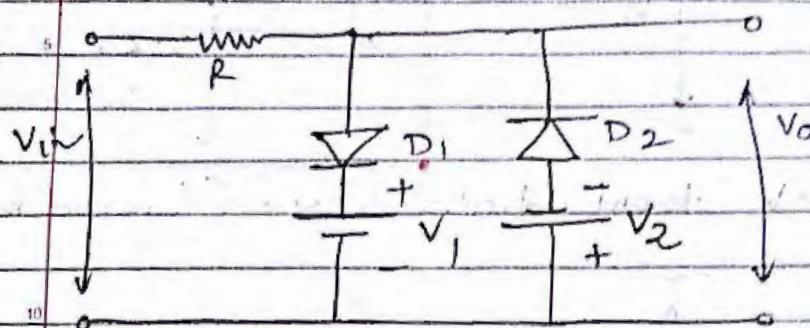


$V_{in}$	$V_o$
$V_{in} > V_1$	$D_1 \text{ ON}, D_2 \text{ OFF}$
$V_o = V_1$	
$V_{in} < V_1$	$V_{in} > (-V_2)$
$D_1 \text{ OFF}, D_2 \text{ ON}$	$V_o = V_{in}$
$-V_2$	$V_{in} < (-V_2), D_2 \text{ ON}$
$-V_2$	$D_1 \text{ OFF}, V_o = -V_2$


→ Operation during positive half cycle:

When  $V_i < V_1$ ,  $D_1$  is OFF &  $D_2$  is ON.

So,  $V_o = V_{in}$

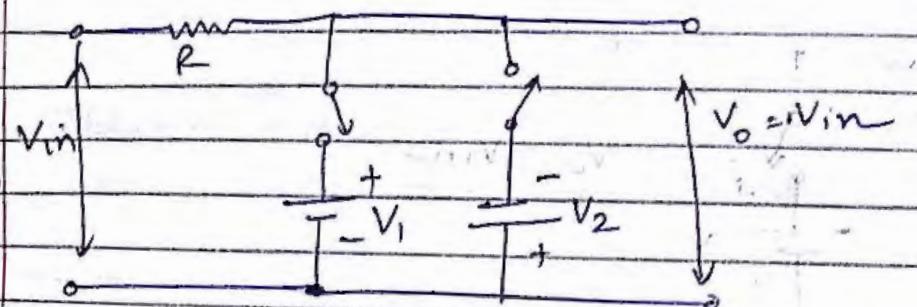

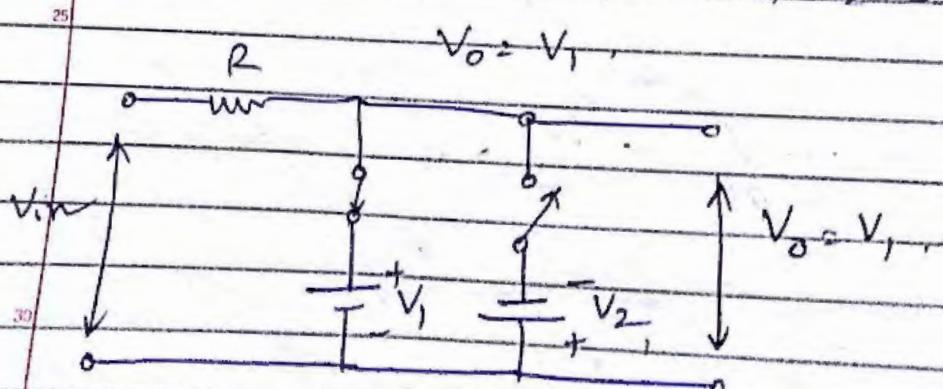
When  $V_i \geq V_1$ ,  $D_1$  is ON,  $D_2$  is OFF.



\* Operation during Negative half-cycle.


→ when  $V_{in} > (-V_2)$ ,

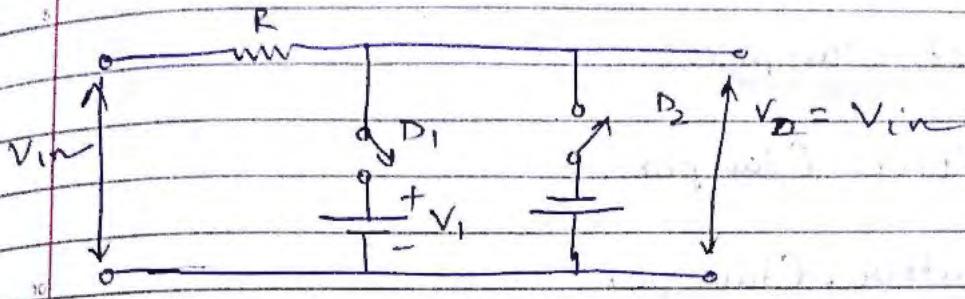$D_1$  OFF,  $D_2$  ON.  $V_o = V_{in}$ .




→ when  $V_{in} < (-V_2)$ .

$D_1$  ON,  $D_2$  OFF.  $V_o = -V_2$ .

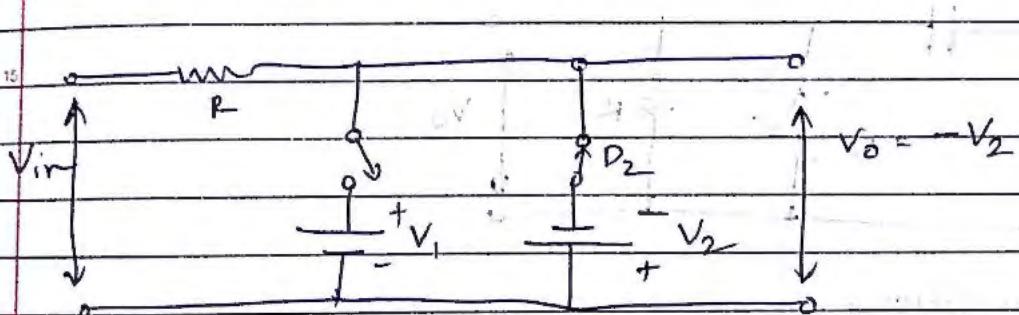

Waveforms:

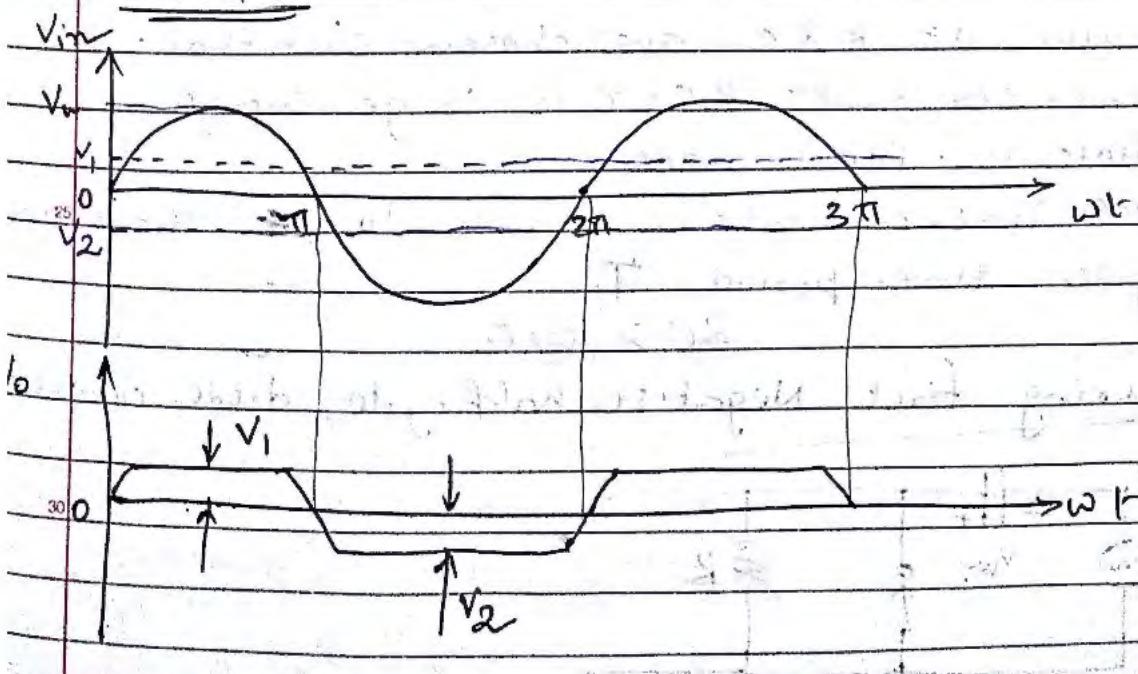

## Clamper Circuit Using Diode


→ Clamper is the circuit which is used to clamp the input signal to a different dc level.

### Types of Clampers:

1) Positive Clamper


2) Negative Clamper.

### \* Positive Clamper:

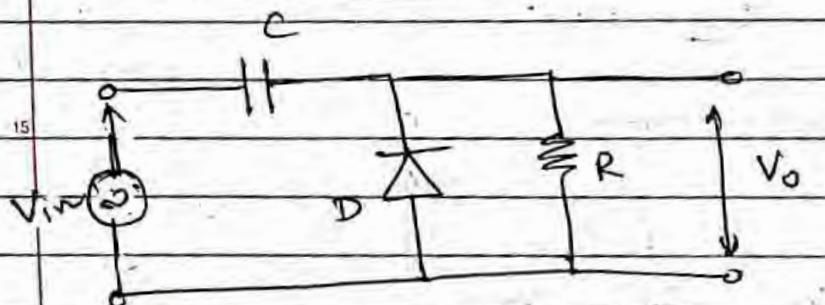

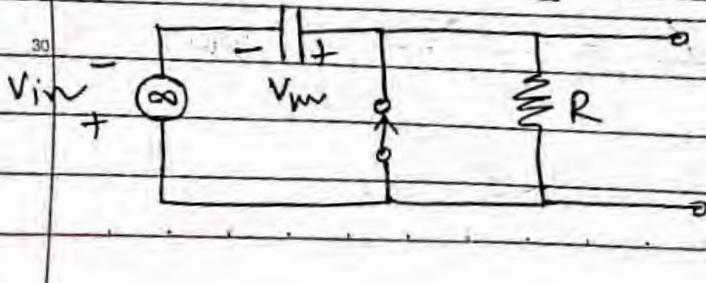
### Assumptions:

- input is a perfect sine waveform
- value of  $R$  &  $C$  are chosen such that the Time constant  $RC = T$  is large enough.
- diode is ideal diode
- $RC$  Time constant is much longer than one cycle time period.  $T$ .  
 $RC > 100T$ .
- During first negative half cycle diode conducts.




Once capacitor charge to  $V_m$ , diode will remain in reverse bias condition.

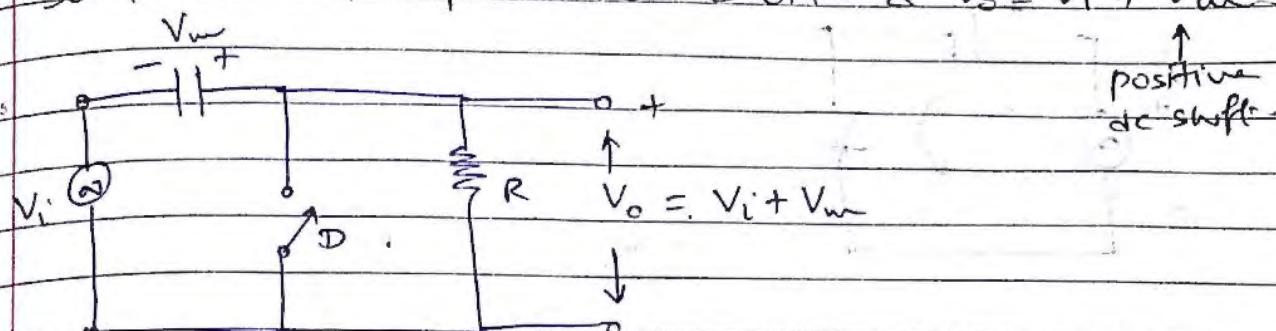So for rest of operation D OFF &  $V_o = V_i + V_m$




(Equivalent Circuit for rest operation)

Waveforms:

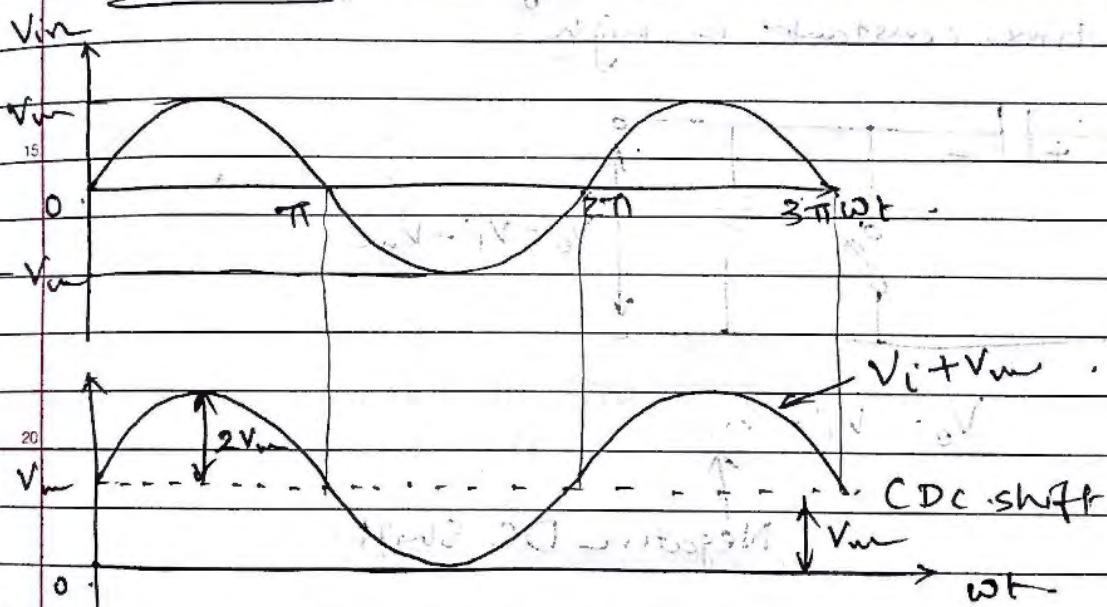


Negative Clamper:

Circuit Diagram:

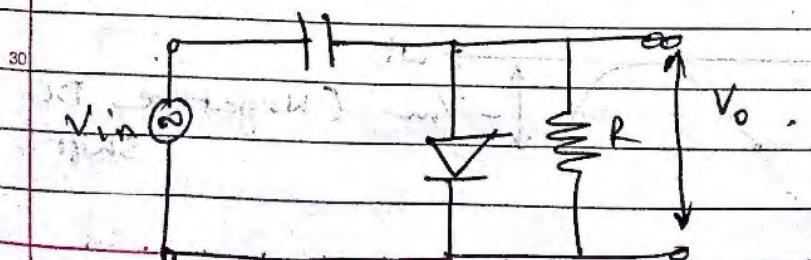

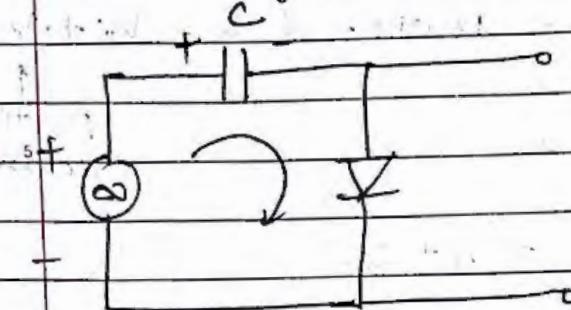→ During first Positive half cycle capacitor will charge as diode will be in forward bias.





→ For Rest of the operation diode will become reverse bias due to charge of capacitor, and capacitor will not discharge through resistor as RC time constant is high.



$$V_o = V_i - V_m$$

↑  
Negative DC Shift.

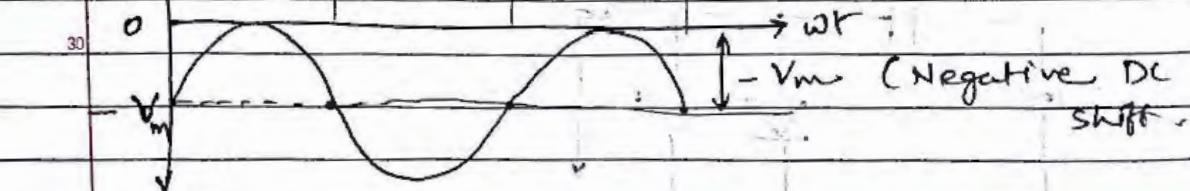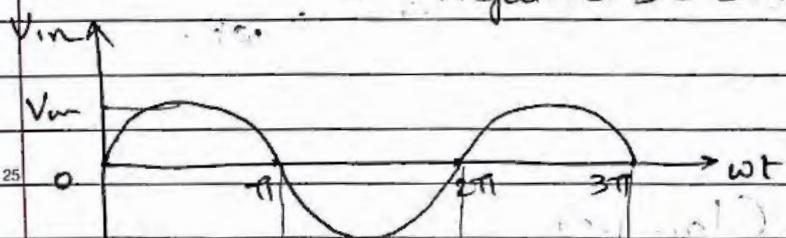


### Biased Clamper:


→ It is possible to obtain DC level shift which is different from  $V_m$ . For this we need to use additional DC source.

### A. Positive biased Clamper:


$$V_c = V_m - V$$

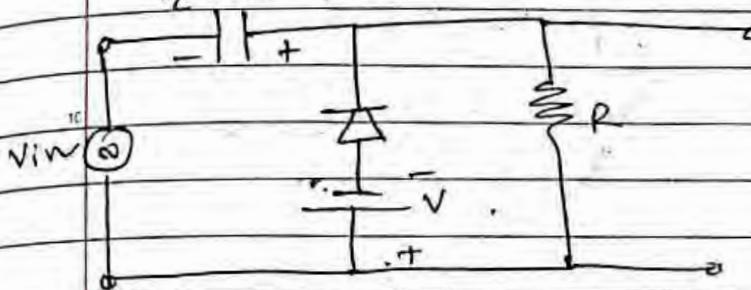

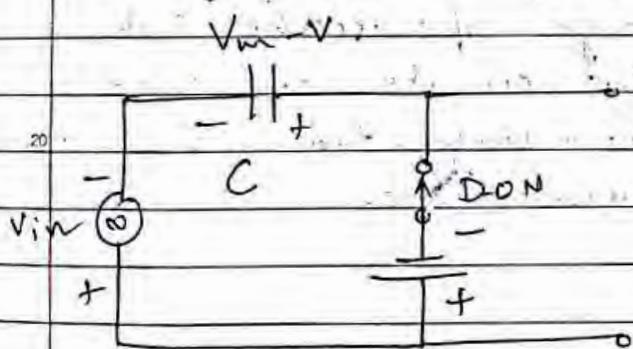
→ During negative half cycle of input, diode will be forward biased & capacitor gets charged to voltage  $(V_m - V)$ , with polarities shown below.



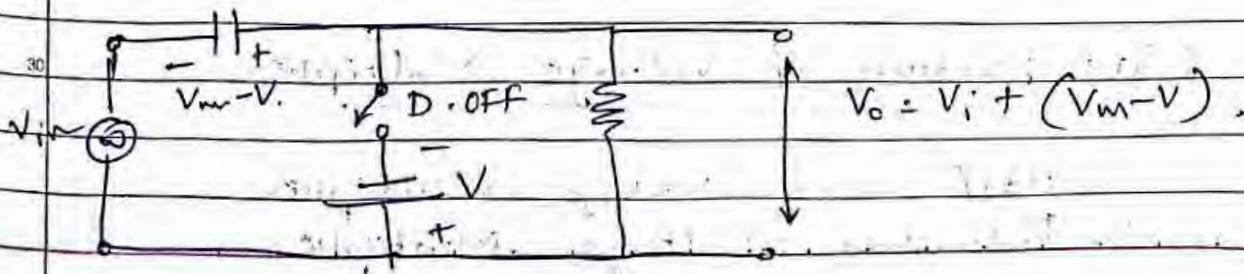→ for rest of the operation, capacitor is fully charged to  $V_m - V$ , and acts as battery, diode will remain permanently reverse biased condition. Circuit is as below.



$$V_o = V_i + (V_m - V)$$

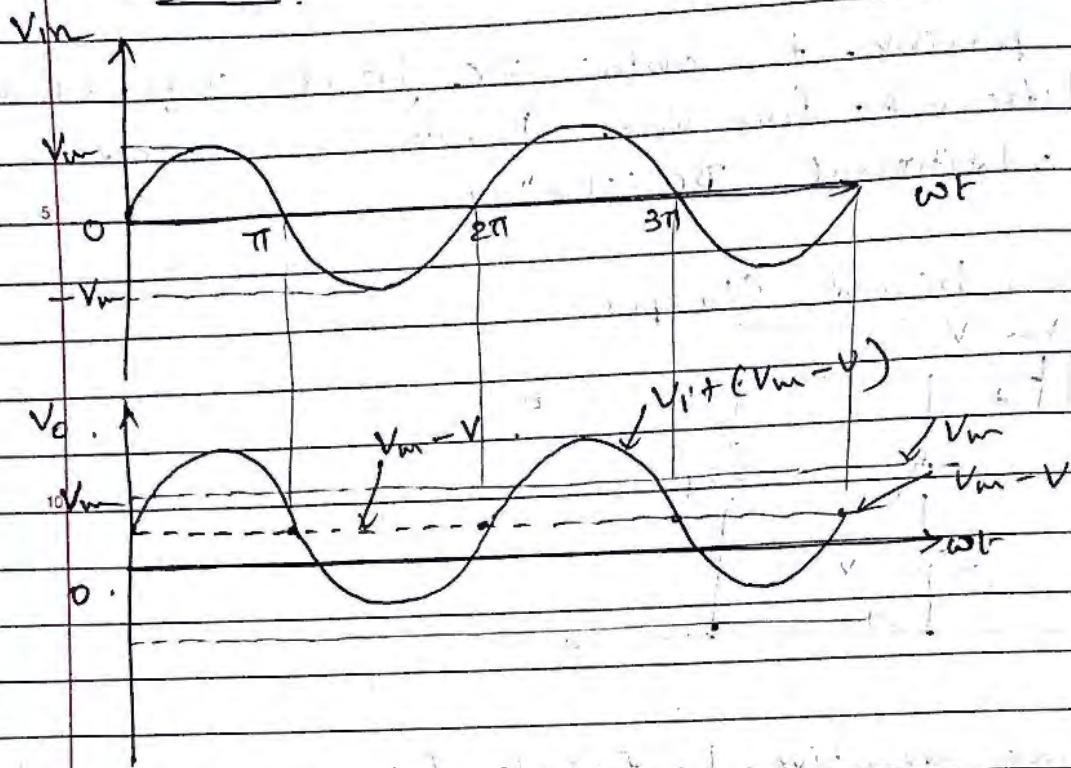Waveforms:Voltage Multiplier Circuits:

- Maximum output voltage of rectifier is  $V_m$ .
- The voltage multiplier circuits are used to obtain higher output voltage than  $V_m$  without changing transformer turns ratio.


Definition:

25) Voltage multiplier is an electrical circuit that converts AC electrical power from lower voltage to higher DC voltage using network of capacitors & diodes.

Classification of Voltage Multiplier:


1. Half wave voltage multiplier
2. Full wave voltage multiplier

## \* Half-wave Voltage Doubler Circuit:

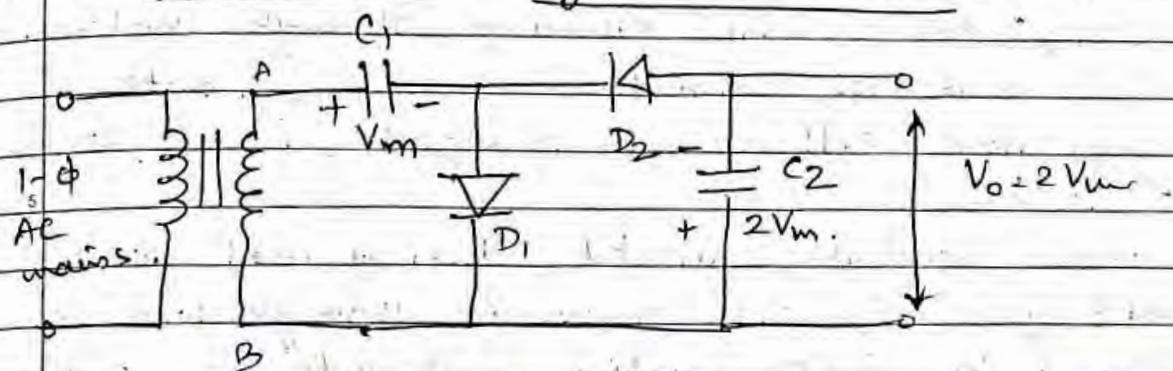


→ Halfwave voltage doubler is shown above.

→ Operation during positive half cycle

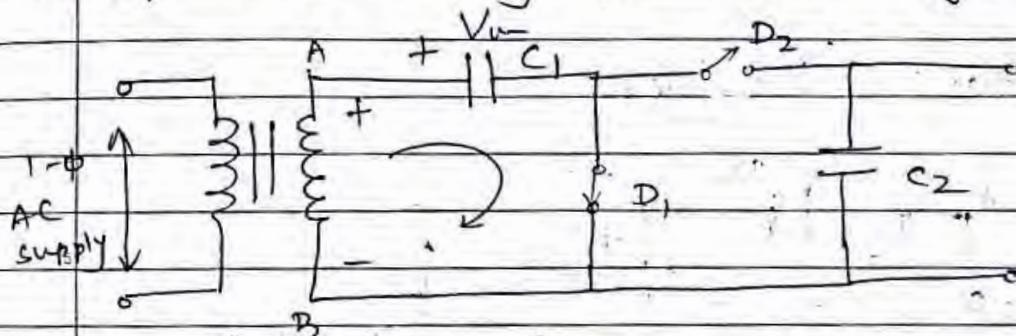

→ Diode  $D_1$  is forward bias &  $D_2$  reverse bias.  
∴  $C_1$  will charge to  $V_m$

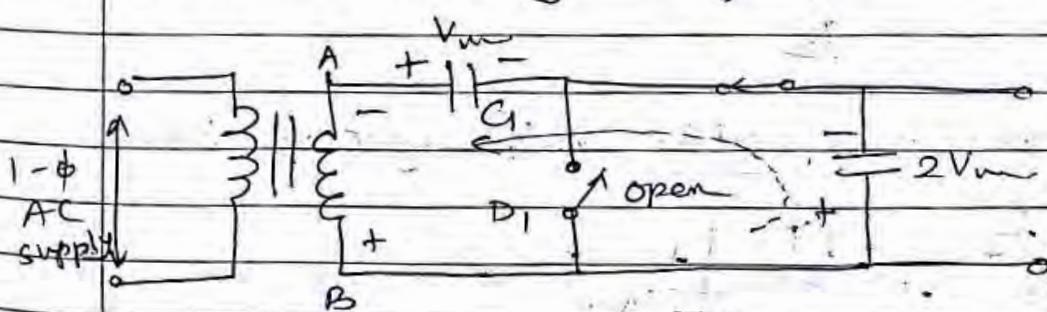→ Operation during Negative half cycle of input:




→ Here  $V_{AB}$  is negative, so  $D_1$  turn off, &  
 $D_2$  turn on.

→ Capacitor  $C_2$  will acquire a voltage of  $2V_m$  with polarities shown in figure.


→  $C_1$  holds the voltage across it constant during the complete negative half cycle.

- In next positive half cycle  $D_2$  is non-conducting & capacitor  $C_2$  will discharge through the load.  
 If load is not connected across  $C_2$ , both capacitors will remain charged, i.e.  $C_1$  to  $V_m$  &  $C_2$  to  $2V_m$ .
- When load is connected during next positive half cycle  $C_2$  will discharge through load & then in next negative half cycle  $C_2$  will charge to  $2V_m$ . PIV Rating of  $D_1$  &  $D_2$  is  $2V_m$ .

### \* Full wave Doubler:

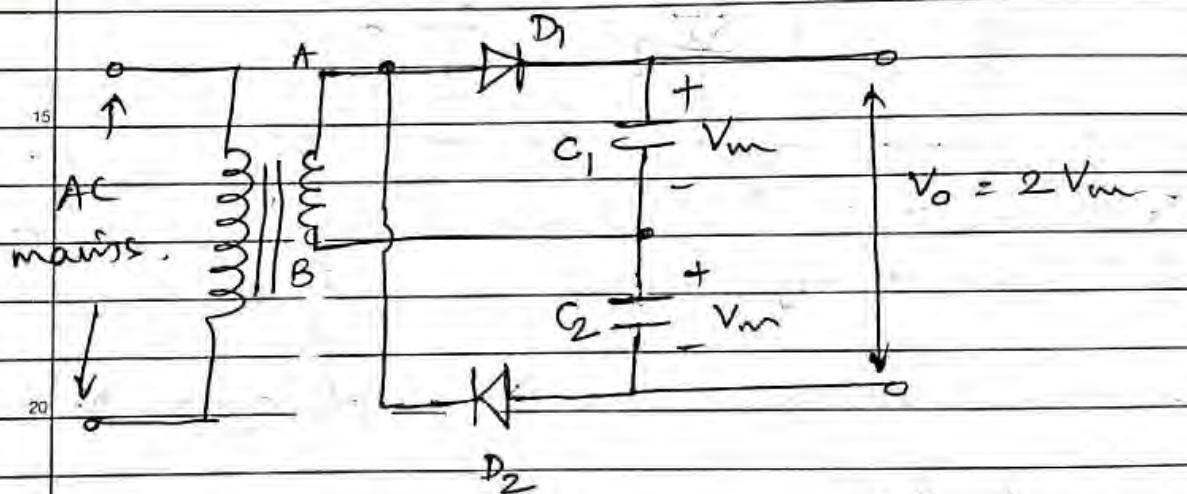


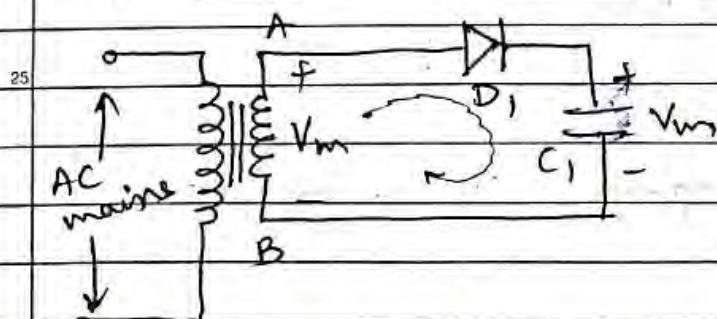Operation in positive half cycle of input:



- In positive half cycle  $V_{AB}$  is positive  
 → Diode  $D_1$  turns on &  $D_2$  turns off,  $C_1$  charges through  $D_1$  to  $V_m$ .

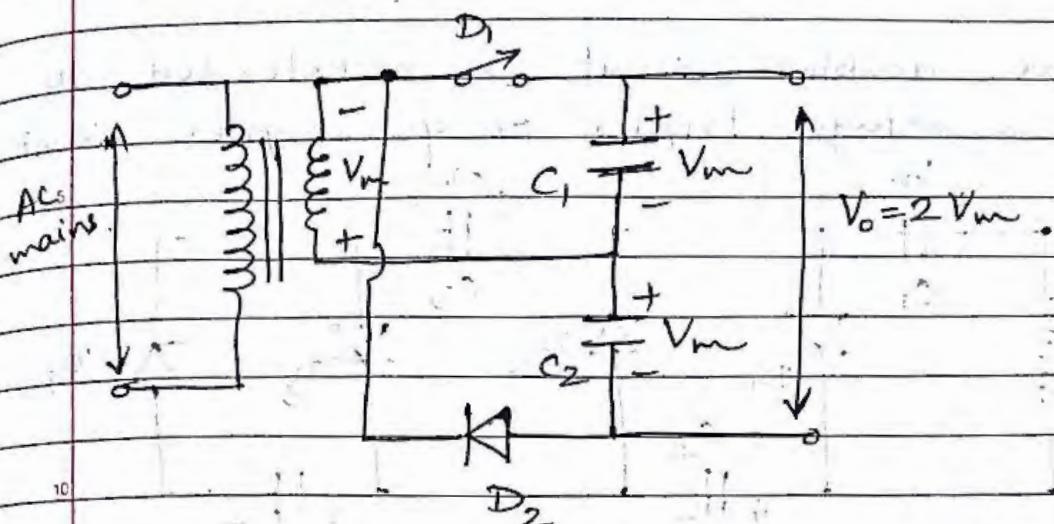Operation in negative half cycle of the input



- During negative half cycle of the input, the secondary voltage \$V\_{AB}\$ is negative
- \$D\_1\$ is reverse biased, \$D\_2\$ is forward biased & \$C\_2\$ charges to \$V\_m\$
- \$V\_o = 2V\_m\$ ie. voltage across two capacitors
- When load is connected, series combination of \$C\_1\$ & \$C\_2\$ will yield a capacitance \$C\$

$$i.e. \quad C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

This will supply load current.


- \$C\_{eq}\$ is lower than \$C\_1\$ as well as \$C\_2\$, so this filter action is poorer than a single capacitor filter circuit.

### PIV Rating of Diode

- PIV rating of diode connected in full wave is \$2V\_m\$.

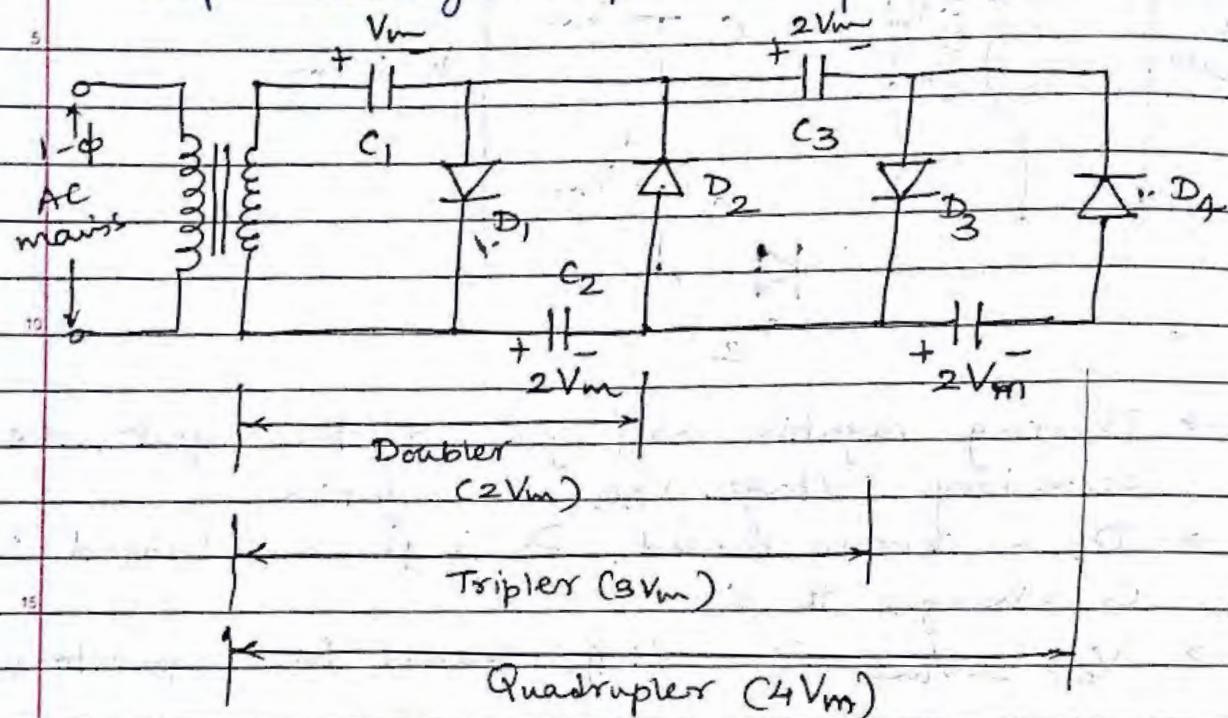
## \* Voltage Tripler & Quadruptier

→ Half wave doubler circuit can be extended to develop a voltage tripler or quadruptier circuit.



→ In the positive half cycle of the input, capacitor C<sub>1</sub> is charged to V<sub>m</sub> through diode D<sub>1</sub> with the polarities as shown.

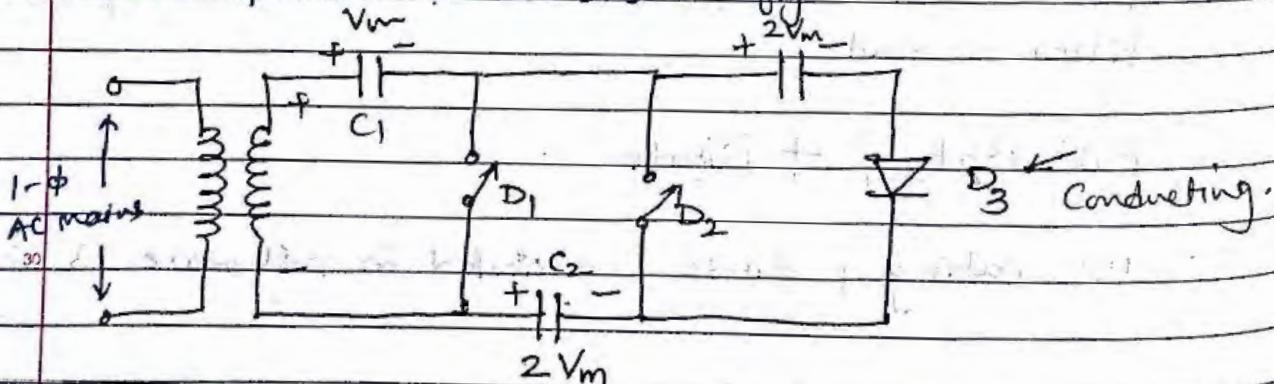→ In the next negative half cycle, the secondary voltage V<sub>AB</sub> is -ve, which turns D<sub>2</sub> on. The capacitor C<sub>2</sub> will charge to 2V<sub>m</sub> with the polarities as shown. fig.




Equivalent Circuit for second positive half-cycle

→ In next positive half cycle of input, diode  $D_3$  is turned ON, As  $V_{in}$  is +ve. This will charge the capacitor  $C_3$  to  $2V_{in}$  as shown in fig.


→ In next positive half cycle, diode  $D_4$  is turned ON, which will charge  $C_4$  to  $2V_{in}$  as shown in fig.

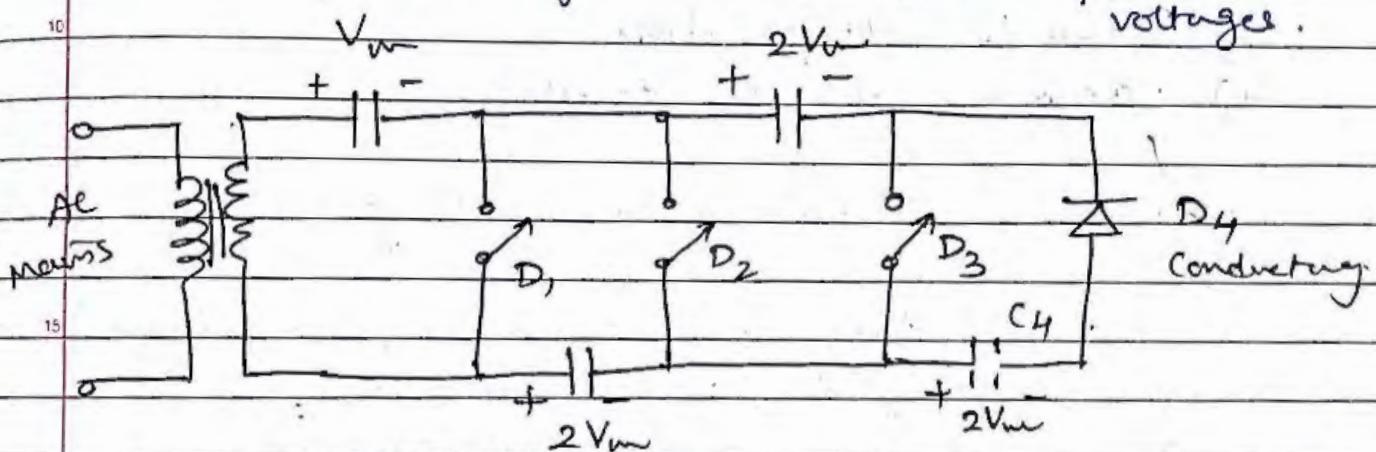→ After charging all capacitors we can tap suitable points to get double, triple or quadruple voltage.



Equivalent Circuit for second negative half cycle.

N - Fold Voltage Multiplier:

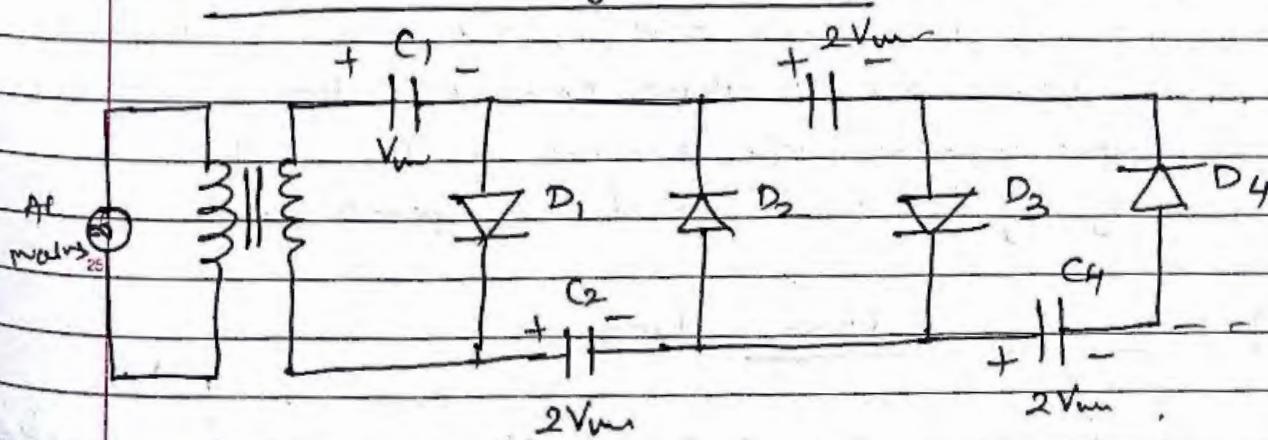

## \* Reading Data sheet of diode.

- The manufacturers of electronic components list the device specifications in data sheets.
- Some of the specifications of p-n junction diode are as follows:

- 1) Reverse Breakdown Voltage
- 2) Maximum forward current
- 3) Forward voltage drop
- 4) Maximum reverse current.

### 1) Reverse Breakdown Voltage:

It is a maximum reverse peak voltage that can be applied across diode.  
it is same as peak inverse voltage.

### 2) Maximum forward current:

It is defined as the maximum value of forward current that can be allowed to pass through a forward biased diode without damaging it at specific temperature.

### 3) Forward Voltage drop:

It is the anode to cathode voltage measured across forward biased diode, it is denoted by  $V_F$ .  
→ typically  $V_F$  for Si diode is between 0.7 V to 0.9 V

(A) Maximum Reverse current:

This is the reverse current at maximum reverse dc rated voltage.

→ This reverse current includes thermally produced saturation current, & surface leakage current.