

SILVER OAK COLLEGE OF ENGINEERING & TECHNOLOGY
ADITYA SILVER OAK INSTITUTE OF TECHNOLOGY
BE - SEMESTER-II • MID SEMESTER-II EXAMINATION – SUMMER 2019

SUBJECT: Basic Electronics (3110016) (EE/CE/IT/EC)

DATE: 26-04-2019

TIME: 10:30 am to 12:00 pm

TOTAL MARKS:40

- Instructions:** 1.Q. 1 is compulsory.
2. Figures to the right indicate full marks.
3. Assume suitable data if required.

- Q.1* (a) Why BJT is called Current Controlled device and FET is Voltage Controlled? [03]
- (b) Derive the relation between α and β . [03]
- (c) Compare CB, CC and CE Configurations. [04]

- Q.2 (a) Draw and explain Input - Output characteristics of CE transistor configuration. [06]
- (b) Draw structure of n-channel JFET and explain its working. [05]
- (c) Draw circuit of transistor as a switch and explain its applications. [04]

OR

- Q.2 (a) List the Biasing methods of transistor. Draw and explain the circuit of voltage divider biasing. [06]
- (b) Draw drain characteristics & Transfer Characteristics of JFET with neat diagram [05]
- (c) Explain DC load line and locate coordinates of Q-point for any transistor configuration. [04]

- Q.3 (a) Describe briefly construction and working of n channel Depletion type MOSFET. [06]
- (b) State the three regions of BJT and explain construction characteristics of each region [05]
- (c) Explain the basic principles of operation of LED and Photodiode. [04]

OR

- Q.3 (a) A Transistor is connected in CE configuration in which collector supply is 8 V, [06]
and the voltage drop across resistance in R_C connected in collector circuit is 0.5
V. The value of R_C is $800\ \Omega$, if $\alpha = 0.96$,

Determine : a) V_{CE} b) I_B c) β

- (b) Describe briefly construction & working of n-channel Enhancement type [05]
MOSFET.

- (c) Write Short Note on Varactor diode. [04]

.....